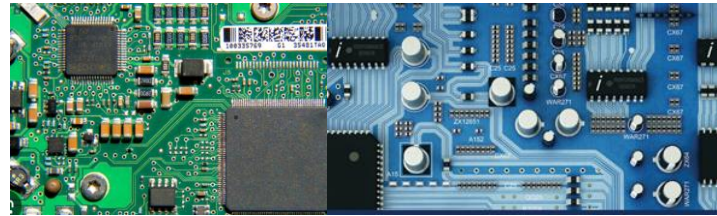




电子科技大学  
格拉斯哥学院  
Glasgow College, UESTC



# Circuit Analysis and Design

Academic year 2025/2026 – Lecture 5


Muhammad Aslam, Masood Ur Rahman, Ali Imran

{Muhammad.Aslam.2, Masood.UrRehman, Ali.Imran}@glasgow.ac.uk

*“A good student never steal or cheat”*
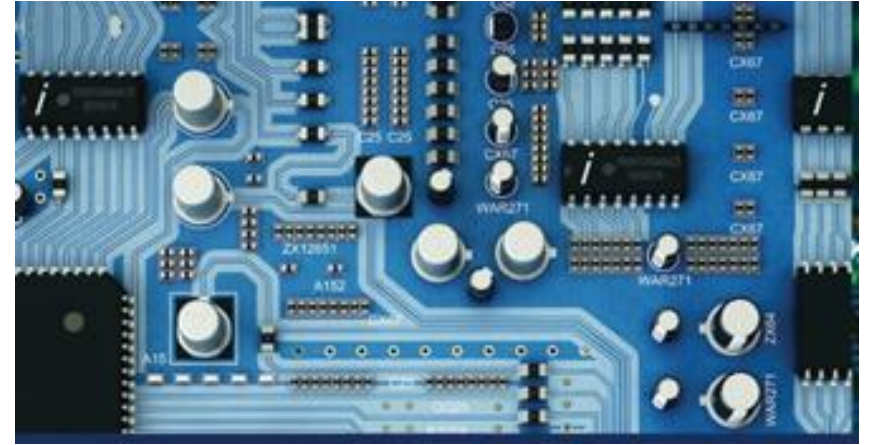
# Agenda

- ❑ Nodal analysis
- ❑ Supernode
- ❑ Summary



# Nodal analysis

❑ It is defined as

*“The method for calculating the **voltage** at the circuit nodes.”*

❑ By knowing the voltages of the Nodes,

- All other voltages, All currents and power can be calculated.

❑ Following are the laws that useful in nodal analysis:

- **Kirchhoff's current law**
- Ohm's law
- Solve equations

# Nodal Analysis – Key Features

- ❑ Nodal analysis is an application of **Kirchhoff's current law**.
- ❑ When there are '**n**' nodes in a given electrical circuit, there will be '**n-1**' simultaneous **equations** to be solved.
- ❑ To obtain all the node voltages, '**n-1**' equations should be solved.
- ❑ The number of non-reference nodes and the number of nodal equations obtained are equal.

# Nodal Analysis

- ❑ **Nodal analysis** is a method of finding all the **unknown node voltages** of a circuit.
- ❑ The method is based on **Kirchhoff's current law (KCL)**: The sum of the currents leaving a node is zero.
- ❑ Nodes can be labeled 1, 2, 3, . . . , or a, b, c, . . . (0 can be used for the reference node), and voltages on these nodes can be labeled  **$V_1, V_2, V_3, \dots$** , or  $V_a, V_b, V_c, \dots$
- ❑ The node voltage of a reference node (0 V) and nodes with specified voltage sources to a reference node are known.
- ❑ For each node whose voltage is unknown, we can write a **node-voltage equation** by summing the currents leaving (entering, or some entering and the rest leaving) the node. This is tantamount to writing KCL at each node.
- ❑ The currents leaving the node through resistors can be found by applying **Ohm's law**.
- ❑ A solution to the node voltages is obtained by solving the set of node-voltage equations.
- ❑ Once all the node voltages are computed, the current in each branch can be found using **Ohm's law**.

# Nodal Analysis : Key steps

Following main steps to be followed to solve any electrical circuit using nodal analysis:

## ❑ **Step 1: Identification of Essential Nodes:**

- Identify principal nodes/essential nodes and select one of them as a reference node. This reference node will be treated as the ground. (0 voltage)
- Essential nodes/principal nodes are usually nodes with more than two branches

## ❑ **Step 2: Labelling the Essential Nodes with Unknown Voltages :**

- Label all the unknown node voltages with respect to the ground for all the principal nodes except the reference node and the nodes whose voltage is known .

## ❑ **Step 3: Writing Equations by applying KCL each Unknown Voltage Nodes.**


- The nodal equations at all the nodes except the reference node should have a nodal equation. The nodal equation is obtained from **Kirchhoff's current law** and then from Ohm's law.

## ❑ **Step 4: Solve the equations**

- Solve the equations of each node to get the required variables.
  - Substitution method
  - Cramer's Rule
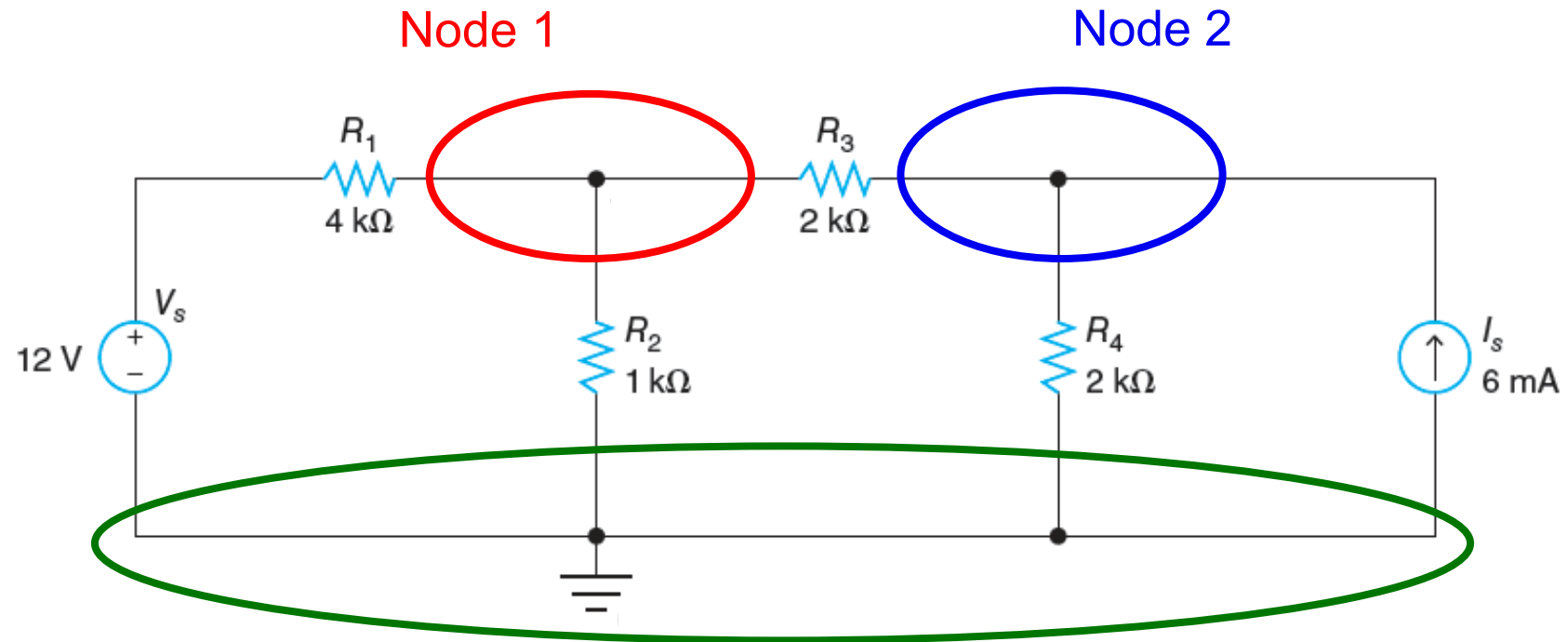
# A Circuit with Two Unknown Node Voltages

□ **Step 1:** Identify essential nodes and Label them



Reference Node Voltage is 0

Figure 3.1

# A Circuit with Two Unknown Node Voltages

□ **Step 2:** Label the unknown Voltages


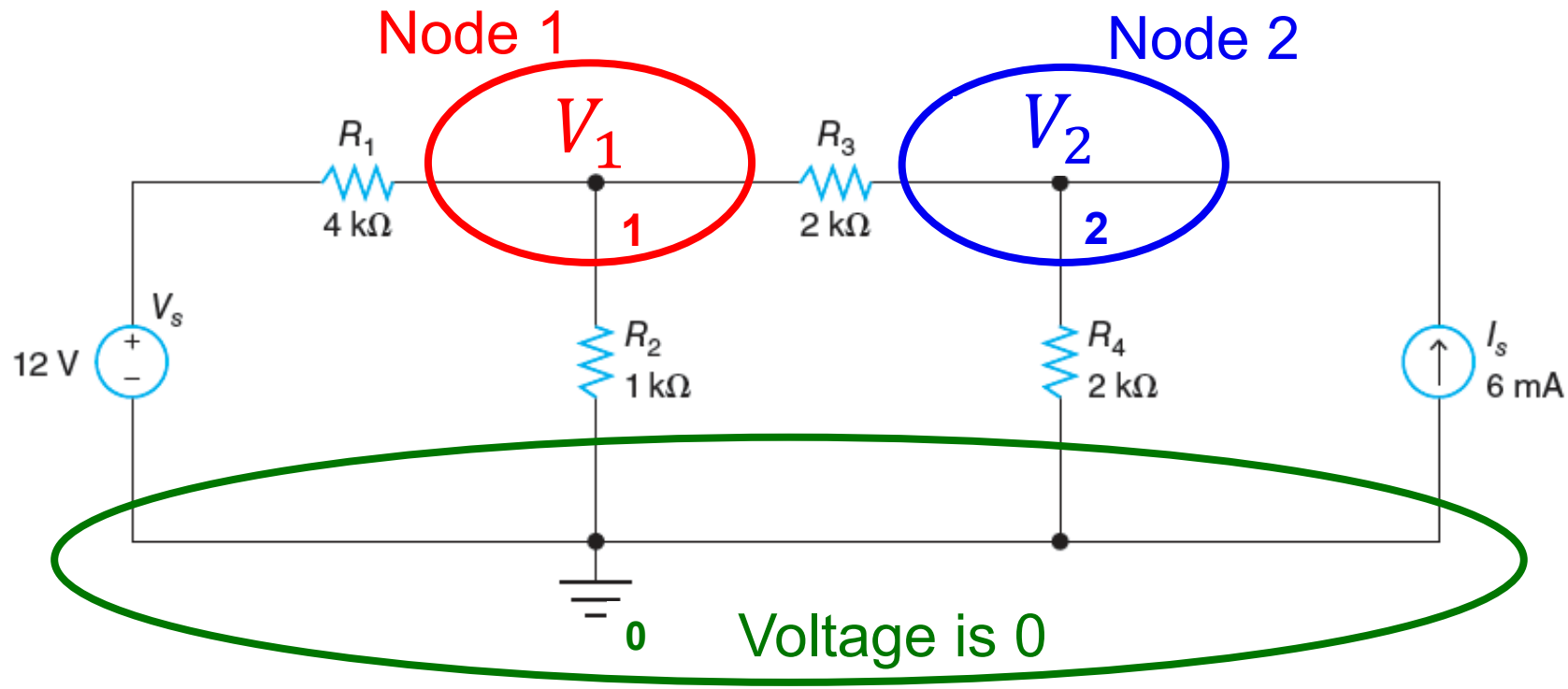


Figure 3.1

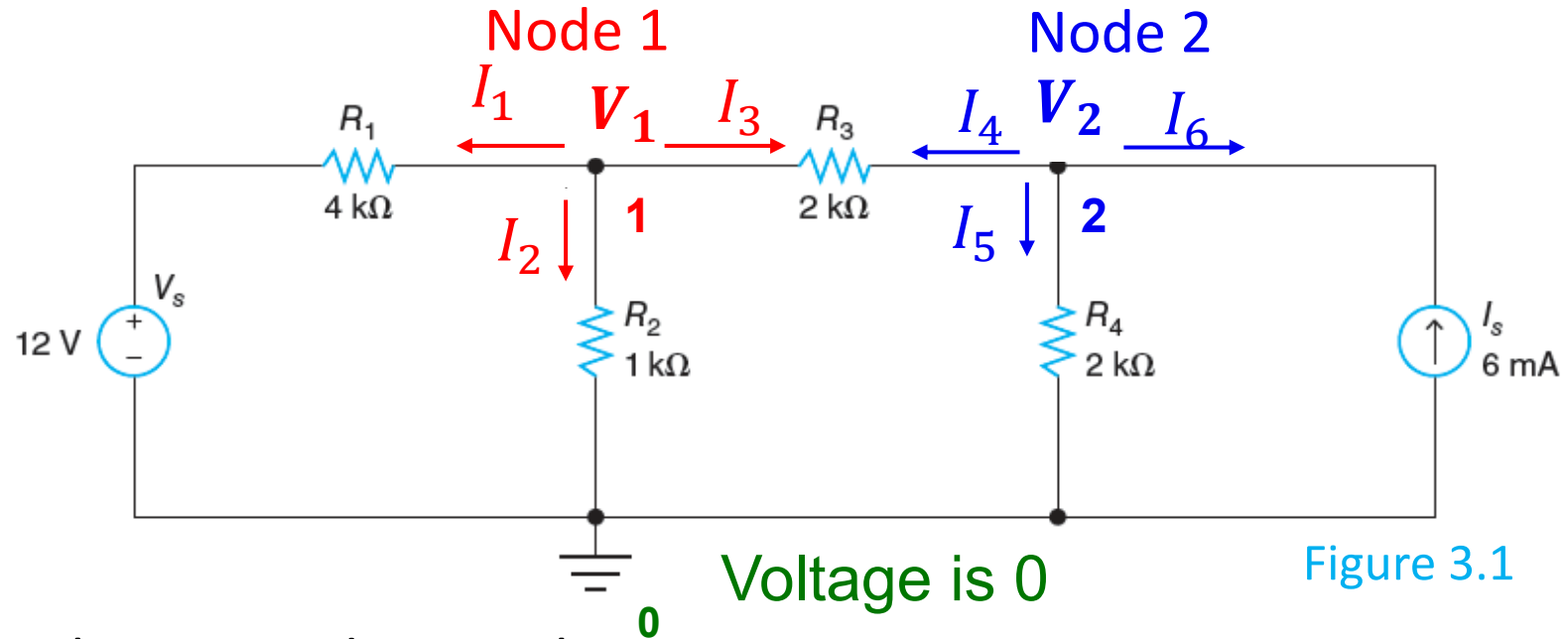

# A Circuit with Two Unknown Node Voltages




- ❑ **Step 3:** Applying KCL at each unknown node to make equations
  - **Two: Unknowns Nodal Voltages**, Apply **Two KCLs** at these nodes and get **Two: Linear Equations** (1) KCL at Node 1 → Get 1<sup>st</sup> Equation (2) KCL at Node 2 → Get 2<sup>nd</sup> Equation
- ❑ **Step 4:** Solve the two Linear Equations to get  $V_1$  at Node1 and  $V_2$  at Node2
- ❑ With these Nodal voltages we can find all currents and powers in the circuit

# Fill in the blanks



Fill in the Blanks

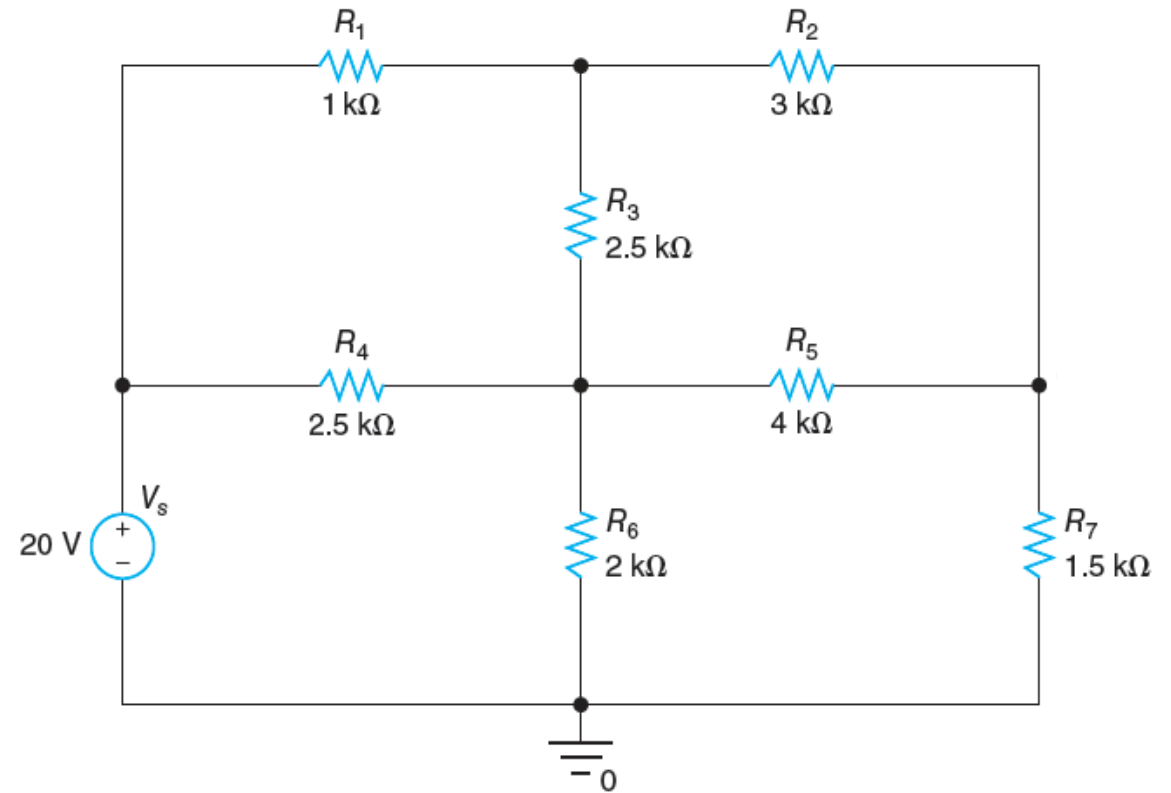

☐ Fill in the blanks

- a) Number of essential nodes \_\_\_\_\_
- b) Number of Unknown voltage nodes \_\_\_\_\_
- c) Number of Equations to be solved \_\_\_\_\_



# Example: Nodal Analysis

❑ Applying KCL at Node 1

❑ Sum of current leaving Node 1 is 0

$$I_1 + I_2 + I_3 = 0$$

❑ By Ohm's Law

$$I_1 = \frac{V_1 - V_s}{R_1} \quad I_2 = \frac{V_1 - 0}{R_2} \quad I_3 = \frac{V_1 - V_2}{R_3}$$

❑ Substitute the currents with the values by Ohm's law


$$\frac{V_1 - V_s}{R_1} + \frac{V_1 - 0}{R_2} + \frac{V_1 - V_2}{R_3} = 0$$

❑ Substituting the values and simplifying the equation will give (1)

$$\frac{V_1 - 12}{4000} + \frac{V_1 - 0}{1000} + \frac{V_1 - V_2}{2000} = 0$$

❑ Multiplying both sides by 4000

$$V_1 - 12 + 4V_1 + 2V_1 - 2V_2 = 0$$

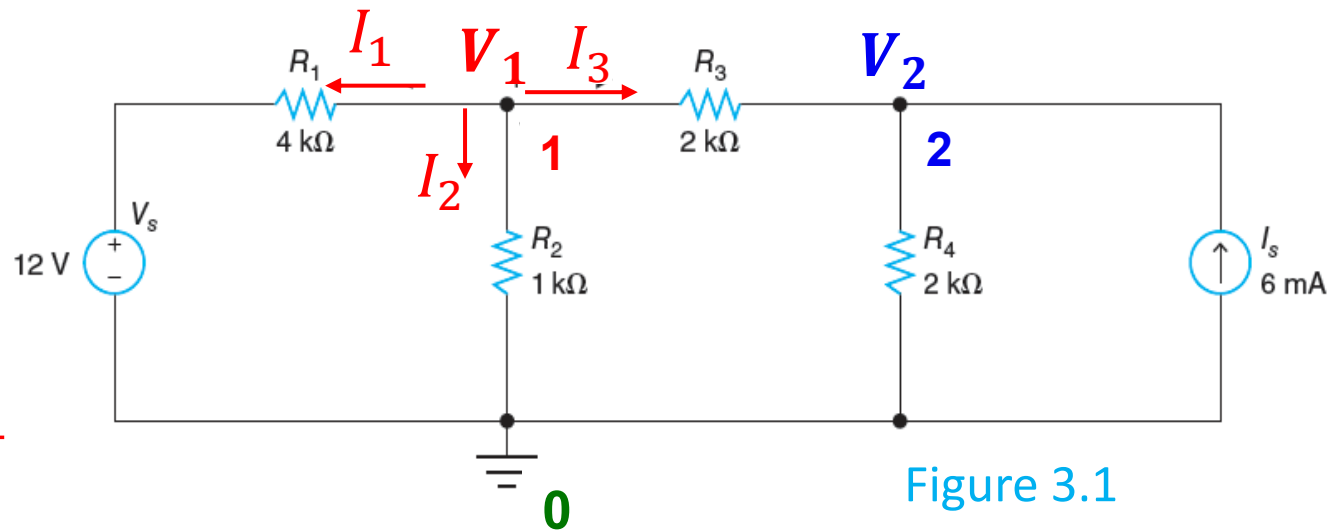

$$7V_1 - 2V_2 = 12 \quad (1)$$

## Example: Nodal Analysis (Continue)

❑ Applying KCL at Node 2

❑ Sum of current leaving Node 2 is 0

$$I_4 + I_5 + I_6 = 0$$

❑ By Ohm's Law

$$I_4 = \frac{V_2 - V_1}{R_3} \quad I_5 = \frac{V_2 - 0}{R_4} \quad I_6 = -I_s$$

❑ Substitute the values by Ohm's Law


$$\frac{V_2 - V_1}{R_3} + \frac{V_2 - 0}{R_4} - I_s = 0$$

❑ Substituting the values and simplifying the equation will give (1)

$$\frac{V_2 - V_1}{2000} + \frac{V_2 - 0}{2000} - 6 \times 10^{-3} = 0$$

$$\boxed{-V_1 + 2V_2 = 12 \quad (2)}$$

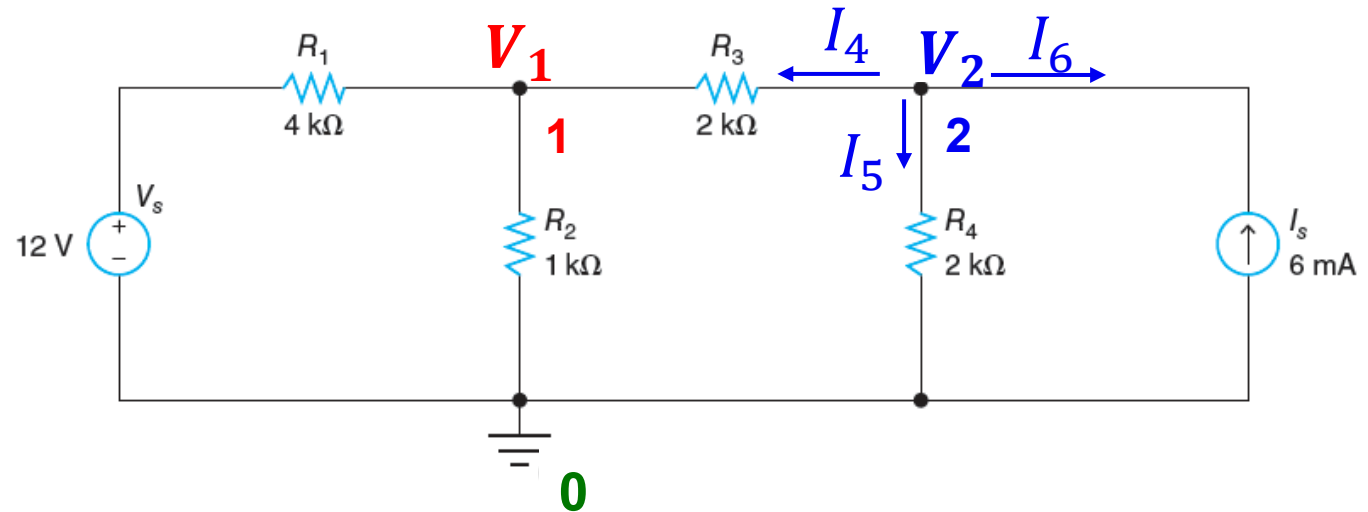❑ Multiply both sides by 2000  $\rightarrow V_2 - V_1 + V_2 - 12 = 0$



## Example: Nodal Analysis (Continue)

□ **Step 4:** Solve the equations (1) and (2)

○ Equation (1) from Node 1


$$7V_1 - 2V_2 = 12 \quad (1)$$

○ Equation (2) from Node 2

$$-V_1 + 2V_2 = 12 \quad (2)$$

○ Adding the (1) and (2) and solving for  $V_1$  and  $V_2$
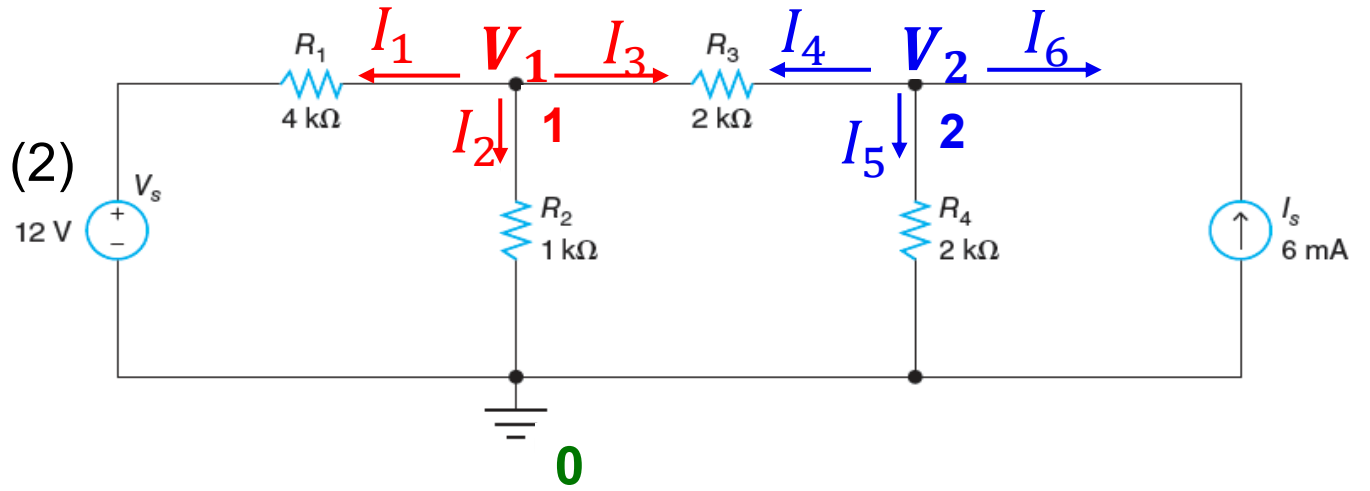
$$7V_1 - 2V_2 - V_1 + 2V_2 = 12 + 12 \quad \rightarrow \quad 6V_1 = 24 \quad \rightarrow \quad V_1 = 4 \quad \text{And} \quad V_2 = 8$$




# EXAMPLE 3.1

❑ Find the nodal voltages at the Unknown Nodes

❑ **Step 1:** Identify Unknown Nodes are ??

❑ **Step 2:** Label Unknown Nodes are ??

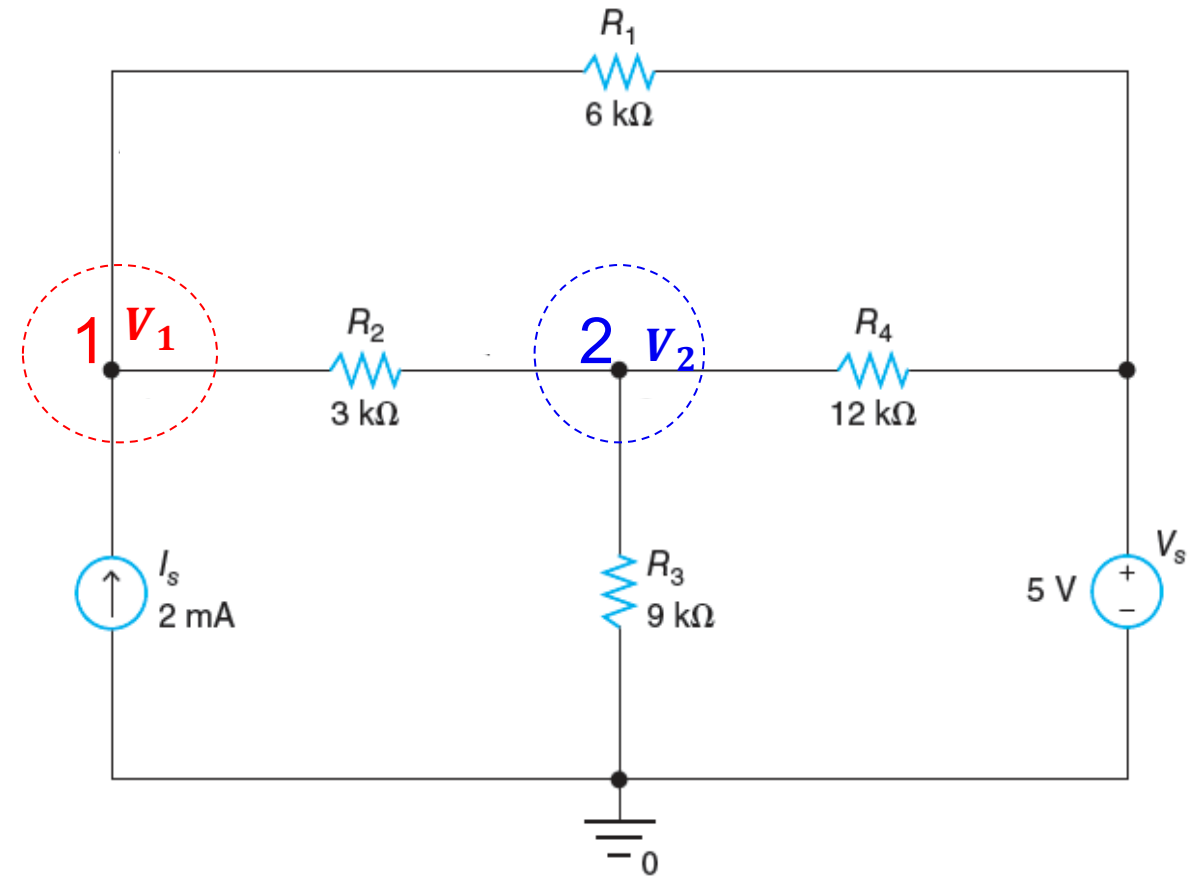

## EXAMPLE 3.1 (Continue)

### □ Step 3: Apply KCL at Node 1

- KCL: Sum of Current Leaving Node 1 is 0

$$I_1 + I_2 + I_3 = 0$$


Note:  $I_3 = -I_s$

- Changing current values with those by Ohm's law

$$\frac{V_1 - V_s}{R_1} + \frac{V_1 - V_2}{R_2} - I_s = 0$$

$$\frac{V_1 - 5}{6000} + \frac{V_1 - V_2}{3000} - 2 \times 10^{-3} = 0$$

$$V_1 - 5 + 2(V_1 - V_2) - 12 = 0$$

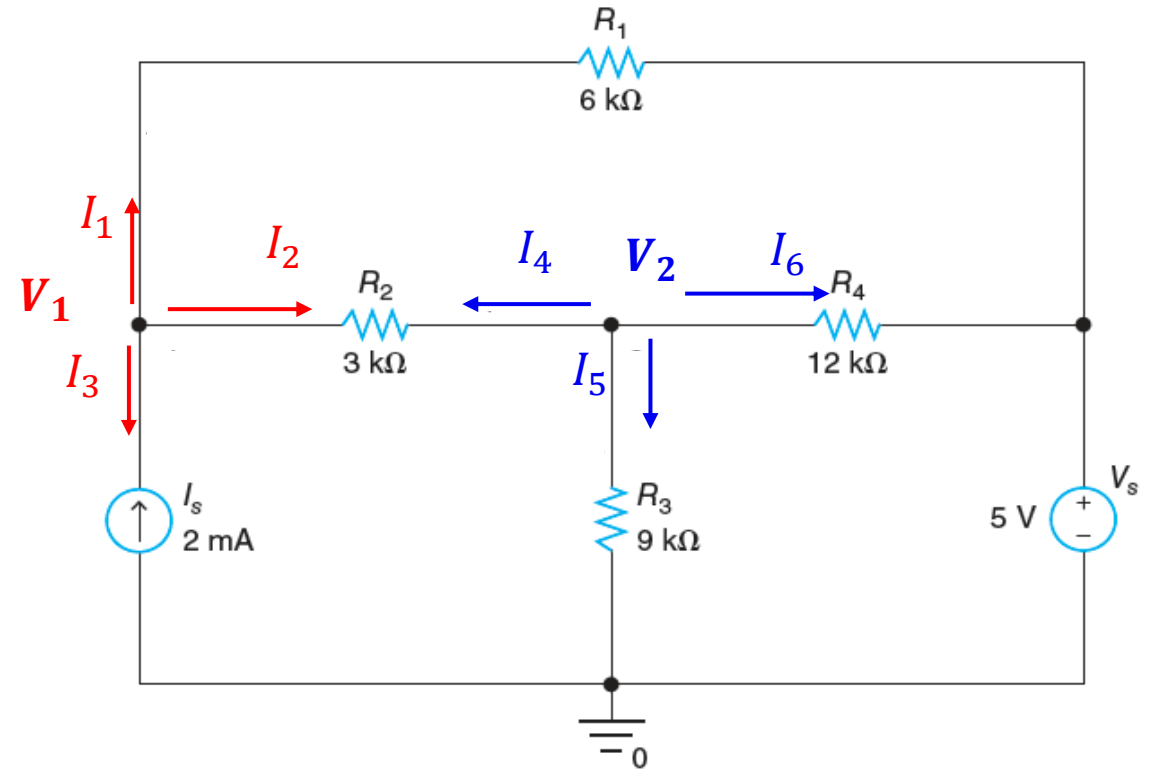

$$3V_1 - 2V_2 = 17 \quad (1)$$

## EXAMPLE 3.1 (Continue )

### □ Step 3: Apply KCL at Node 2

- KCL: Sum of Current Leaving Node 2 is 0

$$I_4 + I_5 + I_6 = 0$$

- Changing current values with those by Ohm's law


$$\frac{V_2 - V_1}{R_2} + \frac{V_2 - 0}{R_3} - \frac{V_2 - V_s}{R_4} = 0$$

$$\frac{V_2 - V_1}{3000} + \frac{V_2}{9000} + \frac{V_2 - 5}{12000} = 0$$

- **Multiplying both sides by 36000**

$$12(V_2 - V_1) + 4V_2 - 3(V_2 - 5) = 0$$

$$12V_2 - 12V_1 + 4V_2 + 3V_2 - 15 = 0$$

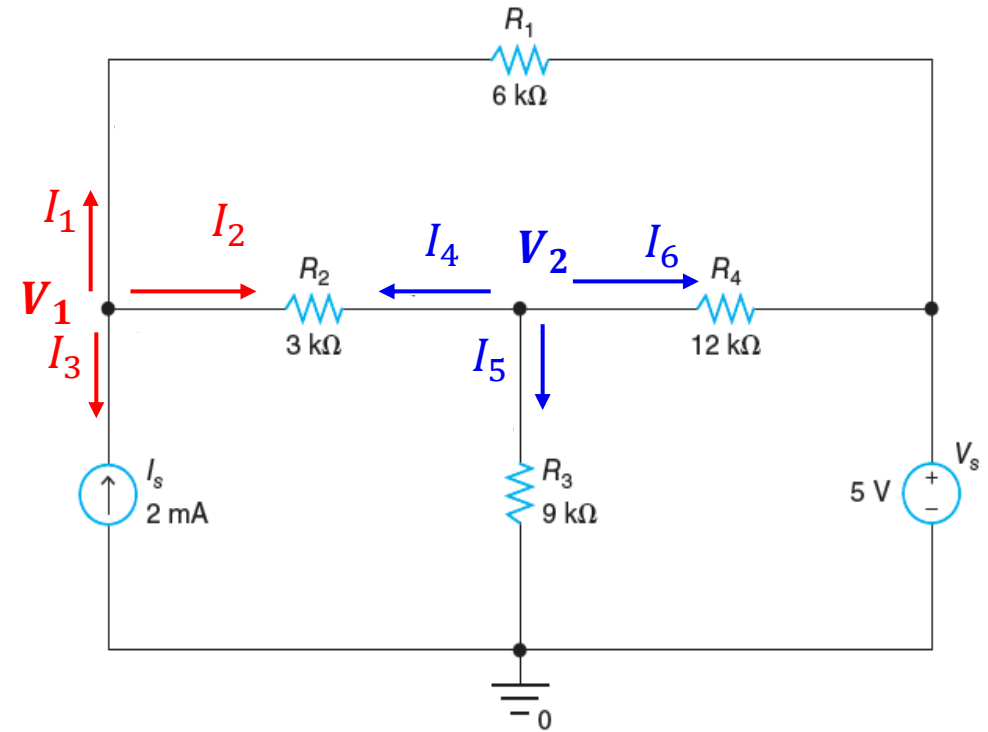

$$-12V_1 + 19V_2 = 15 \quad (2)$$



## EXAMPLE 3.1 (Continue )

□ **Step 4:** Solve the equations (1) and (2)

- Equation 1 from Node 1

$$3V_1 - 2V_2 = 17 \quad (1)$$

- Equation 2 from Node 2

$$-12V_1 + 19V_2 = 15 \quad (2)$$


- Adding the equations (1) and (2) and solving for V1 and V2

$$4(3V_1 - 2V_2) - 12V_1 + 19V_2 = 17 \times 4 + 15$$

$$11V_2 = 83$$

$$V_2 = 7.5454$$


$$V_1 = 10.6969$$

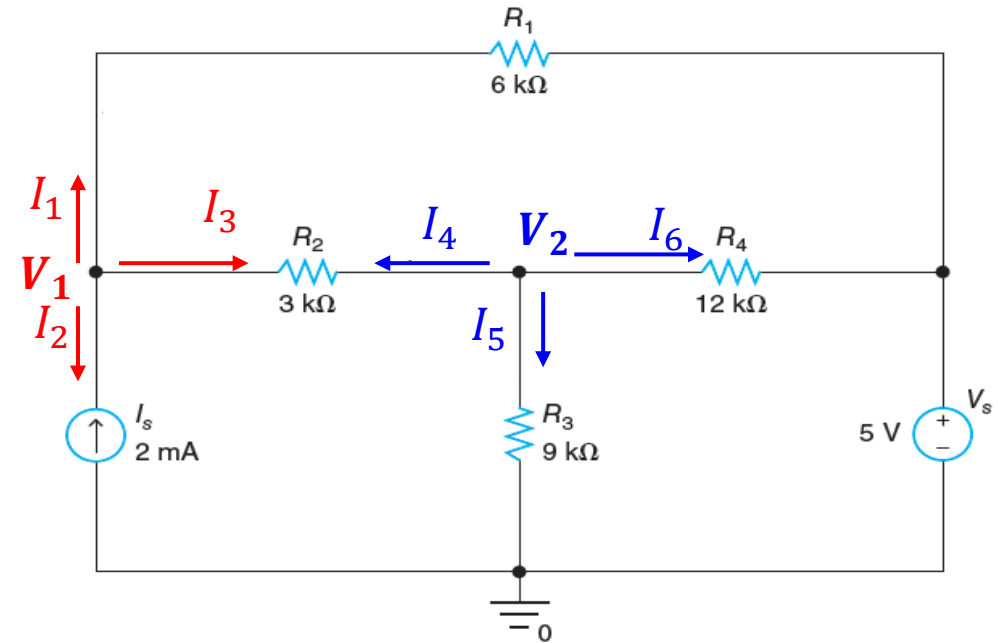

# Class Task

Find nodal voltages

★ Multiple Choice

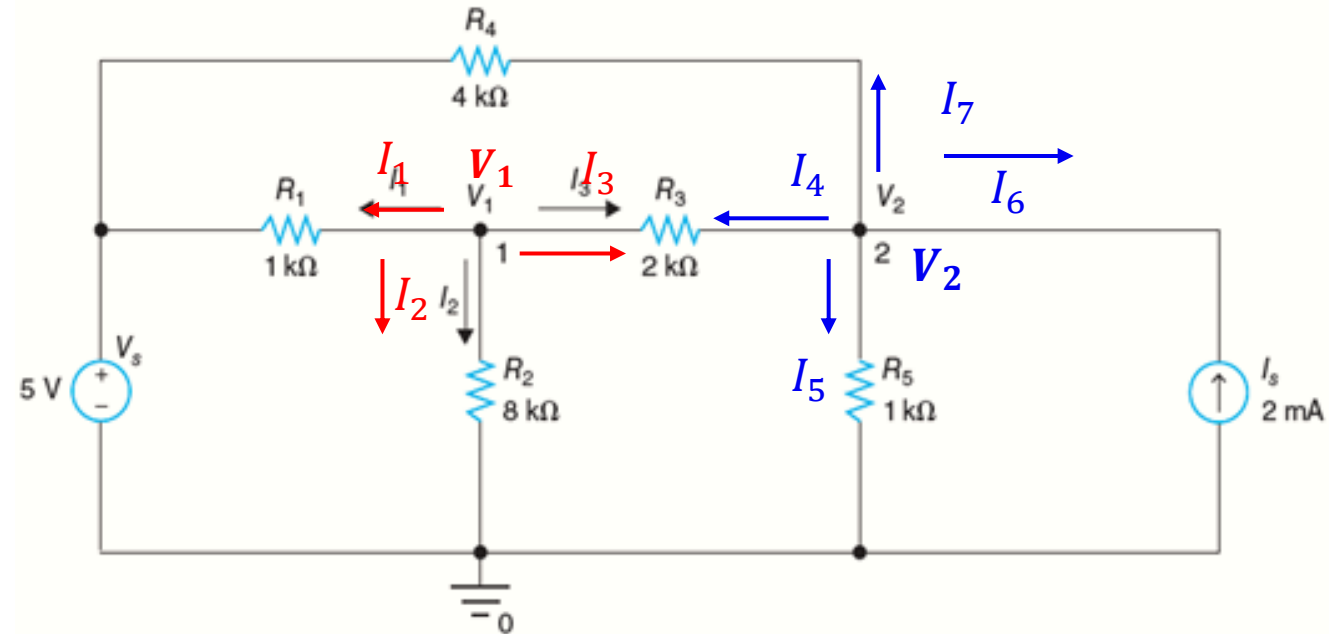

Options


- A.  $V_1 = 3V$ ,  $V_2 = 4V$
- B.  $V_1 = 4V$ ,  $V_2 = 3V$
- C.  $V_1 = 6V$ ,  $V_2 = 4V$



## EXAMPLE 3.3

□ Step 1: Identify Essential nodes

□ Step 2: Label the nodes

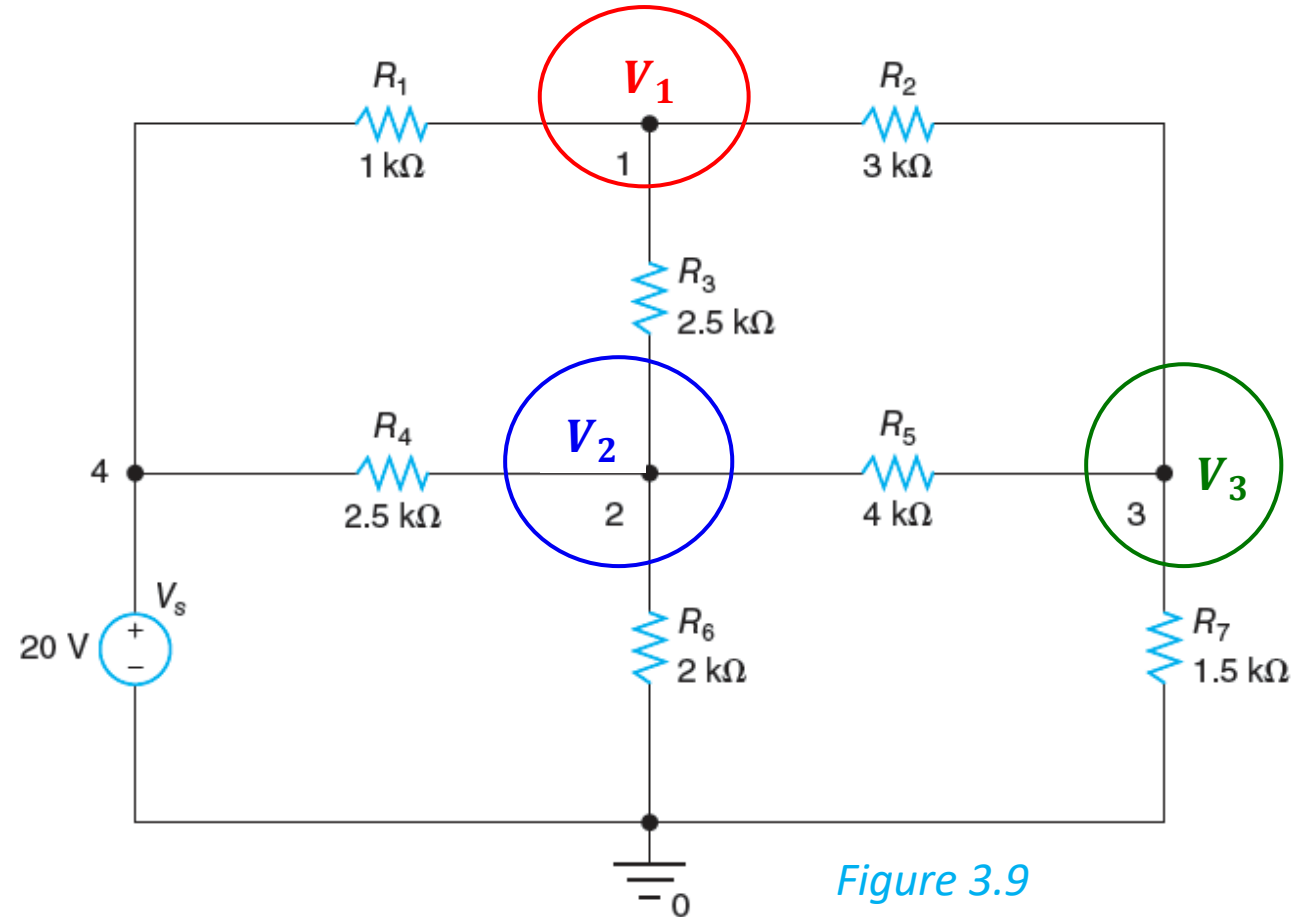

## EXAMPLE 3.3 (Continue )

□ Step3: Apply KCL at **Node 1**, **Node 2** and **Node 3**


○ Sum the currents at node 1:  $\frac{V_1 - 20}{1000} + \frac{V_1 - V_2}{2500} + \frac{V_1 - V_3}{3000} = 0$

○ Multiply by 15000:

$$15V_1 - 300 + 6V_1 - 6V_2 + 5V_1 - 5V_3 = 0 \Rightarrow \mathbf{26V_1 - 6V_2 - 5V_3 = 300} \quad (1)$$

○ Sum the currents leaving node 2  $\Rightarrow \frac{V_2 - 20}{2500} + \frac{V_2 - V_1}{2500} + \frac{V_2 - V_3}{4000} + \frac{V_2}{2000} = 0$

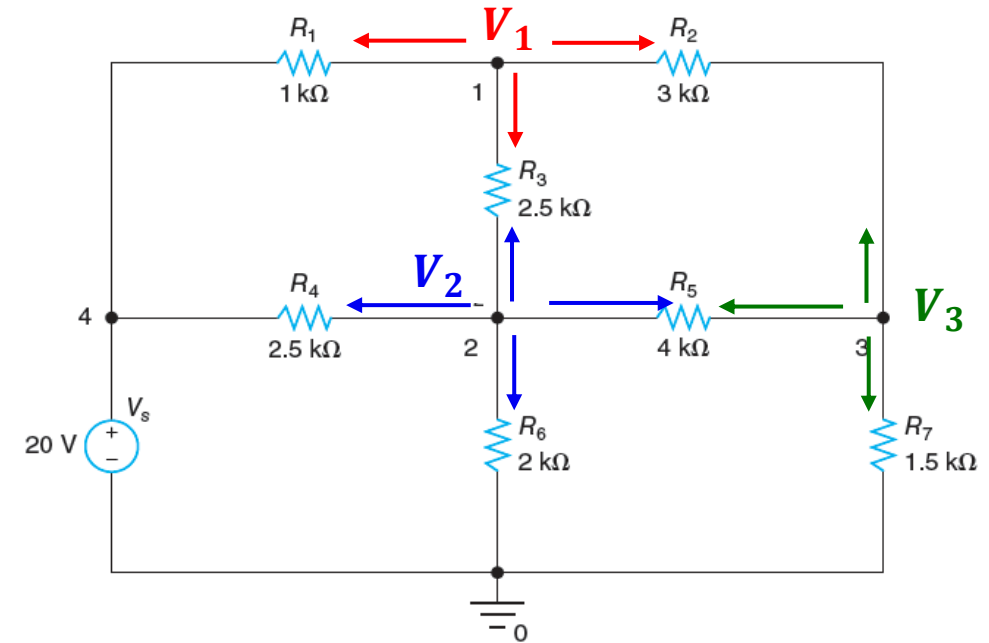○ Multiply by 20000:  $8V_2 - 160 + 8V_2 - 8V_1 + 5V_2 - 5V_3 + 10V_2 = 0 \Rightarrow \mathbf{-8V_1 + 31V_2 - 5V_3 = 160} \quad (2)$



## EXAMPLE 3.3 (Continue )

❑ **Step 3** : Apply KCL at Node 3 Sum the currents leaving **node 3**:

$$\frac{V_3 - V_1}{3000} + \frac{V_3 - V_2}{4000} + \frac{V_3}{1500} = 0$$

❑ Multiply by 12000:


$$4V_3 - 4V_1 + 3V_3 - 3V_2 + 8V_3 = 0 \Rightarrow -4V_1 - 3V_2 + 15V_3 = 0 \quad (3)$$

❑ Multiply (1) ( $26V_1 - 6V_2 - 5V_3 = 300$ ) by 3  $\Rightarrow 78V_1 - 18V_2 - 15V_3 = 900 \quad (4)$


❑ Add (3) and (4)  $\Rightarrow 74V_1 - 21V_2 = 900 \quad (5)$

❑ Multiply (2) ( $-8V_1 + 31V_2 - 5V_3 = 160$ ) by 3:  $-24V_1 + 93V_2 - 15V_3 = 480 \quad (6)$

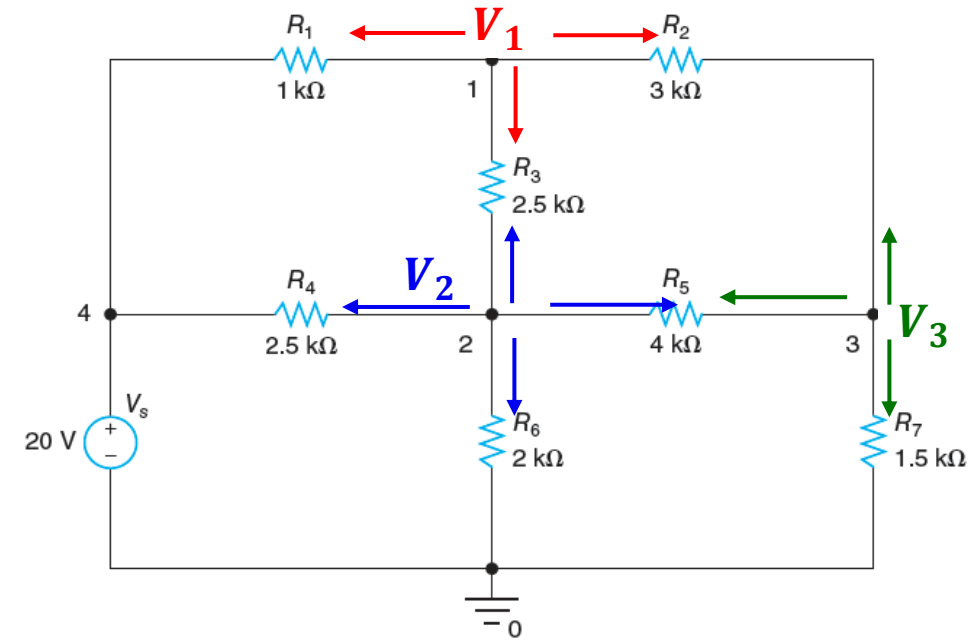❑ Add (3) and (6):  $-28V_1 + 90V_2 = 480 \quad (7)$



## EXAMPLE 3.3 (Continue )

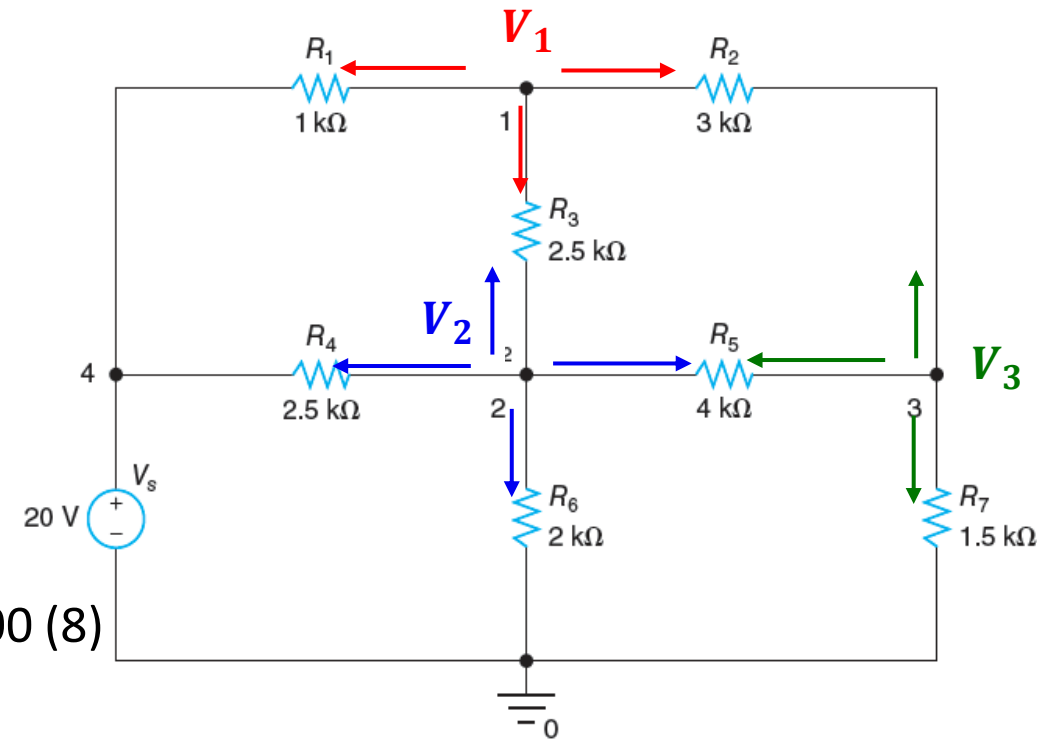

- Multiply (5) ( $74V_1 - 21V_2 = 900$ ) by 30  $\Rightarrow 2220V_1 - 630V_2 = 27000$  (8)
- Multiply (7) ( $-28V_1 + 90V_2 = 480$ ) by 7  $\Rightarrow -196V_1 + 630V_2 = 3360$  (9)
- Add (8) and (9)  $\Rightarrow 2024V_1 = 30360 \Rightarrow \mathbf{V_1 = 15\text{ V} (11)}$
- Substitute (11) in (8)  $\Rightarrow \mathbf{V_2 = (2220V_1 - 27000)/630 = 10\text{ V} (12)}$
- Substitute (11) and (12) in (1)  $\Rightarrow \mathbf{V_3 = (26V_1 - 6V_2 - 300)/5 = 6\text{ V}}$

# Solving Equations Methods

□ If we have two or more linear equations, we can solve them in different methods.

Two popular methods are

1. Substitution Method
2. Cramer's Rule

## □ Substitution Method

- Solve the equations using simple substitution methods as we did in the examples above

## □ Cramer's Rule

- Read in the book to apply Cramer's Rule in solving equations OR
- Go to this website to know about Cramer Rule

<https://www.purplemath.com/modules/cramers.htm>

## EXAMPLE 3.4

□ Find  $V_1$  and  $V_2$

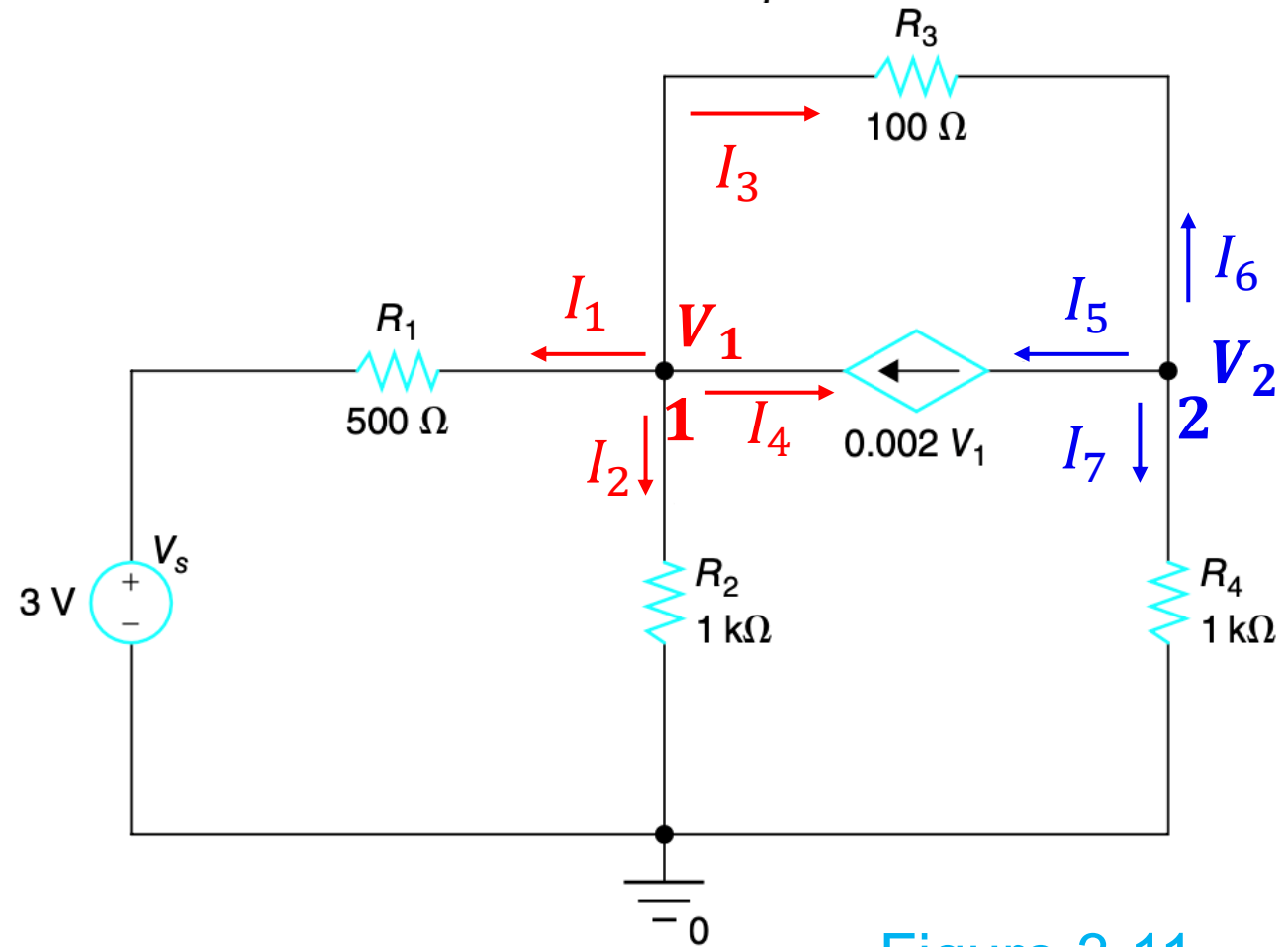


Figure 3.11



## EXAMPLE 3.4 (Cont..)

□ Apply KCL at **Node 1**

○ Sum of current at Node 1 = 0

$$I_1 + I_2 + I_3 + I_4 = 0$$

$$I_4 = -I_5 = 0.002V_1$$


○ Changing current values with those by Ohm's law

$$\frac{V_1 - V_s}{500} + \frac{V_1 - 0}{1000} + \frac{V_1 - V_2}{100} - 0.002V_1 = 0$$

$$\frac{V_1 - 3}{500} + \frac{V_1}{1000} + \frac{V_1 - V_2}{100} - 0.002V_1 = 0$$

○ Multiplying both sides by 1000
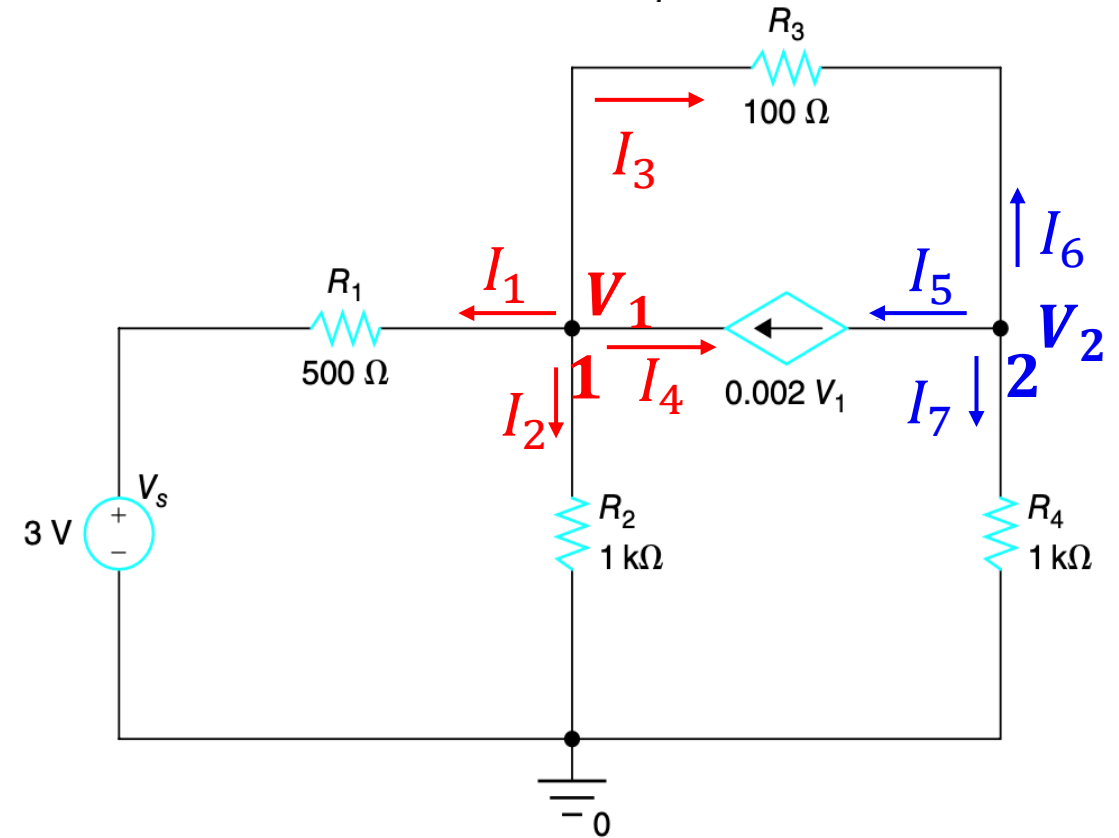
$$2V_1 - 6 + V_1 + 10V_1 - 10V_2 - 2V_1 = 0$$



$$11V_1 - 10V_2 = 6 \quad (1)$$

## EXAMPLE 3.4 (Cont..)

### □ Apply KCL at **Node 2**

- Sum of current at Leaving **Node 2** = 0

$$I_5 + I_6 + I_7 = 0$$


$$I_5 = 0.002V_1$$

- Changing current values with those by Ohm's law

$$0.002V_1 + \frac{V_2 - V_1}{100} + \frac{V_2 - 0}{1000} = 0$$

- Multiplying both sides by 1000

$$2V_1 + 10V_2 - 10V_1 + V_2 = 0$$

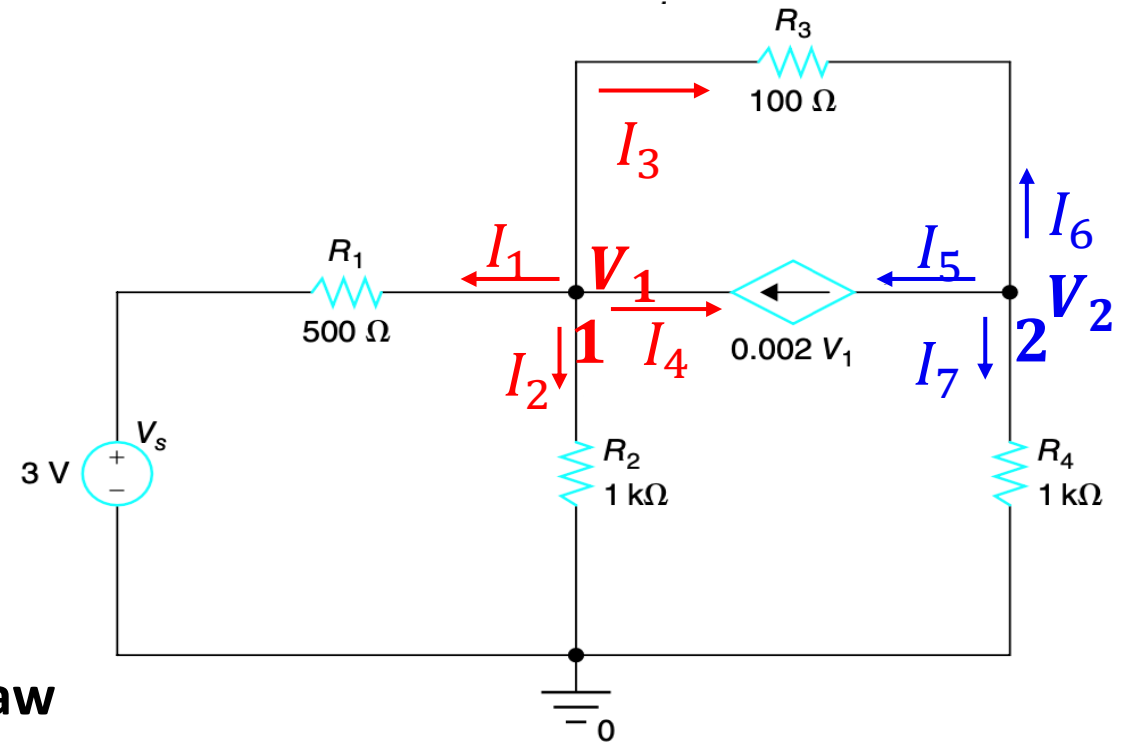

$$-8V_1 + 11V_2 = 0 \quad (2)$$

## EXAMPLE 3.4 (Cont..)


- Two equations after applying KCL at Node 1 and Node 2 are:

$$11V_1 - 10V_2 = 6 \quad (1)$$

$$-8V_1 + 11V_2 = 0 \quad (2)$$

- Solving the Equation (1) and (2), we should get

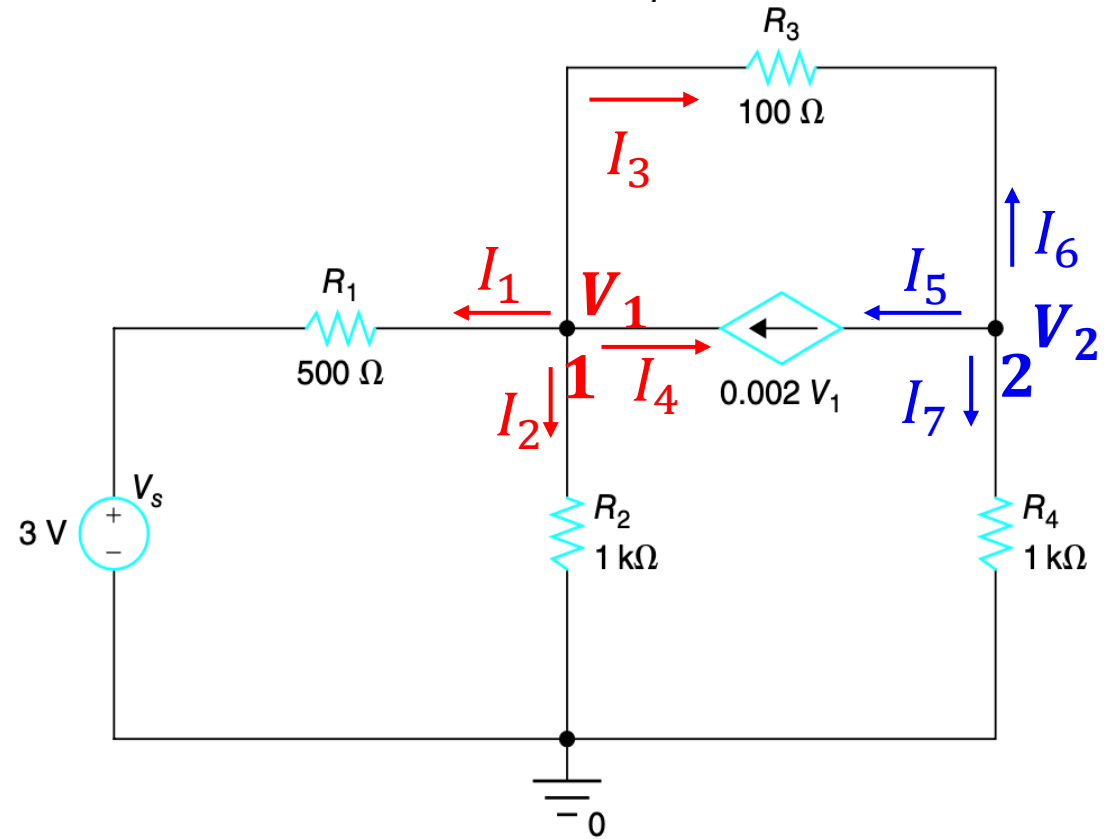
$$V_1 = 1.6098 \text{ V} \quad V_2 = 1.1707 \text{ V}$$


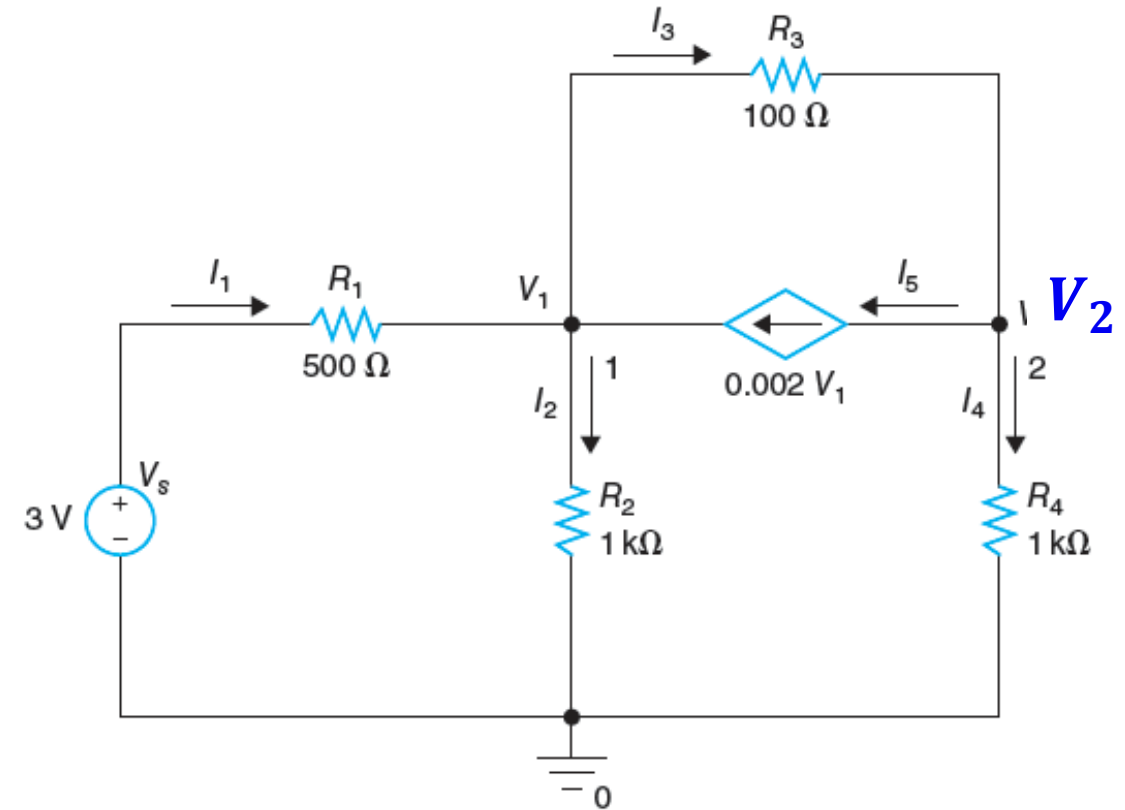
## EXAMPLE 3.4 (Cont..)


□ Currents:

- $I_1 = (V_s - V_1)/R_1 = 2.7805 \text{ mA}$
- $I_2 = V_1/R_2 = 1.6098 \text{ mA}$
- $I_3 = (V_1 - V_2)/R_3 = 4.3902 \text{ mA}$
- $I_4 = V_2/R_4 = 1.1707 \text{ mA}$
- $I_5 = 0.002V_1 = 3.2195 \text{ mA}$



## EXAMPLE 3.5

□ Find  $V_1$  and  $V_2$

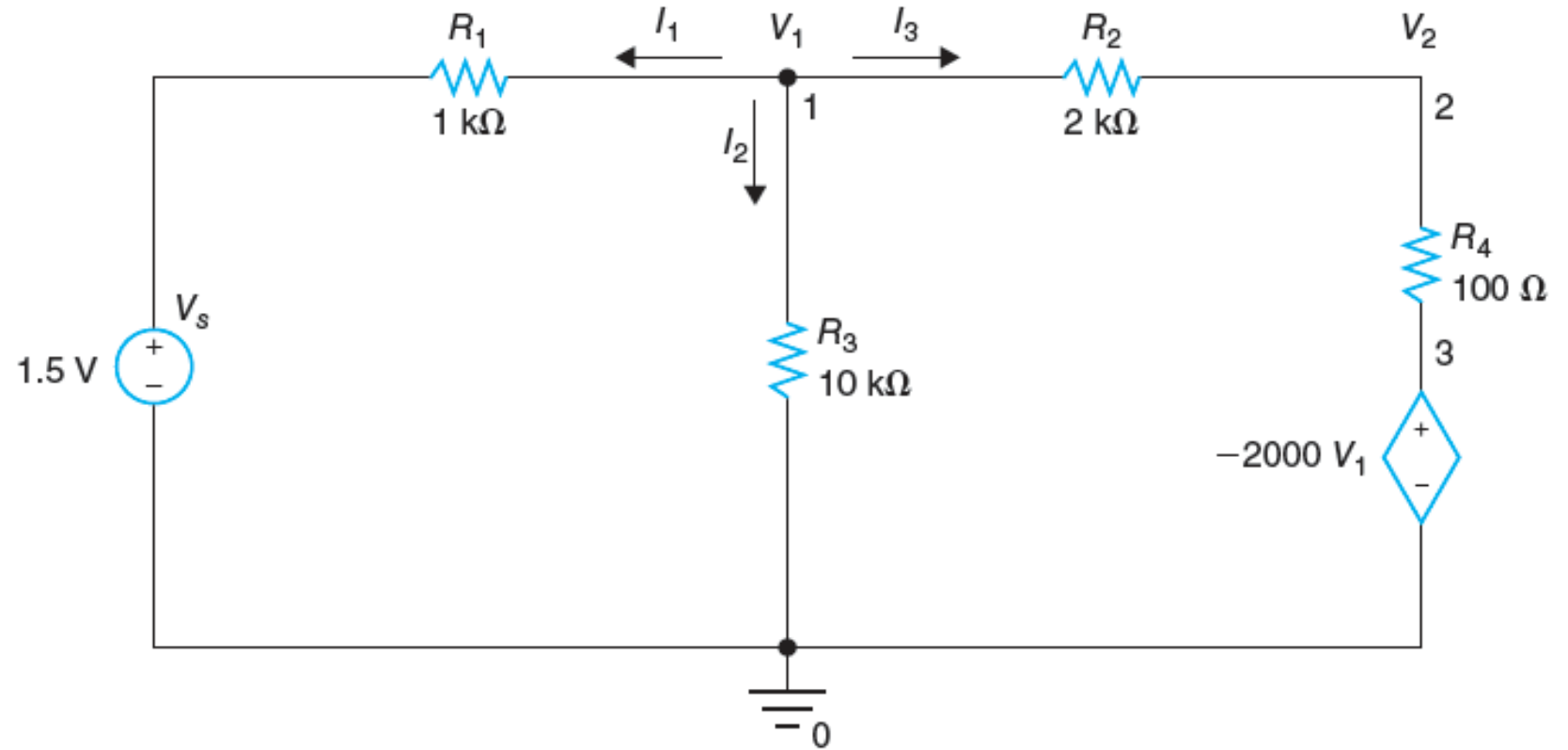

## EXAMPLE 3.5 (Cont..)

### □ KCL at Node 1

- Sum the currents leaving **node 1**:

$$I_1 + I_2 + I_3 = 0$$

$$I_1 = \frac{V_1 - V_s}{R_1}, \quad I_2 = \frac{V_1 - 0}{R_3}, \quad I_3 = \frac{V_1 - (-2000V_1)}{R_2 + R_4}$$


$$\frac{V_1 - 1.5}{1000} + \frac{V_1}{10000} + \frac{V_1 - (-2000V_1)}{2100} = 0$$

- Multiply by 21000  $\Rightarrow 21V_1 - 31.5 + 2.1V_1 + 10V_1 + 20000V_1 = 0 \Rightarrow 20033.1V_1 = 31.5 \Rightarrow V_1 = 1.5724 \text{ mV}$

- And  $V_2$  can be found out if we know  $I_3$

$$I_3 = \frac{V_1 - (-2000V_1)}{2100} = 1.4982 \text{ mA}$$
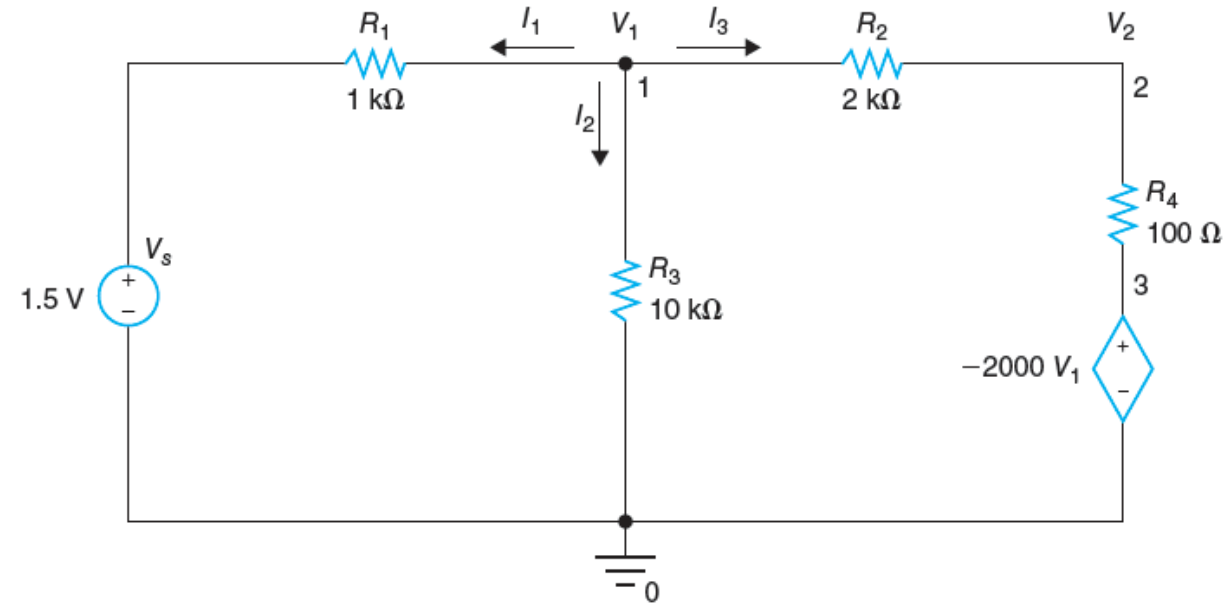
$$V_2 = V_1 - R_2 I_3 = -2.9949 \text{ V}$$



**Home Work: P3.1 to P3.32**

# Supernode


❑ **Super Node is a Special Situation in Nodal Analysis**, where a voltage source is between two Nodes with unknown voltages

- Lets say we have the circuit on right
- KCL at **Node 1**: Sum current leaving **Node1** = 0

$$-3A + I_1 + I_2 = 0$$

- By Ohm's Law find  $I_1$  and  $I_2$
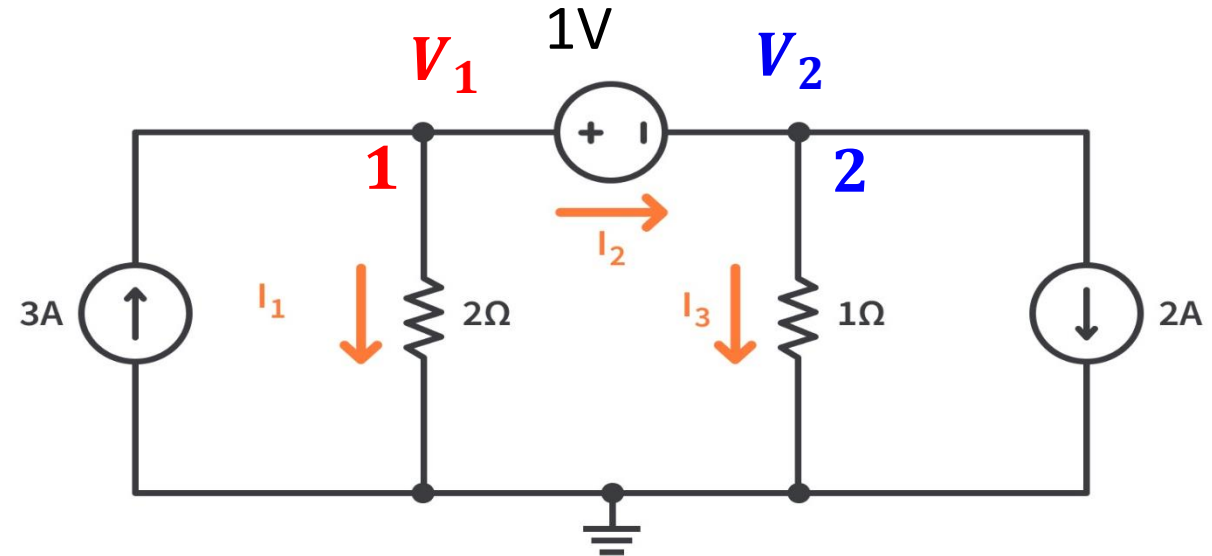
$$I_1 = \frac{V_1 - 0}{2} \quad I_2 = \frac{V_1 - V_2}{1} ???$$



- ❑ If there is a **voltage source in a circuit between two nodes** whose voltages are unknown, **we do not know the current through the voltage source**
- ❑ What is the current source resistance ? If it is ideal source than the current source resistance is zero.
- ❑ **Solution**

- **Node 1** and **Node 2** are combined to make one **Super Node**

## Supernode (Cont..)

- ❑ If there is a **voltage source in a circuit between two nodes** whose voltages are unknown, we **do not know the current through the voltage source**, and it is not possible to write the node equations for the two nodes that include the voltage source. In this case, **combine the two nodes to form a supernode**.
- ❑ We can then write the node equation for this supernode.
- ❑ One additional equation, commonly referred to as a **constraint equation** relating the two node voltages, can be obtained by representing the voltage source as a potential drop or as a potential rise between the two nodes.



## Supernode (Cont..)

❑ Combine the two nodes to get one **Super Node**

❑ We get two Equations for the super node

1. Constraint Equation from the source between Nodes

$$V_1 - V_2 = 1 \quad (1)$$

2. KCL for the **super node**  $\rightarrow -3A + I_1 + I_3 + 2A$

○ By Ohm's Law

$$-3 + \frac{V_1 - 0}{2} + \frac{V_2 - 0}{1} + 2 = 0$$

$$V_1 + 2V_2 = 2 \quad (2)$$


○ From (2)  $\rightarrow V_1 - V_2 = 1 \rightarrow V_1 = V_2 + 1$

○ Substitute ( $V_1 = V_2 + 1$ ) into (2)


$$V_2 + 1 + 2V_2 = 2 \Rightarrow 3V_2 = 1 \Rightarrow V_2 = \frac{1}{3}V$$

○ And  $V_1$  is
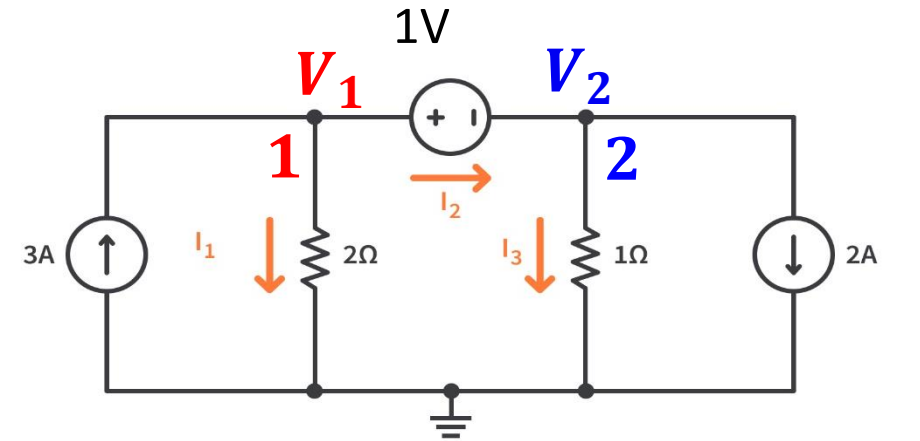
$$V_1 = \frac{1}{3} + 1 \Rightarrow V_1 = \frac{4}{3}V$$



**Assume no voltage source**

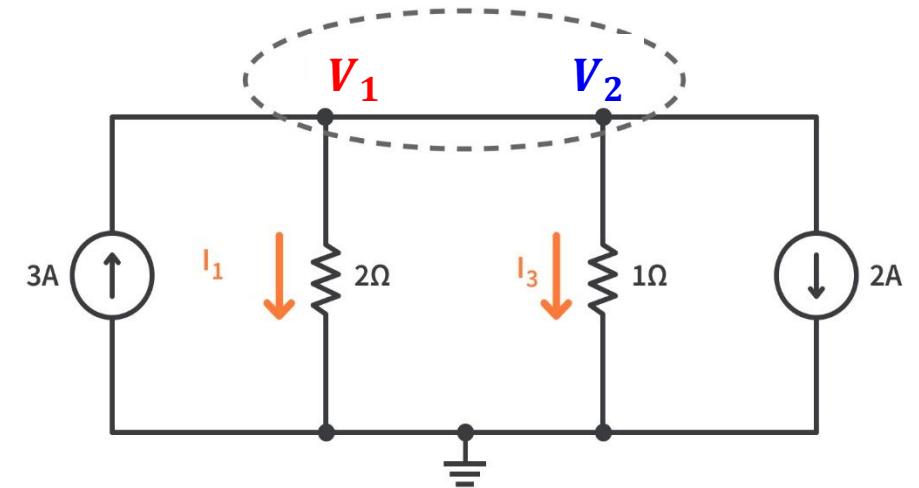


# Quiz

★ Multiple Choice

❑ Which node is super node?

Question: The super node is

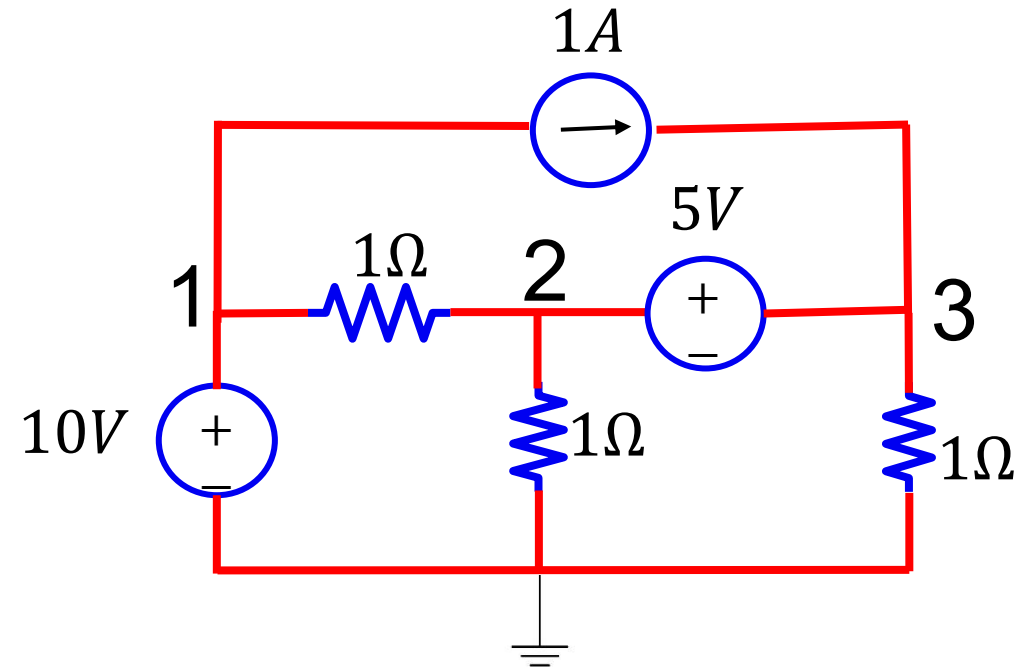- A. Node 1 and Node 2
- B. Node 2 and Node 3
- C. Node 1 and Node 0



## Supernode – Example

- The currents  $I_5, I_6$  flow in opposite direction.
- Unknown currents  $I_5, I_6$  through  $V_{s2}$  but  $I_6 = -I_5$ .

○ KCL at node 1  $\rightarrow I_1 + I_2 + I_5 = 0$  (1)

○ KCL at node 2  $\rightarrow I_3 + I_4 + I_6 = I_3 + I_4 - I_5 = 0$  (2)

- Add (1) and (2)

○  $I_1 + I_2 + I_5 = 0$  and  $I_3 + I_4 - I_5 = 0$ ,  $\rightarrow I_1 + I_2 + I_5 + I_3 + I_4 - I_5 = 0 \rightarrow I_1 + I_2 + I_3 + I_4 = 0$  (3)

- (3) is the sum of currents leaving nodes 1 and 2. As  $I_5 + I_6 = 0$ , therefore,  $I_5$  and  $I_6$  are not included in the sum.

○ Use Ohm's Law in (3)  $\frac{V_1 - 8}{2000} + \frac{V_1}{1000} + \frac{V_2 - 8}{1000} + \frac{V_2}{2000} = 0$

○ Multiply by 2000  $\rightarrow V_1 - 8 + 2V_1 + 2V_2 - 16 + V_2 = 0 \Rightarrow 3V_1 + 3V_2 = 24$  (4)

○ Since  $V_2$  is 4V higher than  $V_1$ , the constraint equation is given by  $V_2 = V_1 + 4$  (5)

○ Substitute (5) in (4)  $\rightarrow 3V_1 + 3V_1 + 12 = 24 \Rightarrow 6V_1 = 12 \Rightarrow V_1 = 2 \text{ V}$

○ Substitute (6) in (4)  $\rightarrow V_2 = 6 \text{ V}$

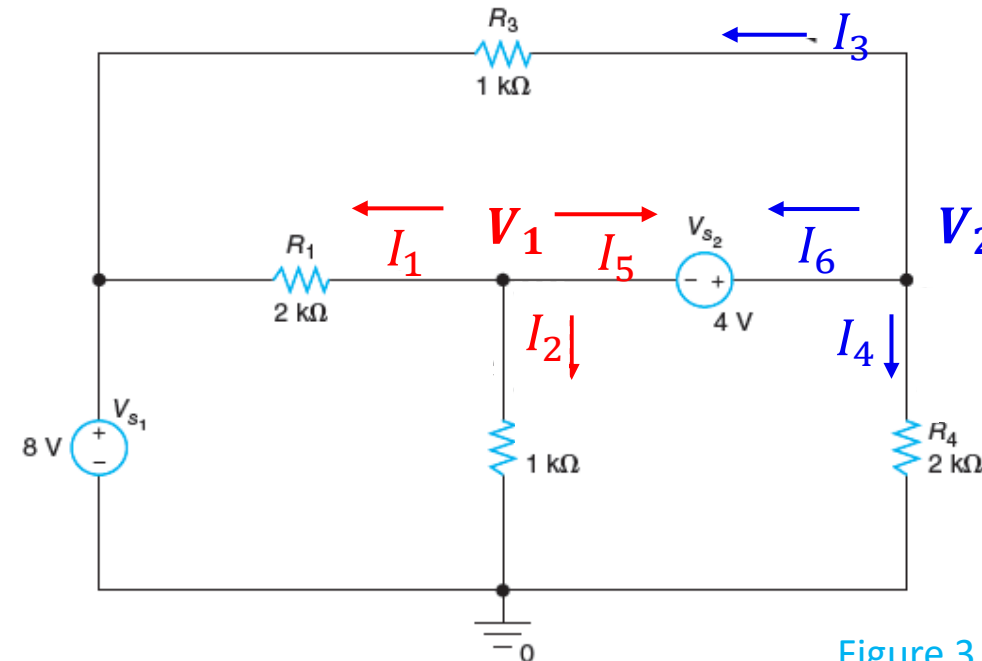


Figure 3.17

## EXAMPLE 3.8

□ Find  $V_1$ ,  $V_2$ ,  $V_3$ .

- Constraint equation:  $V_3 = V_2 + 7$  (1)
- Sum the currents leaving the **supernode** consisting of node 2 and node 3:

$$\frac{V_2 - V_1}{2000} + \frac{V_2}{4000} + \frac{V_3 - V_1}{2000} + \frac{V_3}{1000} = 0$$

- Multiply by 4000  $\rightarrow 2V_2 - 2V_1 + V_2 + 2V_3 - 2V_1 + 4V_3 = 0 \Rightarrow$   
 $-4V_1 + 3V_2 + 6V_3 = 0 \Rightarrow -4V_1 + 3V_2 + 6(V_2 + 7) = 0 \Rightarrow -4V_1 + 9V_2 = -42$  (2)

- Sum the currents leaving node 1:  $-0.009 + \frac{V_1 - V_2}{2000} + \frac{V_1 - V_3}{2000} = 0$

- Multiply by 2000  $\rightarrow 2V_1 - V_2 - V_3 = 18$  (3)

- Substitute (1) into (3)

$$2V_1 - V_2 - V_2 - 7 = 18$$


$$2V_1 - 2V_2 = 25$$
 (4)

- Multiply (4) by 2  $\rightarrow 4V_1 - 4V_2 = 50$  (5)

- Add (2) and (5)  $\rightarrow 5V_2 = 8 \Rightarrow V_2 = 1.6$  V,

- From (4)  $\rightarrow V_1 = V_2 + 12.5 = 14.1$  V

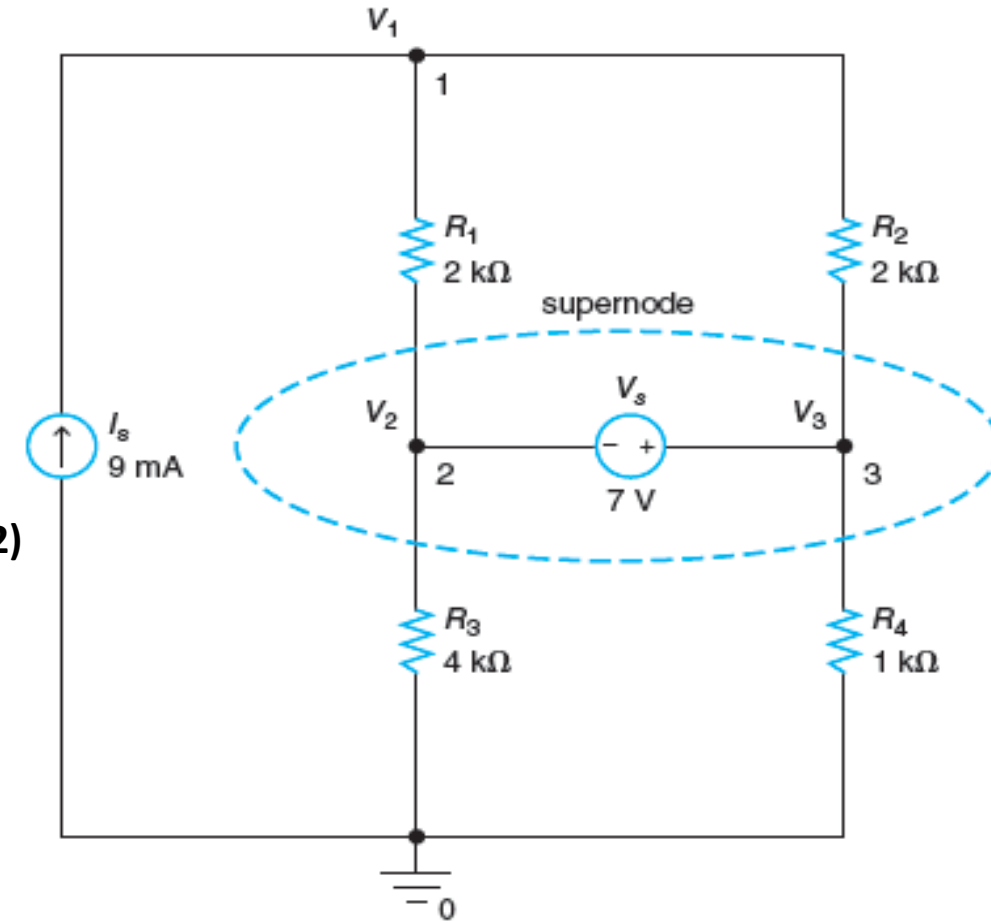
- From (1)  $\rightarrow V_3 = V_2 + 7 = 8.6$  V



**Home Work: P3.33 to P3.49**

## EXAMPLE 3.7

□ Find  $V_1$ ,  $V_2$ , and  $V_3$ .

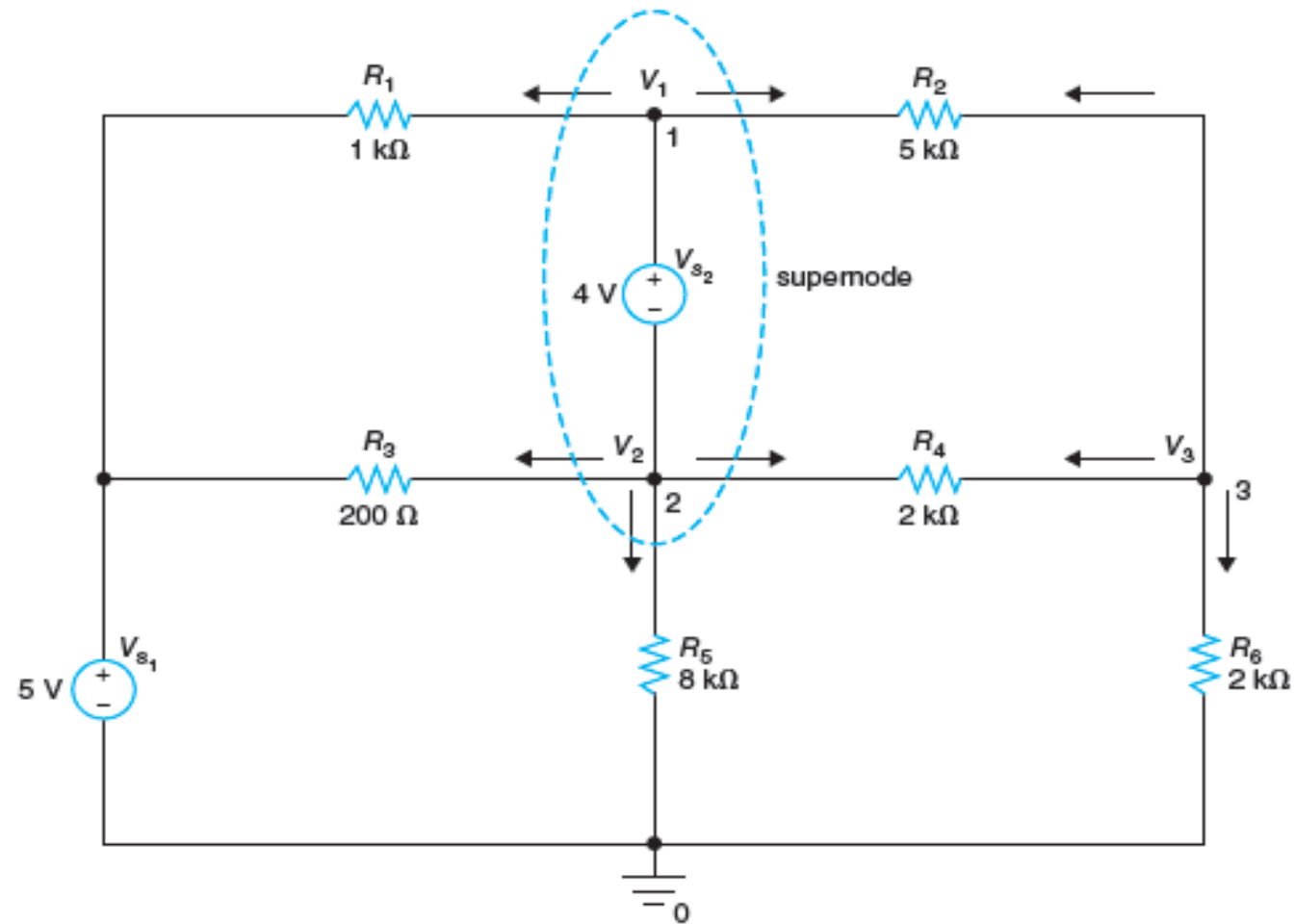

# EXAMPLE 3.7 (Cont..)

- Sum the currents leaving the **supernode** consisting of **node 1** and **node 2**:

$$\frac{V_1 - 5}{1000} + \frac{V_1 - V_3}{5000} + \frac{V_2 - 5}{200} + \frac{V_2 - V_3}{2000} + \frac{V_2}{8000} = 0$$

- Multiply by 8000  $\Rightarrow 8V_1 - 40 + 1.6V_1 - 1.6V_3 + 40V_2 - 200 + 4V_2 - 4V_3 + V_2 \Rightarrow 9.6V_1 + 45V_2 - 5.6V_3 = 240$  (1)

- Sum the currents leaving **node 3**:  $\frac{V_3 - V_1}{5000} + \frac{V_3 - V_2}{2000} + \frac{V_3}{2000} = 0$

- Multiply by 10k  $\Rightarrow 2(V_3 - V_1) + 5(V_3 - V_2) + 5V_3 = 0 \Rightarrow -2V_1 - 5V_2 + 12V_3 = 0$  (2)

- Constraint equation:  $V_1 = V_2 + 4$  (3)

- Substitute (3) in (1)  $\Rightarrow 54.6V_2 - 5.6V_3 = 201.6$

- Substitute (3) in (2)  $\Rightarrow -7V_2 + 12V_3 = 8$


- Solve (5) for  $V_2 \Rightarrow V_2 = (12/7)V_3 - 8/7$

- Substitute (6) in (4)  $\Rightarrow 54.6[(12/7)V_3 - 8/7] - 5.6V_3 = 201.6$

- Solve (7) for  $V_3 \Rightarrow V_3 = (201.6 + 54.6 \times 8/7) / (54.6 \times 12/7 - 5.6) = 3$

- Substitute (8) in (6)  $\Rightarrow V_2 = 4$  V

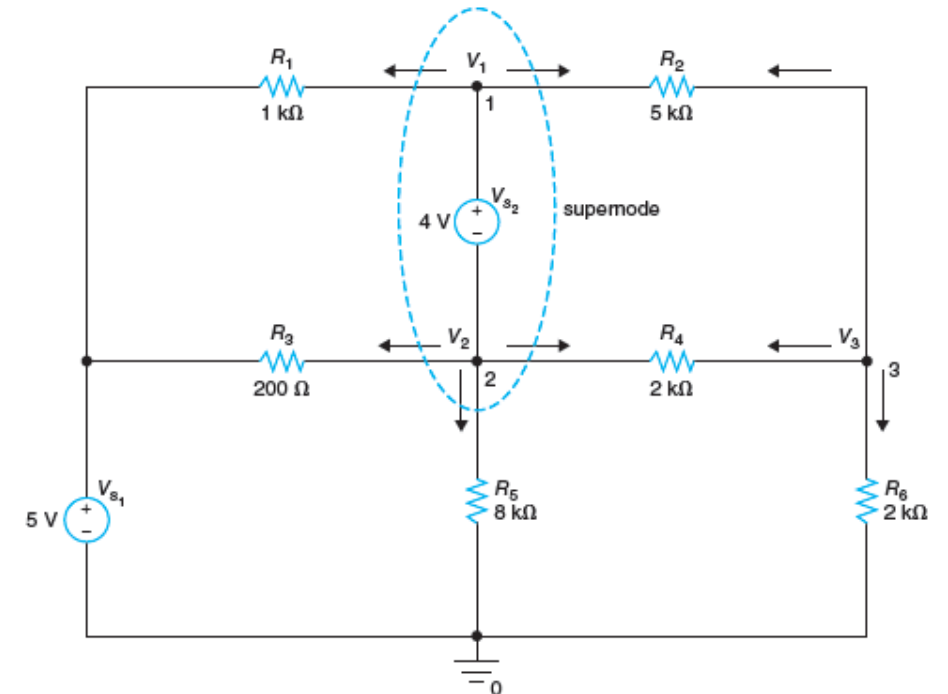- Substitute (9) in (3)  $\Rightarrow V_1 = 8$  V



# Summary

- ❑ Node Analysis
- ❑ Supernode
- ❑ What will we study in next lecture.