



电子科技大学
格拉斯哥学院
Glasgow College, UESTC



Circuit Analysis and Design

Academic Year 2025/2026 – Semester 1

Lecture 15 – Operational Amplifier Circuits


Masood Ur-Rehman, Muhammad Aslam, Ali Imran

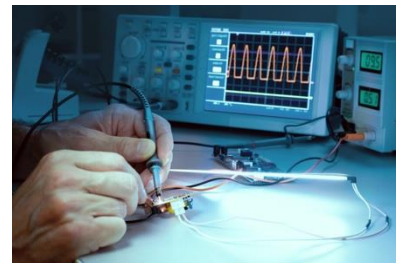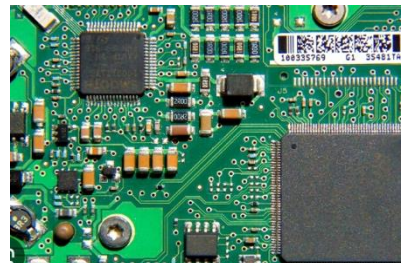{masood.urrehman, muhammad.aslam.2, ali.imran}@glasgow.ac.uk



Agenda

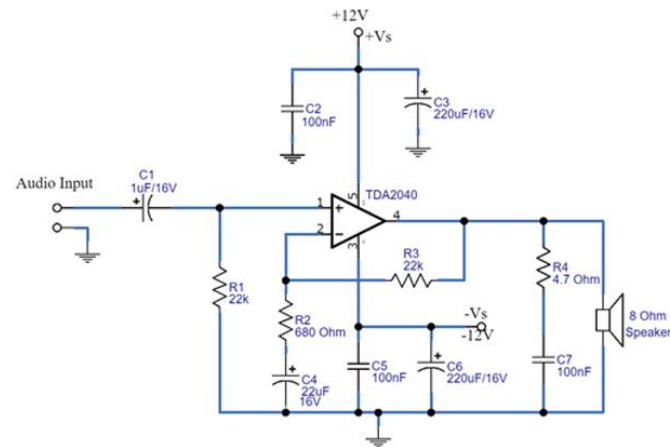- ❑ Ideal op amp
- ❑ Sum and difference
- ❑ Analysis of inverting configuration
- ❑ Analysis of non-inverting configuration



Introduction

- ❑ An operational amplifier (commonly called op amp or op amp) is a device that can be used to perform **mathematical operations** such as
 - **Addition, Subtraction, amplification, attenuation, integration, and differentiation.**
 - It is a versatile integrated circuit (IC) chip that is widely **used in amplifiers, filters, signal conditioning, and instrumentation circuits.**
- ❑ Circuit symbol for an op amp is shown in Figure 5.1 and Figure 5.2 shows pin configuration for a typical 8-pin package.

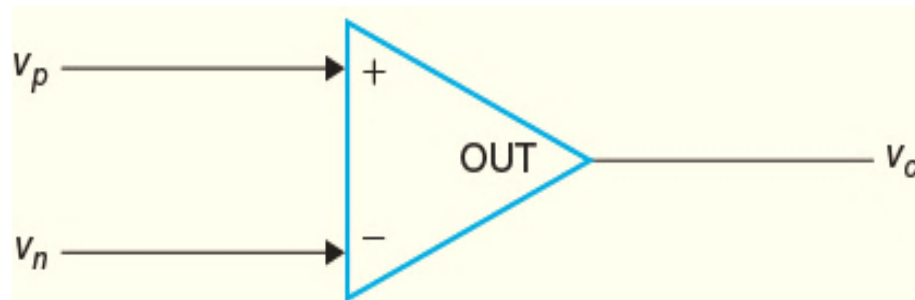


FIGURE 5.1

Circuit symbol for an op amp.

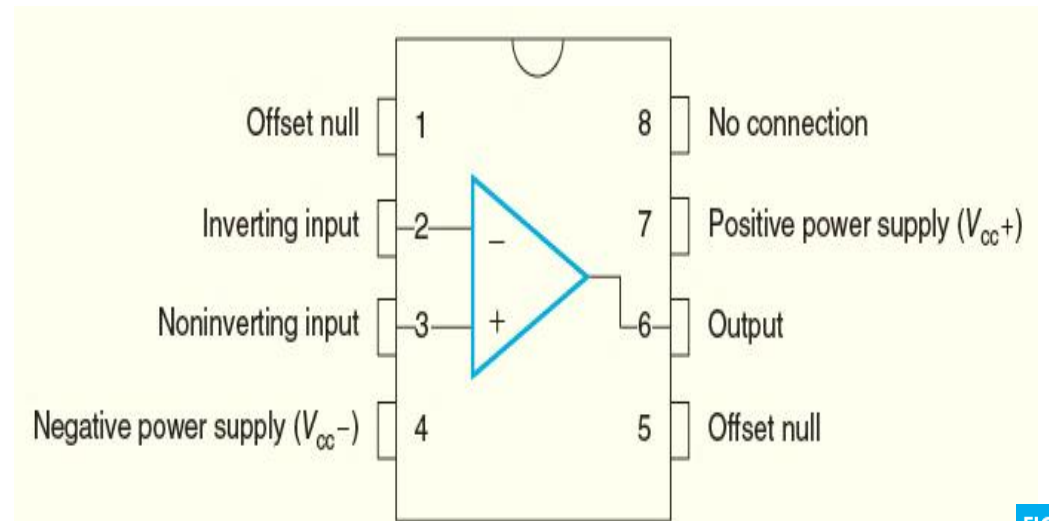



FIGURE 5.2

Configurations OP-AMP

□ There are two configurations to operate an OP-AMP


Inverting Configuration

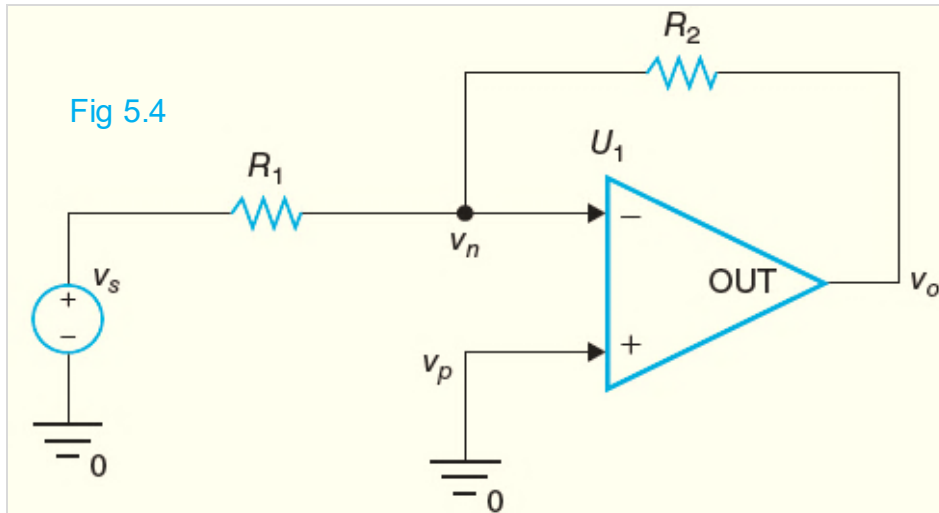- Figure 5.4 shows inverting configuration of an op amp.
- Input voltage v_s is applied to inverting input through a resistor R_1 .
- Resistor R_2 provides a feedback path between the output terminal and the inverting input terminal.
- **Output voltage v_o is inverted compared to input v_n**



Non-Inverting Configuration

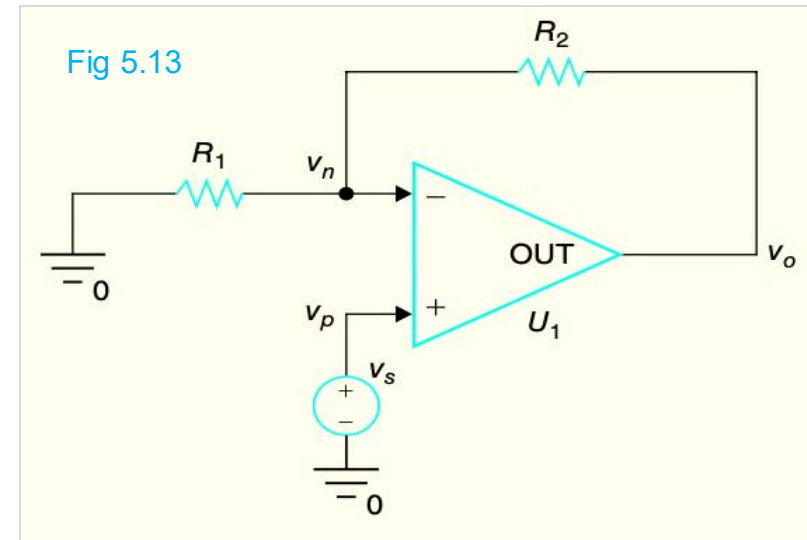- Figure 5.13 shows non-inverting configuration of an op amp.
- Input voltage v_s is applied to non-inverting input.
- Inverting terminal is connect to ground through a resistor R_1 .
- Resistor R_2 provides a feedback path between the output terminal and the inverting input terminal.
- **Output voltage v_o is in phase with input voltage v_p**



Op Amp Equivalent Circuit (VCVS Model)

- Op amps can be modeled as a voltage-controlled voltage source (VCVS), as shown in Figure 5.3. In the model,

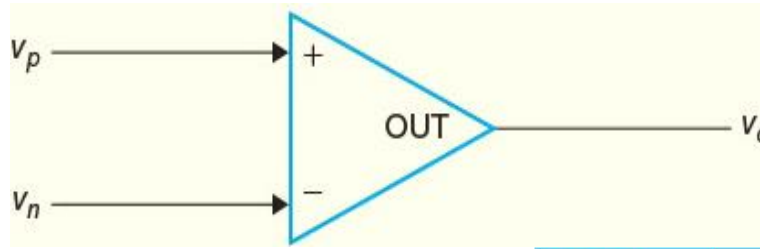


FIGURE 5.1
Circuit symbol for an op amp.


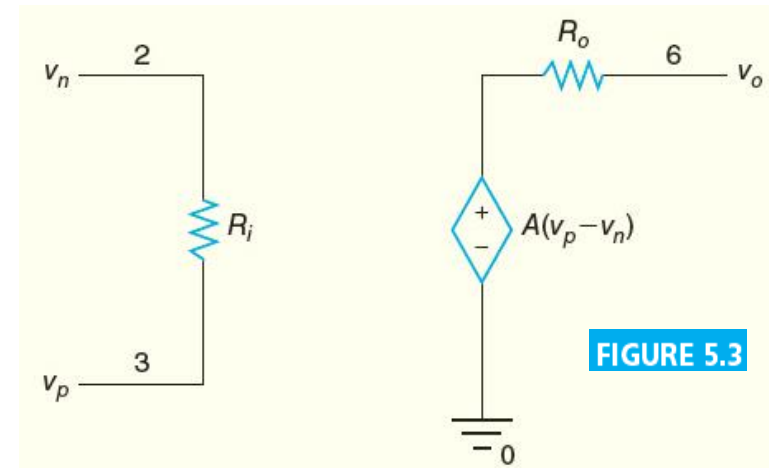


FIGURE 5.3

- v_n : is the voltage on the Inverting input (pin 2),
 - v_p : is the voltage on the Noninverting input (pin 3),
 - v_o : is the voltage on the Output (pin 6),
 - R_i : is the Input Resistance,
 - R_o : is the Output Resistance,
 - A : is the unloaded voltage Gain.
- In general, the input resistance R_i is large, the output resistance R_o is small, and the gain A is large.

Ideal OP-AMP

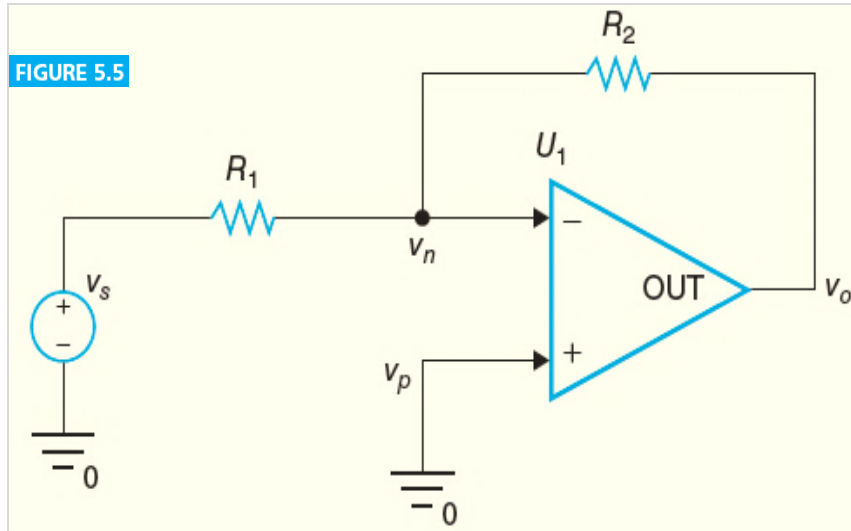- Let's consider the inverting configuration. When the op amp is replaced by the model (VCVS) shown in Figure 5.3, we obtain the circuit shown in Figure 5.5.





- An Ideal OP-AMP Assumes

- $R_i = \infty$, $R_o = 0$, A is large in Fig. 5.5 we can get Fig 5.6, then we can prove that

$$v_d = v_p - v_n = 0 \text{ OR } v_p = v_n \text{ and } i_{R_i} = 0$$

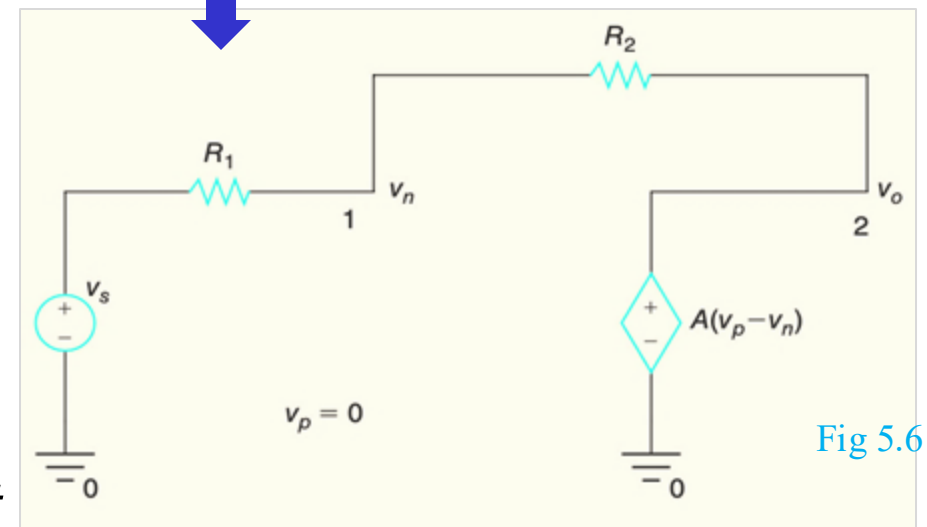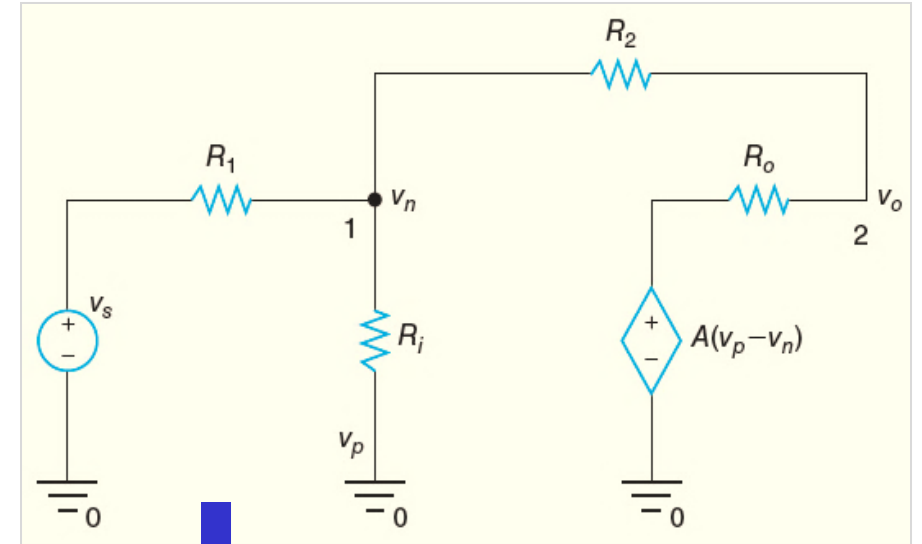v_p and v_n are virtually same OR $i_R = 0$ i.e. virtually short



Ideal OP-AMP (Cont..)

□ For an Idea OP-AMP after assuming $R_i = \infty$, $R_o = 0$, in a circuit we can prove the following

1. Current flowing into op-amp from positive terminal is zero ($i_p = 0$)
2. Current flowing into op-amp from negative terminal is zero ($i_n = 0$)
3. Voltage difference v_d between v_p and v_n is 0, that means $v_p = v_n$

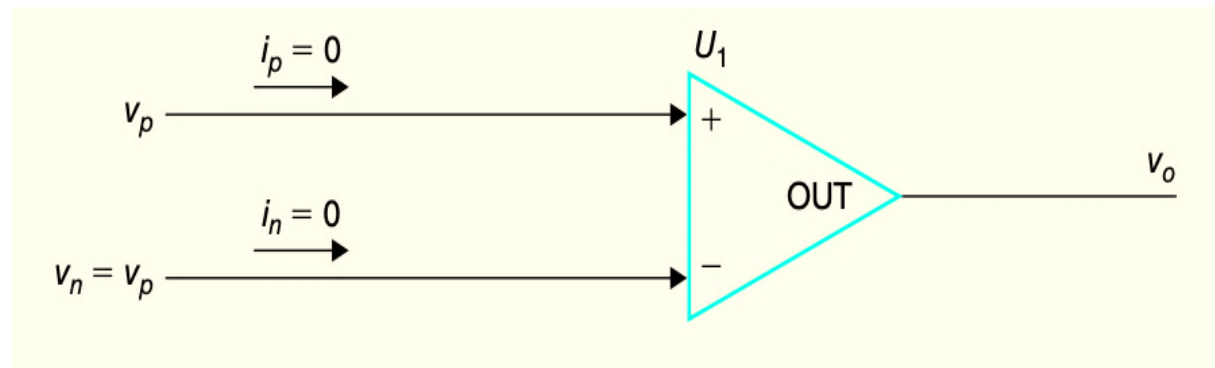


FIGURE 5.10

An op amp showing zero input currents and a virtual short.

- These assumptions make analysis very simple, and the results of practical and ideal op-amp are not that much difference
- In the analysis, generally, we try to compute output voltage v_o .

Quiz

Will be shown and solved in the Class

Summing Amplifier (Inverting Config.)

□ An inverting amplifier with two inputs is shown in Figure 5.30.

□ **KCL: Sum the currents leaving at node 1 = 0** : Note for ideal OP-AMP voltage at Node 1 is $v_n = v_p = 0$ or ($V = U_1 = 0$)

$$\frac{0 - v_1}{R_1} + \frac{0 - v_2}{R_2} + \frac{0 - v_o}{R_f} = 0$$


□ Solve for V_o :

$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 \right)$$

□ If $R_1 = R_f, R_2 = R_f, V_o = -(V_1 + V_2)$

□ If $R_1 = R_f/k_1, R_2 = R_f/k_2$, we obtain
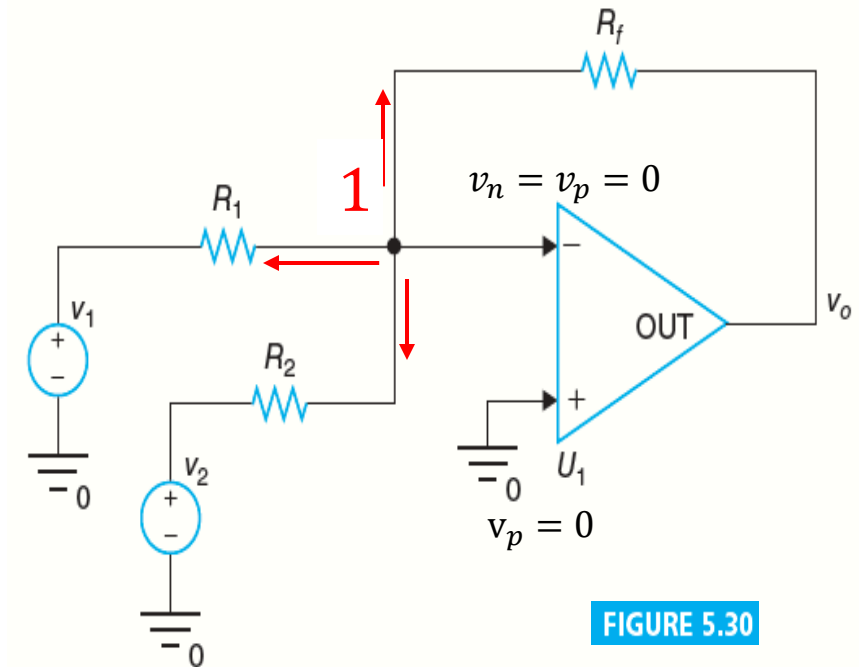
$$v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 \right) = -(k_1 v_1 + k_2 v_2)$$



Summing Amplifier (Inverting Config.)

- ❑ To get positive sum instead of negative, connect another OP-AMP as shown in Figure 5.31
- ❑ Let v_a be voltage at the output of first op amp. KCL at **Node 2** : Sum of currents leaving = 0

$$\frac{0 - v_a}{R_3} + \frac{0 - v_0}{R_4} = 0 \Rightarrow v_a = -\frac{R_3}{R_4} v_0 \quad (1)$$

- ❑ Sum currents leaving **Node 1** = 0:


$$\frac{0 - v_1}{R_1} + \frac{0 - v_2}{R_2} + \frac{0 - v_a}{R_f} = 0$$

$$v_a = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2\right) \quad (2)$$

- ❑ Substituting v_a from 1 in 2, and solve for v_o is

$$v_o = \frac{R_4}{R_3} \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 \right)$$
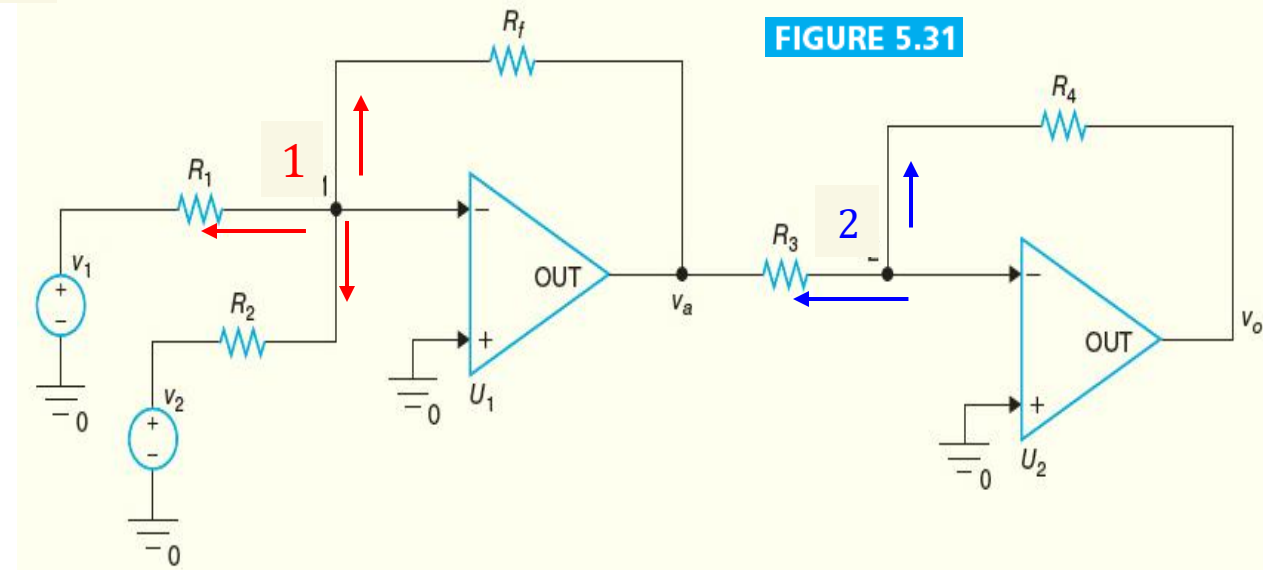
$$\text{If } R_3 = R_4, R_f = R_1 = R_2 = R \Rightarrow v_o = v_1 + v_2$$



Summing Amplifier (Inverting Config.)

□ An inverting amplifier with N inputs is shown in Figure 5.32.

□ Sum the currents leaving **node 1**: $\frac{0-v_1}{R_1} + \frac{0-v_2}{R_2} + \dots + \frac{0-v_N}{R_N} + \frac{0-v_o}{R_f} = 0$

□ Solve for **V_o**:
$$v_o = -\left(\frac{R_f}{R_1}v_1 + \frac{R_f}{R_2}v_2 + \dots + \frac{R_f}{R_N}v_N\right)$$

□ If $R_1 = R_2 = \dots = R_N = R_f$,

$$v_o = -(v_1 + v_2 + \dots + v_N)$$

□ If $R_1 = R_f/k_1$, $R_2 = R_f/k_2$, ..., $R_N = R_f/k_N$, we obtain

$$v_o = -(k_1v_1 + k_2v_2 + \dots + k_Nv_N)$$

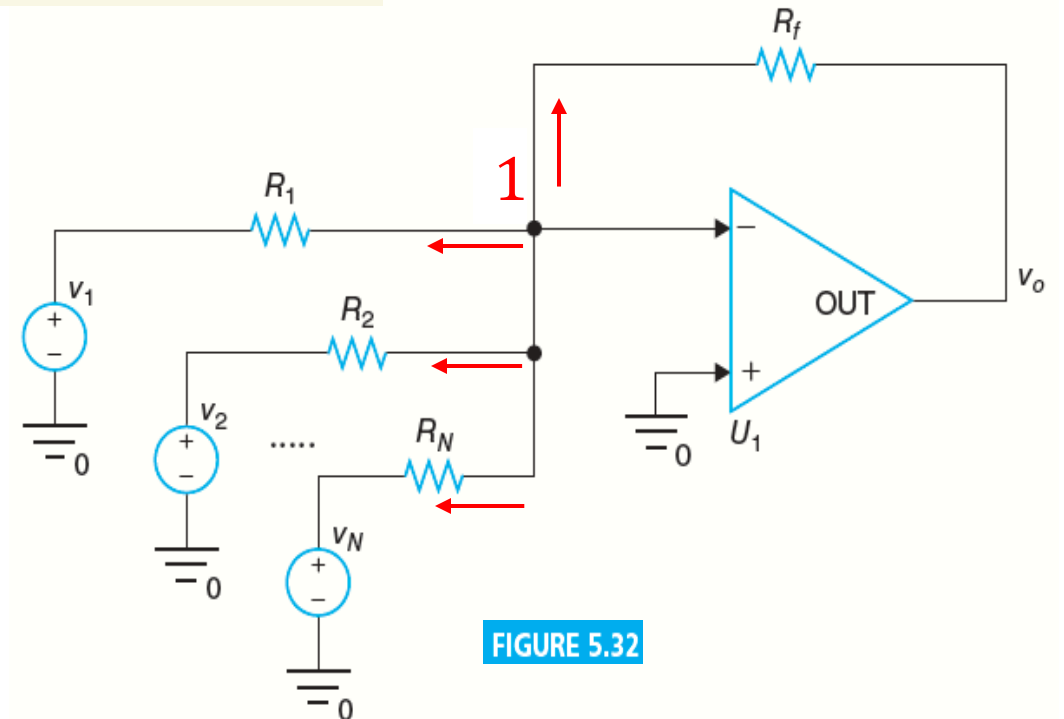


FIGURE 5.32

Summing Amplifier (Noninverting Configuration)

□ A non-inverting amplifier with two inputs is shown in Figure 5.33.

□ Voltage divider rule on **R_5 - R_4** :

$$v_n = \frac{R_4}{R_4 + R_5} v_o \Rightarrow v_o = \frac{R_4 + R_5}{R_4} v_n$$


□ Sum the currents leaving **node 1**: (note $v_p = v_n$)

$$\frac{v_p - v_1}{R_1} + \frac{v_p - v_2}{R_2} + \frac{v_p}{R_3} = 0 \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v_p = \frac{v_1}{R_1} + \frac{v_2}{R_2},$$

$$v_o = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \frac{R_4 + R_5}{R_4} \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} \right) \quad (1)$$

□ If **$R_1 = R_2 = R_3 = R_4 = R$** and **$R_5 = 2R$** ,
then, **V_o** becomes **$V_o = V_1 + V_2$**

□ If **$R_3 = R_4 = R$** , **$R_1 = R/k_1$** , **$R_2 = R/k_2$** , and **$R_5 = R(k_1 + k_2)$** ,
 v_o becomes **$v_o = k_1 v_1 + k_2 v_2$** (2)

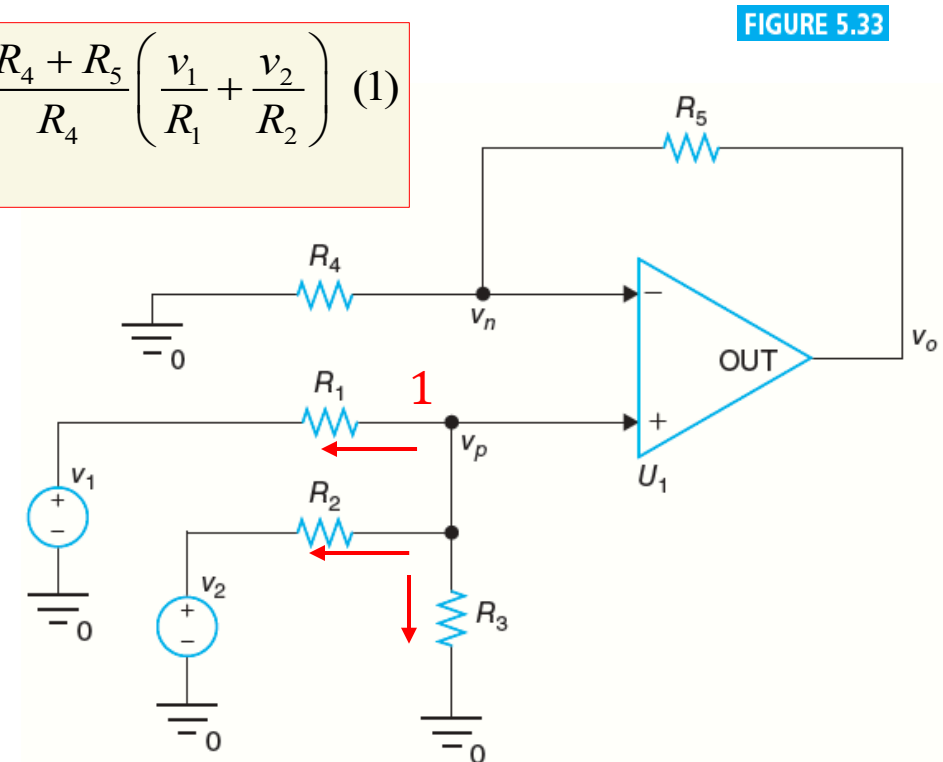


EXAMPLE 5.7

□ Design an op amp circuit for $V_o = 0.5V_1 + 3V_2$.

- $k_1 = 0.5$, $k_2 = 3$
- Let $R = 3 \text{ k}\Omega$. Then,
- $R_3 = R_4 = R = 3 \text{ k}\Omega$
- $R_1 = R/k_1 = 6 \text{ k}\Omega$
- $R_2 = R/k_2 = 1 \text{ k}\Omega$
- $R_5 = R(k_1 + k_2) = 10.5 \text{ k}\Omega$
- The circuit is shown in Figure 5.34.

If $R_3 = R_4 = R$, $R_1 = R/k_1$, $R_2 = R/k_2$, and
 $R_5 = R(k_1 + k_2)$,
 $v_o = k_1 v_1 + k_2 v_2$

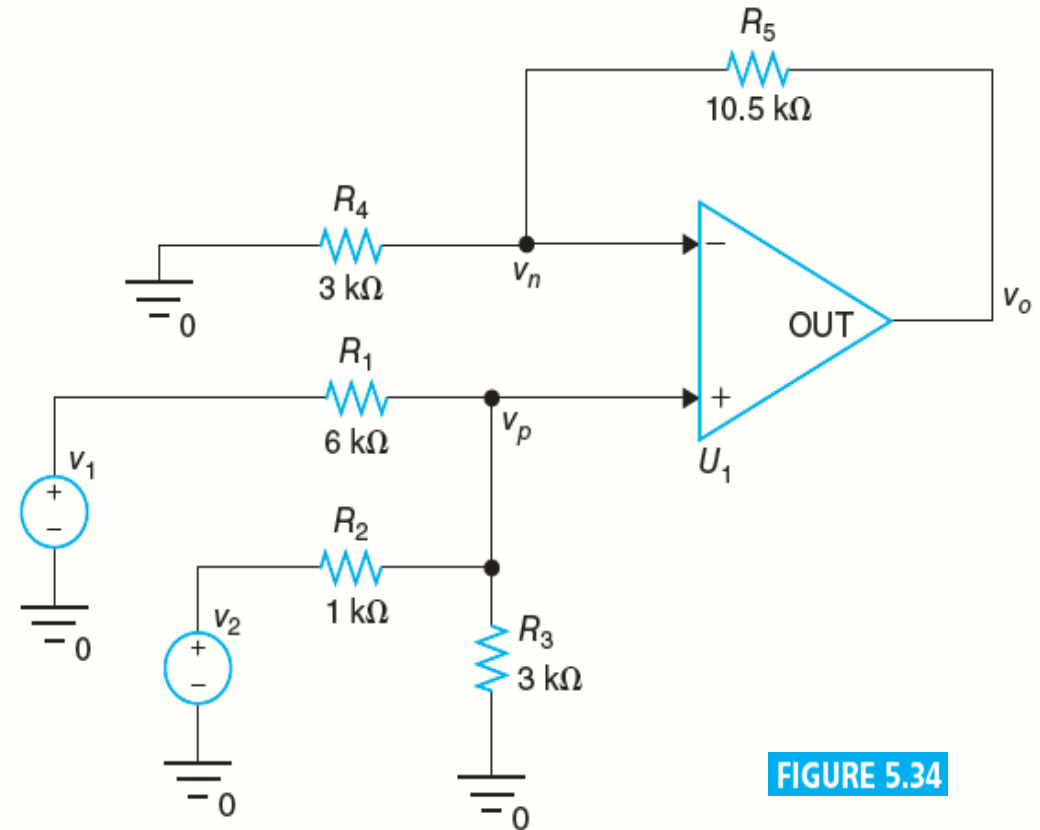Summing Amplifier (Noninverting Configuration)



Quiz

Will be shown and solved in the Class

EXAMPLE 5.8

- Design a circuit for **converting a polar binary signal V_1** (1 is represented by a pulse with 5 V, and 0 is represented by a pulse with -5 V) **to a unipolar binary signal v_o** (1 is represented by a pulse with 5 V, and 0 is represented by a pulse with 0 V).

- If $R_1 = R_2 = R_3 = R_5 = R$ and $R_4 = 2R$, v_o becomes

$$v_o = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \frac{R_4 + R_5}{R_4} \left(\frac{v_1}{R_1} + \frac{v_2}{R_2} \right) = \frac{1}{2} (v_1 + v_2)$$

- The circuit is shown in Figure 5.36 ($v_2 = 5$ V).

- Alternate choice:

$$k_1 = k_2 = 0.5$$

$$R = 10 \text{ k}\Omega, R_3 = R_4 = R = 10 \text{ k}\Omega, R_1 = R/k_1 = 20 \text{ k}\Omega,$$

$$R_2 = R/k_2 = 20 \text{ k}\Omega, R_5 = R(k_1 + k_2) = 10 \text{ k}\Omega$$

- Figure 5.37 shows sample waveforms.

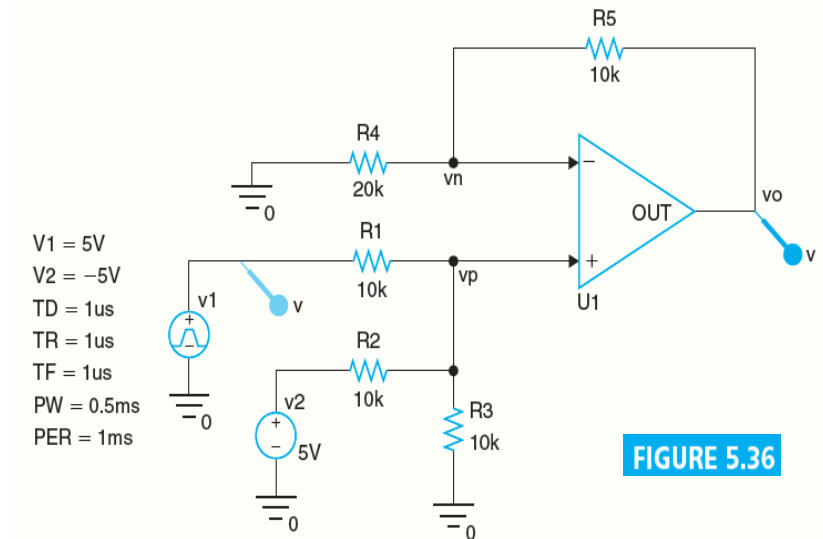


FIGURE 5.36

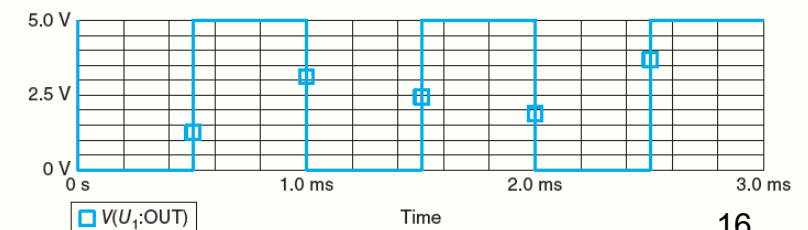
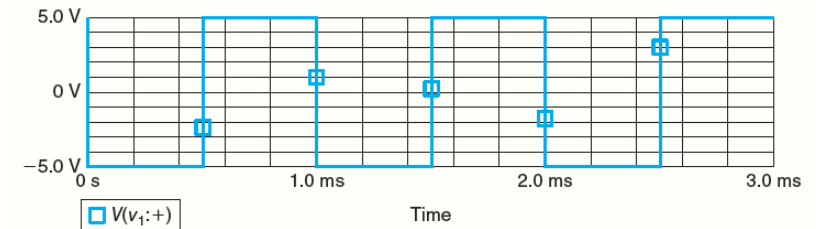


FIGURE 5.37

Summing Amplifier (Noninverting Configuration, N Inputs)

□ A non-inverting summing amplifier with N inputs is shown in Figure 5.38.

□ Voltage divider rule on $R_{N+3} - R_{N+2}$:

$$v_n = \frac{R_{N+2}}{R_{N+2} + R_{N+3}} v_o \Rightarrow v_o = \frac{R_{N+2} + R_{N+3}}{R_{N+2}} v_n$$

□ Sum the currents leaving **node 1**: Note $V_n = V_p$

$$\frac{v_p - v_1}{R_1} + \dots + \frac{v_p - v_N}{R_N} + \frac{v_p}{R_{N+1}} = 0 \Rightarrow \left(\frac{1}{R_1} + \dots + \frac{1}{R_N} \right) v_p = \frac{v_1}{R_1} + \dots + \frac{v_N}{R_N}$$

$$v_o = \frac{1}{\frac{1}{R_1} + \dots + \frac{1}{R_N}} \frac{R_{N+2} + R_{N+3}}{R_{N+2}} \left(\frac{v_1}{R_1} + \dots + \frac{v_N}{R_N} \right) \quad (1)$$

□ If $R_1 = R_2 = \dots = R_{N+2} = R$ and $R_{N+3} = NR$, v_o becomes

$$v_o = v_1 + v_2 + \dots + v_N$$

□ If $R_{N+1} = R_{N+2} = R$, $R_1 = R/k_1, \dots, R_N = R/k_N$, and

$$R_{N+3} = R(k_1 + k_2 + \dots + k_N), \quad v_o = k_1 v_1 + k_2 v_2 + \dots + k_N v_N \quad (2)$$

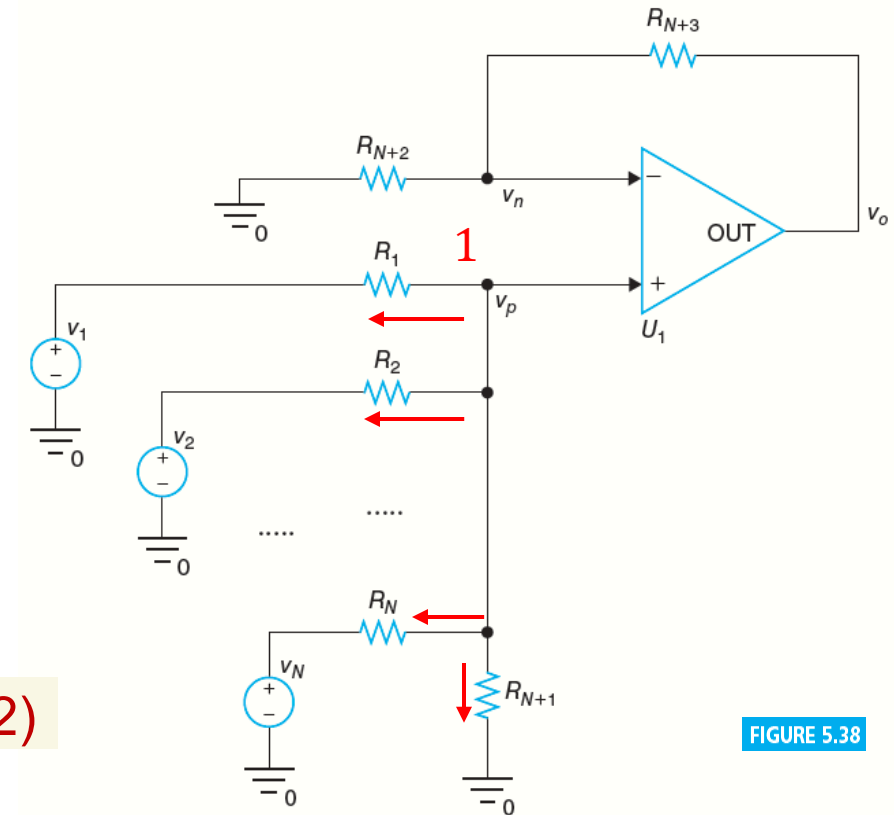


FIGURE 5.38

Difference Amplifier

- ❑ A difference amplifier is shown in Figure 5.41.

- ❑ Voltage divider rule on R_3 - R_4 :
$$v_p = \frac{R_4}{R_3 + R_4} v_2 \quad (1)$$

- ❑ Sum the currents leaving **node 1**:

$$\frac{v_n - v_1}{R_1} + \frac{v_n - v_o}{R_2} = 0 \Rightarrow v_o = \frac{R_1 + R_2}{R_1} v_n - \frac{R_2}{R_1} v_1 \quad (2)$$

- ❑ Substitute Equation (1) into Equation (2):

$$v_o = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) v_2 - \frac{R_2}{R_1} v_1 \quad (3)$$


- ❑ If $R = R_1 = R_2 = R_3 = R_4$, Equation (3) becomes

$$v_o = v_2 - v_1$$

v_o is the difference of v_2 and v_1 .

FIGURE 5.41

Difference amplifier.

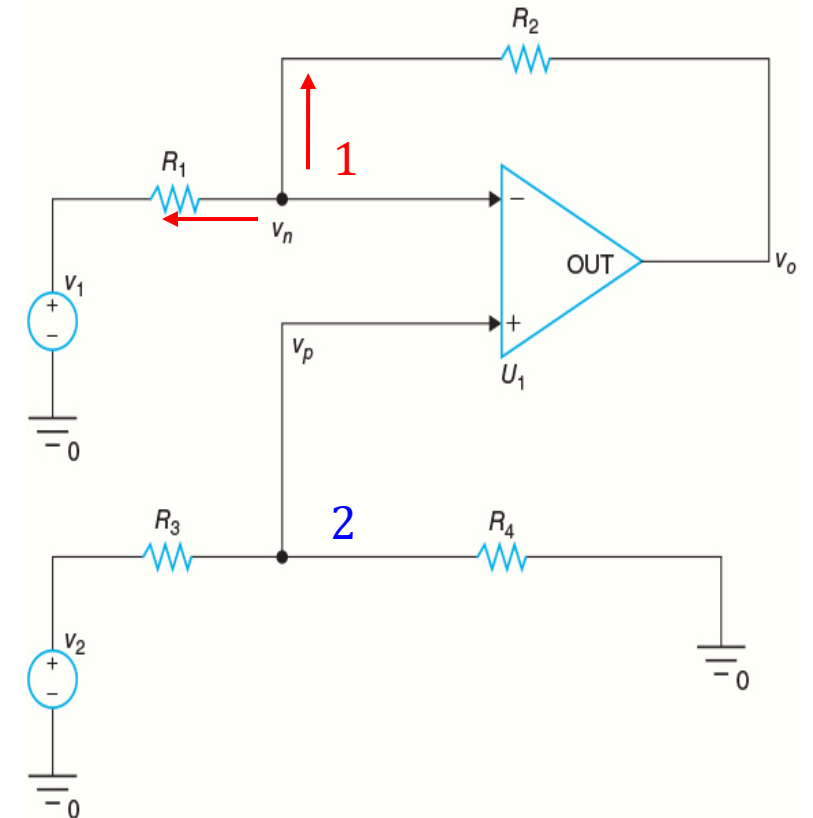

EXAMPLE 5.9

- Design a circuit for converting a **unipolar binary signal** v_2 (1 is represented by a pulse with 5 V, and 0 is represented by a pulse with 0 V) to a **polar binary signal** v_o (1 is represented by a pulse with 5 V, and 0 is represented by a pulse with -5 V).

$$V_o = 2(v_2 - 2.5)$$

- If $R_3 = R_1$, $R_4 = R_2$, $R_2 = 2R_1$, $v_1 = 2.5$ V, we get

$$v_o = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) v_2 - \frac{R_2}{R_1} v_1 = 2(v_2 - 2.5)$$

- We choose $R_1 = R_3 = 10 \text{ k}\Omega$, $R_2 = R_4 = 20 \text{ k}\Omega$ in the circuit shown in Figure 5.42.

- Figure 5.43 shows sample waveforms.

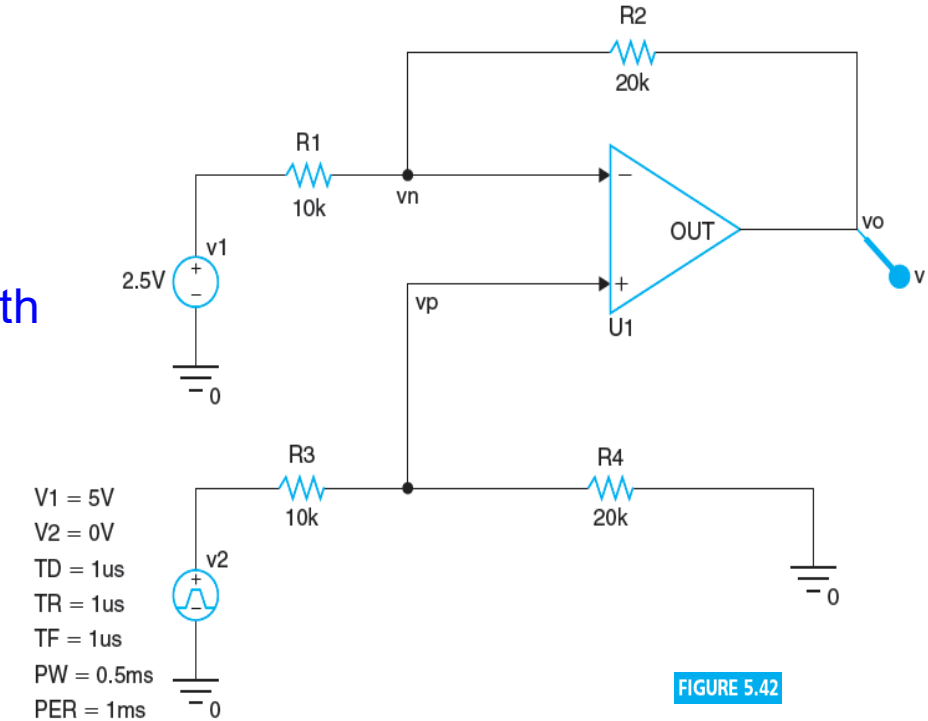


FIGURE 5.42

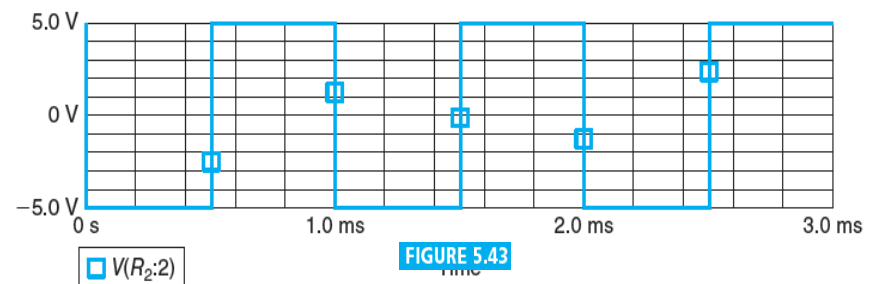
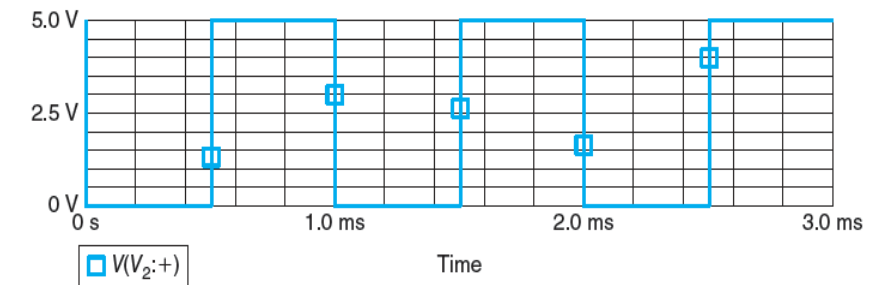


FIGURE 5.43

Op Amp Circuit to Implement $v_o = 7v_1 - 2v_2$

- We can use the superposition principle to show that the circuit shown in Figure 5.44 provides an output voltage given by $v_o = 7v_1 - 2v_2$.

- Deactivate v_2 by short-circuiting it. $v_a = 0$. U_2 is configured as a noninverting amplifier. Thus,

$$v_o = (1 + R_4/R_3)v_1 = (1 + 6)v_1 = 7v_1$$

- Deactivate v_1 by short-circuiting it. From the voltage divider rule, the voltage at node 1 is given by $v_2/3$. Thus, $v_a = v_2/3$. U_2 is configured as an inverting amplifier. Thus,

$$v_o = (-R_4/R_3)v_a = (-6)v_2/3 = -2v_2$$

- Adding the two outputs, we obtain

$$v_o = 7v_1 - 2v_2$$

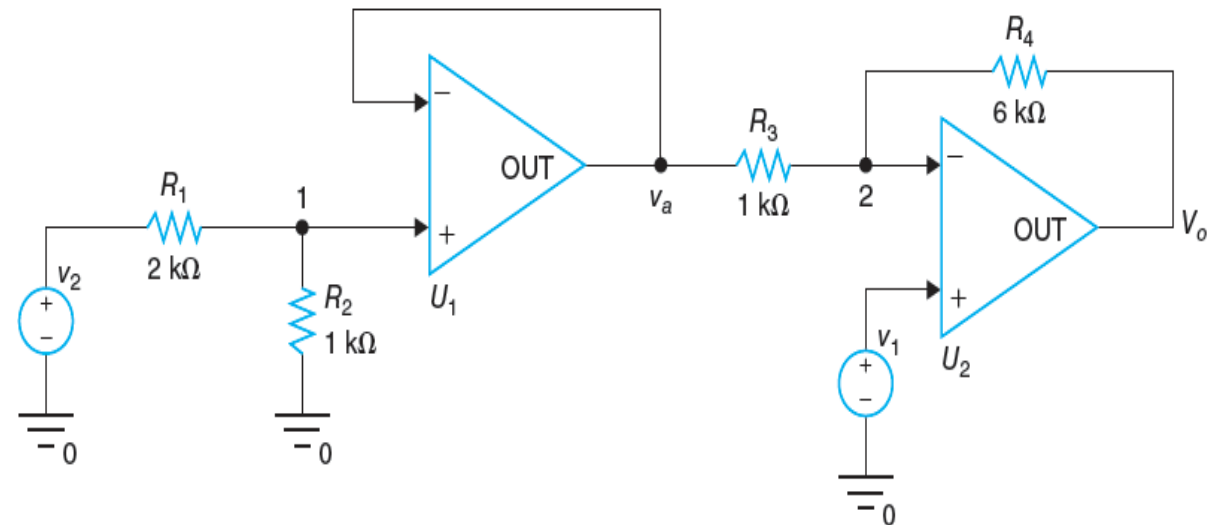


FIGURE 5.44

Analysis of OP-AMP

- ❑ Before in these sections, We assumed that $R_i = \infty$ and $R_o = 0$.
- ❑ In the coming sections, we will analyze circuits, including R_i and R_o and see how these considerations impact, differently from our assumptions
- ❑ We will analyze both configurations of OP-AMP, i.e.
 - Analysis of Inverting OP-AMP and
 - Analysis of Non-inverting OP-AMP

Analysis of Inverting Configuration

- A model for an inverting configuration is shown in Figure 5.52. Notice that $V_p = 0$.
- KCL: Summing the currents leaving **node 2 = 0**, we obtain

$$\frac{v_o - v_n}{R_2} + \frac{v_o + Av_n}{R_o} = 0 \Rightarrow v_n = \frac{R_o + R_2}{R_o - R_2 A} v_o, \quad v_o = \frac{R_o - R_2 A}{R_o + R_2} v_n \quad (1)$$

- KCL: Summing the currents leaving **node 1 = 0**, we obtain

$$\frac{v_n - v_s}{R_1} + \frac{v_n}{R_i} + \frac{v_n - v_o}{R_2} = 0 \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_i} + \frac{1}{R_2} \right) v_n - \frac{v_o}{R_2} = \frac{v_s}{R_1} \quad (2)$$

- Solving Equations (1) and (2) for V_n and V_o , we get

$$v_n = \frac{R_i(R_o + R_2)v_s}{R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + A R_1 R_i} \quad (3)$$

$$v_o = \frac{-R_i(-R_o + R_2 A)v_s}{R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + A R_1 R_i} \quad (4)$$

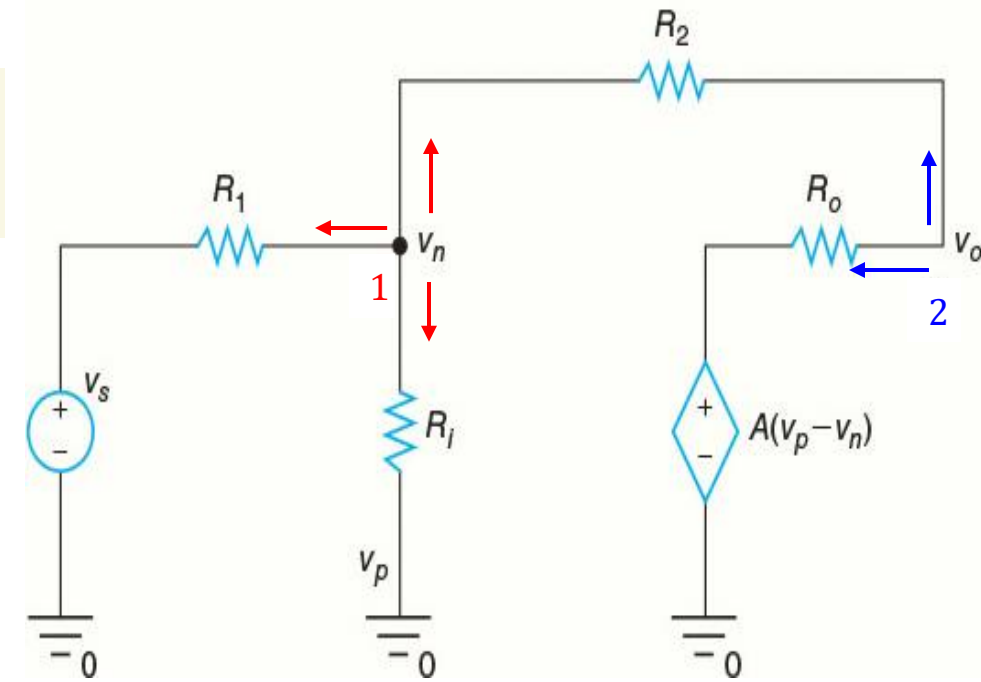


FIGURE 5.52
A model for an inverting configuration.

Analysis of Inverting Configuration (Cont.)

- If $R_o = 0$ and $R_i = \infty$, and $A \gg (R_1 + R_2)$ Equations (3) and (4) become, respectively

$$v_n = \frac{R_2 v_s}{R_1 + R_2 + AR_1} \cong \frac{R_2}{AR_1} v_s \approx 0 \quad (5)$$

$$v_o = \frac{-R_2 A v_s}{R_1 + R_2 + AR_1} \cong -\frac{R_2}{R_1} v_s \quad (6)$$

- Current flowing into the OP-AMP from negative terminal is : I_n

$$i_n = \frac{v_n}{R_i} = \frac{(R_o + R_2)v_s}{R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + AR_1 R_i} \approx \frac{R_2 v_s}{R_1 A R_i} \approx 0$$

- Current through R_1 is given by

$$i_1 = \frac{v_s - v_n}{R_1} = \frac{R_o + R_2 + R_i + AR_i}{R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + AR_1 R_i} v_s$$

- Input Resistance is given by

$$R_{in} = \frac{v_s}{i_1} = \frac{R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + AR_1 R_i}{R_o + R_2 + R_i + AR_i} \approx R_1$$

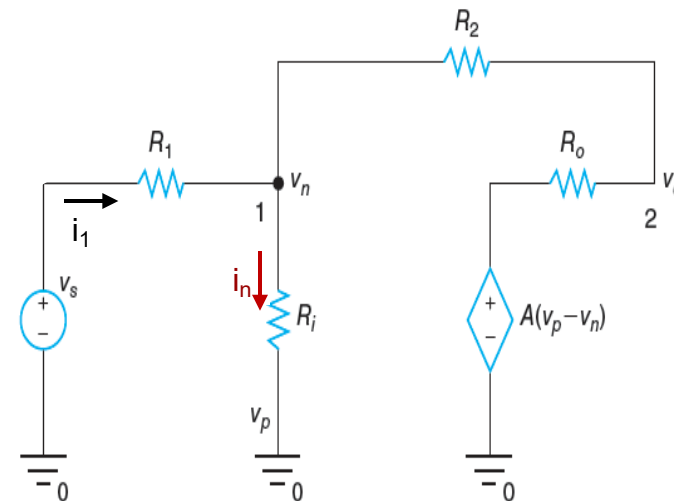


FIGURE 5.52

Analysis of Inverting Configuration (Cont.)

- ❑ **Output Resistance:** Apply test voltage V_t between node 2 and ground as shown in Figure 5.53. From the voltage divider rule, V_n is given by

$$v_n = \frac{R_1 \parallel R_i}{R_2 + (R_1 \parallel R_i)} v_t = \frac{\frac{R_1 R_i}{R_1 + R_i}}{R_2 + \frac{R_1 R_i}{R_1 + R_i}} v_t = \frac{R_1 R_i}{R_1 R_2 + R_2 R_i + R_1 R_i} v_t$$

- ❑ The current out of the test voltage source is

$$i_t = \frac{v_t - v_n}{R_2} + \frac{v_t + A v_n}{R_o} = \frac{v_t - \frac{R_1 R_i}{R_1 R_2 + R_2 R_i + R_1 R_i} v_t}{R_2} + \frac{v_t + A \frac{R_1 R_i}{R_1 R_2 + R_2 R_i + R_1 R_i} v_t}{R_o}$$

- ❑ Output Resistance is the ratio of V_t to i_t : $R_{out} = v_t / i_t$

$$R_{out} = \frac{R_o (R_1 R_2 + R_2 R_i + R_1 R_i)}{R_o R_1 + R_o R_i + A R_1 R_i + R_1 R_2 + R_2 R_i + R_1 R_i} \cong \frac{R_o (R_2 + R_1)}{A R_1} \approx 0$$

- ❑ The output resistance is close to zero for the inverting configuration.

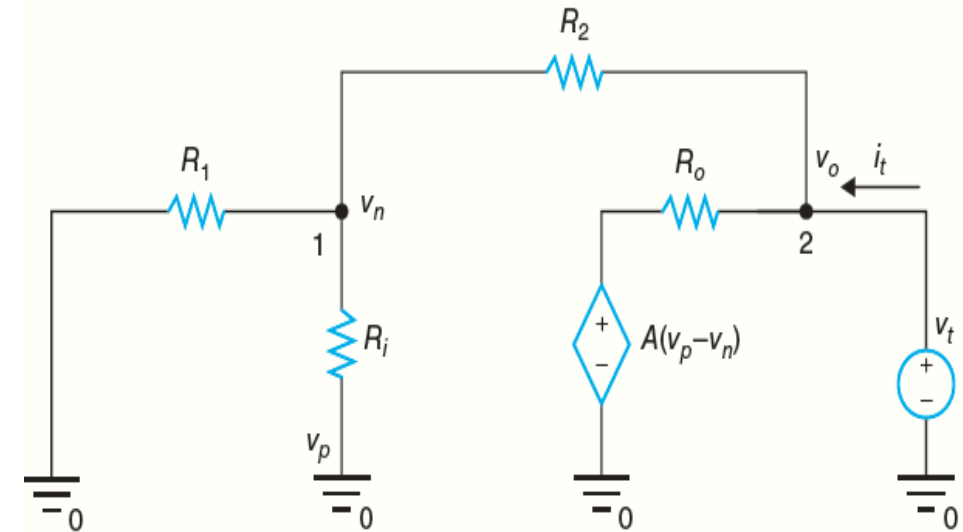


FIGURE 5.53

EXAMPLE 5.10

□ Find V_o in the circuit shown in Figure 5.54.

- Summing the currents leaving **Node 1 = 0**, we obtain
- Multiplication by 5000 yields

$$5V_n - 5 + 5V_n + V_n - V_o = 0 \Rightarrow 11V_n - V_o = 5 \quad (1)$$

- Summing the currents leaving **Node 2 = 0**, we obtain
- Multiplication by 5000 yields

$$V_o - V_n + 5V_o + 5000V_n = 0 \Rightarrow 4999V_n + 6V_o = 0 \quad (2)$$

- Multiply Equation (1) by 6: $66V_n - 6V_o = 30 \quad (3)$

- Add Equations (2) and (3): $5065V_n = 30$

- $V_n = 30/5065 = 0.005923 \text{ V} \quad (4)$

- Substitute Equation (4) into Equation (1):

$$V_o = 11V_n - 5 = -4.934847 \text{ V}$$

- Due to small value of A, V_o is off from -5 V (ideal model).

$$\frac{V_n - 1}{1000} + \frac{V_n}{1000} + \frac{V_n - V_o}{5000} = 0$$

$$\frac{V_o - V_n}{5000} + \frac{V_o - 1000(0 - V_n)}{1000} = 0$$

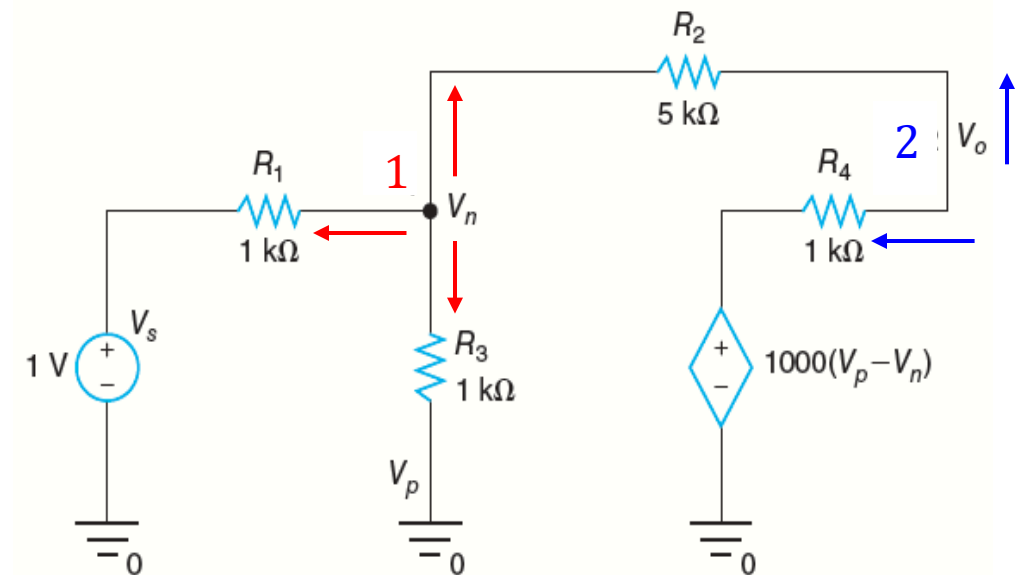


FIGURE 5.54

Analysis of Noninverting Conf.

□ A model for a noninverting configuration is shown in Figure 5.56.

□ KCL: Summing the currents leaving **node 2** = 0, we obtain

$$\frac{v_o - v_n}{R_2} + \frac{v_o - A(v_s - v_n)}{R_o} = 0 \quad (1)$$

□ KCL: Summing the currents leaving **node 1** = 0

$$\frac{v_n}{R_1} + \frac{v_n - v_s}{R_i} + \frac{v_n - v_o}{R_2} = 0 \Rightarrow \left(\frac{1}{R_1} + \frac{1}{R_i} + \frac{1}{R_2} \right) v_n = \frac{v_s}{R_i} + \frac{v_o}{R_2} \quad (2)$$

□ Solving Equations (1) and (2) for **V_n** and **V_o**, we get

$$v_n = \frac{R_1(R_o + R_2 + AR_i)v_s}{R_oR_i + R_oR_1 + R_iR_2 + R_1R_2 + R_1R_i + AR_1R_i} \quad (3)$$


$$v_o = \frac{(R_oR_1 + R_1R_iA + R_2R_iA)v_s}{R_oR_i + R_oR_1 + R_iR_2 + R_1R_2 + R_1R_i + AR_1R_i} \quad (4)$$

□ Current in OP-AMP from Negative Terminal is

$$i_n = \frac{v_n - v_s}{R_i} = \frac{((R_oR_1 + R_1R_2 + AR_iR_1)v_s)}{R_i(R_oR_i + R_oR_1 + R_iR_2 + R_1R_2 + R_1R_i + AR_1R_i)} - \frac{v_s}{R_i}$$

FIGURE 5.56

Model of a noninverting configuration.

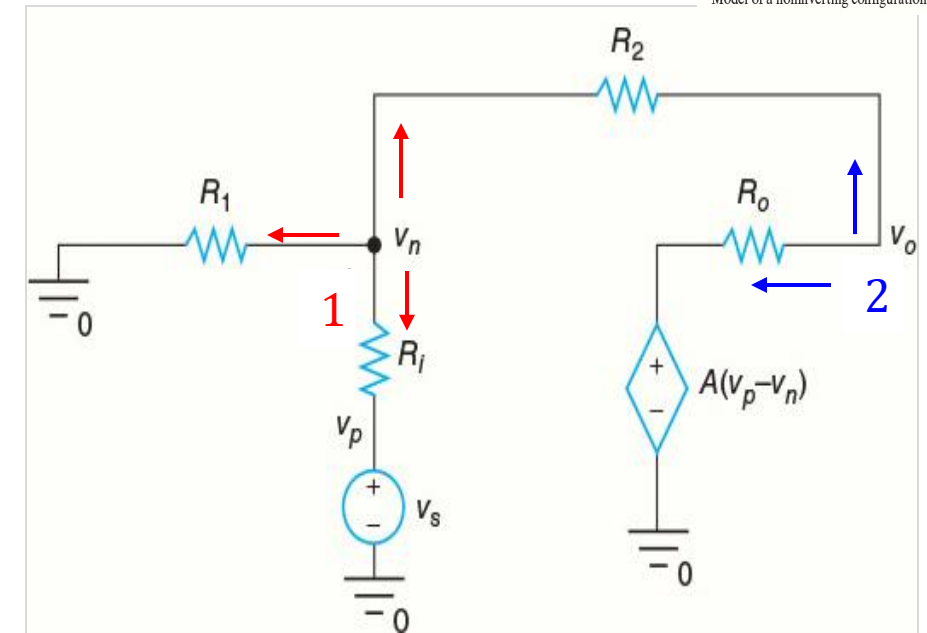

Analysis of Noninverting Configuration (Cont.)

- ❑ The current through R_i is given by

$$i_i = \frac{v_s - v_n}{R_i} = \frac{v_s}{R_i} - \frac{(R_o R_1 + R_1 R_2 + A R_1 R_i) v_s}{R_i (R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + A R_1 R_i)} = \frac{(R_o + R_2 + R_1) v_s}{R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + A R_1 R_i} \approx 0$$

- ❑ The **input resistance** is given by


$$R_{in} = \frac{v_s}{i_i} = \frac{R_o R_i + R_o R_1 + R_i R_2 + R_1 R_2 + R_1 R_i + A R_1 R_i}{R_o + R_2 + R_1} \cong \frac{A R_1 R_i}{R_o + R_2 + R_1} \approx \frac{A R_1 R_i}{R_2 + R_1}$$

- ❑ If $R_o = 0$ and $R_i = \infty$, equations (3) and (4) become:

$$v_n = \frac{A R_1 v_s}{R_1 + R_2 + A R_1} \approx v_s \quad (5)$$

$$v_o = \frac{A (R_1 + R_2) v_s}{R_1 + R_2 + A R_1} \cong \left(1 + \frac{R_2}{R_1} \right) v_s \quad (6)$$
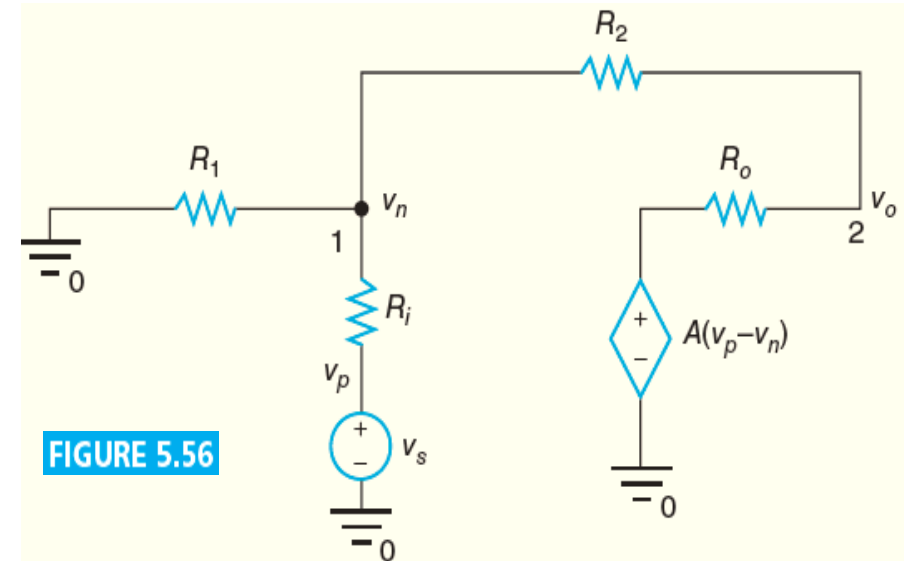
$$i_n = \frac{v_s}{R_i} - \frac{v_s}{R_i} = 0 \quad (7)$$



Analysis of Noninverting Configuration (Cont.)

- **Output resistance**, Apply **test voltage** between node 2 and ground as shown in Figure 5.57. From the voltage divider rule, v_n is given by

$$v_n = \frac{R_1 \parallel R_i}{R_2 + (R_1 \parallel R_i)} v_t = \frac{\frac{R_1 R_i}{R_1 + R_i}}{R_2 + \frac{R_1 R_i}{R_1 + R_i}} v_t = \frac{R_1 R_i}{R_1 R_2 + R_2 R_i + R_1 R_i} v_t$$


- The current out of the test voltage source is

$$i_t = \frac{v_t - v_n}{R_2} + \frac{v_t + A v_n}{R_o} = \frac{v_t - \frac{R_1 R_i}{R_1 R_2 + R_2 R_i + R_1 R_i} v_t}{R_2} + \frac{v_t + A \frac{R_1 R_i}{R_1 R_2 + R_2 R_i + R_1 R_i} v_t}{R_o}$$

- The output resistance is the ratio of v_t to i_t :

$$R_{out} = \frac{R_o (R_1 R_2 + R_2 R_i + R_1 R_i)}{R_o R_1 + R_o R_i + A R_1 R_i + R_1 R_2 + R_2 R_i + R_1 R_i} \cong \frac{R_o (R_2 + R_1)}{A R_1} \approx 0$$

- The output resistance is close to zero for noninverting configuration.

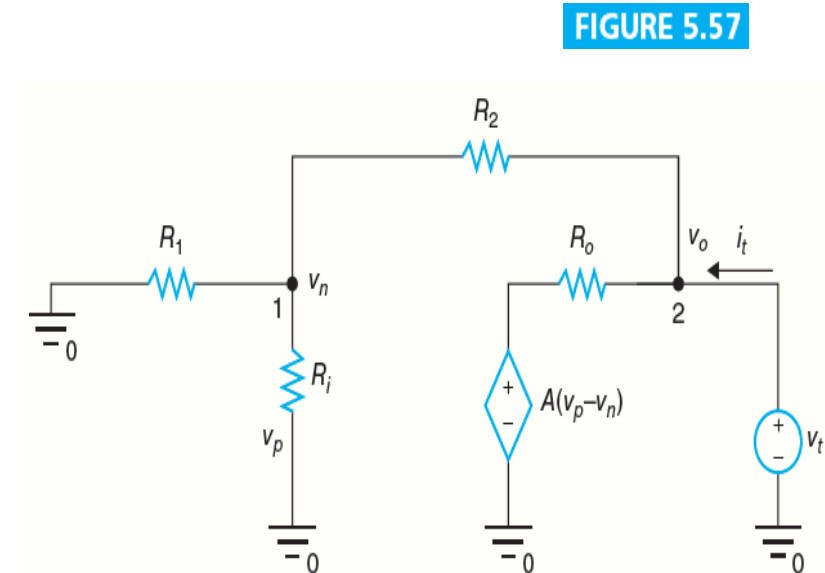

EXAMPLE 5.11

□ Find V_o in the circuit shown in Figure 5.58.

▪ Summing the currents leaving **node 1**, we obtain

$$\frac{V_n - 1}{2000} + \frac{V_n}{1000} + \frac{V_n - V_o}{9000} = 0$$

▪ Multiplication by 18000 yields

$$9V_n - 9 + 18V_n + 2V_n - 2V_o = 0 \Rightarrow 29V_n - 2V_o = 9 \quad (1)$$

▪ Summing the currents leaving **node 2**, we obtain $\frac{V_o - V_n}{9000} + \frac{V_o - 2000(1 - V_n)}{3000} = 0$

▪ Multiplication by 9000 yields

$$V_o - V_n + 3V_o - 6000 + 6000V_n = 0 \Rightarrow 5999V_n + 4V_o = 6000 \quad (2)$$

▪ Multiply Equation (1) by 2: $58V_n - 4V_o = 1 \quad (3)$

▪ Add Equations (2) and (3): $6057V_n = 6018$

▪ $V_n = 6018/6057 = 0.99356117 \text{ V} \quad (4)$

▪ Substitute Equation (4) into Equation (1):

$$V_o = (29/2)V_n - (9/2) = 9.90664 \text{ V}$$

▪ Due to small value of A , V_o is off from 10 V (ideal model).

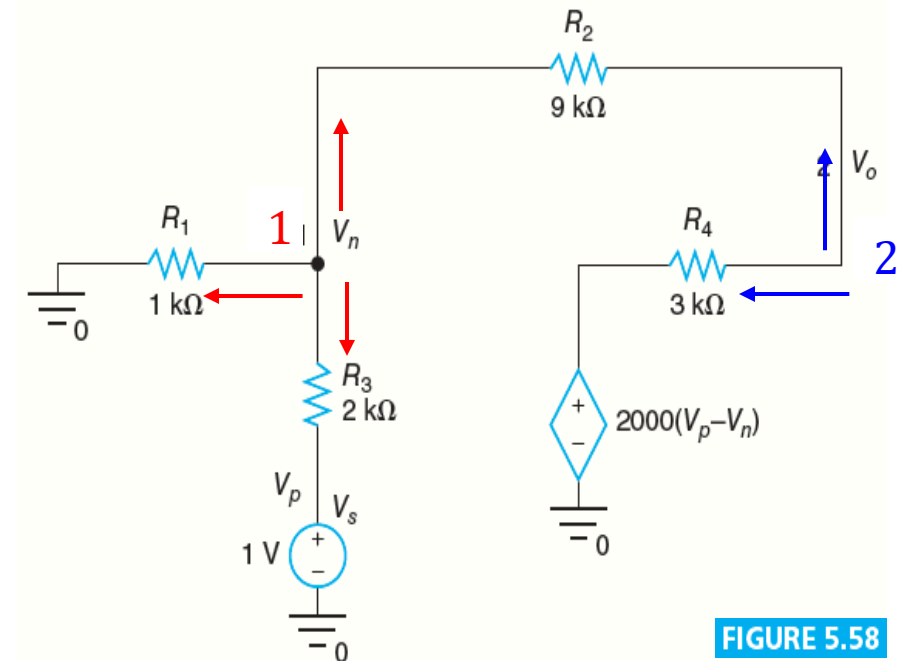


FIGURE 5.58

Summary

- ❑ Without the negative feedback component from the output, the output v_o will be large due to large gain A . The negative feedback component provides comparable gain in the denominator to offset the effects of large gain in the numerator.
- ❑ In the **ideal op amp model**, assume large input resistance ($R_i = \infty$), small output resistance ($R_o = 0$), and large gain A . Then, the current flowing into (or out of) the two input terminals is zero, that is, $i_p = 0$, and $i_n = 0$. Also, the voltage at the negative input terminal is equal to the voltage at the positive input terminal ($v_n = v_p$). This is called **virtual short**.
- ❑ In the **inverting configuration** of op amp, v_o , v_n , i_{R_i} , R_{in} , R_{out} are given by

$$v_o = -\frac{R_2}{R_1} v_s \quad v_n \cong \frac{R_2}{AR_1} v_s \approx 0 \quad i_{R_i} = \frac{v_d}{R_i} = \frac{-v_n}{R_i} \cong -\frac{R_2}{R_1 AR_i} v_s \approx 0 \quad R_{in} = \frac{v_s}{i_1} \approx R_1 \quad R_{out} \cong \frac{R_o(R_2 + R_1)}{AR_1} \approx 0$$

- ❑ In the **noninverting configuration** of op amp, v_o , v_n , i_{R_i} , R_{in} , R_{out} are given by

$$v_o \cong \left(1 + \frac{R_2}{R_1}\right) v_s \quad v_n = \frac{AR_1 v_s}{R_1 + R_2 + AR_1} \approx v_s \quad i_{R_i} = \frac{v_s - v_n}{R_i} \approx 0 \quad R_{in} \approx \frac{AR_1 R_i}{R_2 + R_1} \quad R_{out} \cong \frac{R_o(R_2 + R_1)}{AR_1} \approx 0$$

Summary (Continued)

❑ A summing amplifier can be designed in inverting configuration or in noninverting configuration.

❑ In the **inverting configuration**, for N inputs, the output can be

$$v_o = -(k_1 v_1 + k_2 v_2 + \dots + k_N v_N)$$

❑ In the **noninverting configuration**, for N inputs, the output can be

$$v_o = k_1 v_1 + k_2 v_2 + \dots + k_N v_N$$

❑ The output of a **difference amplifier** is given by

$$v_o = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{R_4}{R_3 + R_4} \right) v_2 - \frac{R_2}{R_1} v_1$$

If $R = R_1 = R_2 = R_3 = R_4$, the output is given by $v_o = v_2 - v_1$