





Circuit Analysis and Design

Academic Year 2025/2026 – Semester 1

Lecture 13 – RL Circuits

Masood Ur-Rehman, Muhammad Aslam and Ali Imran

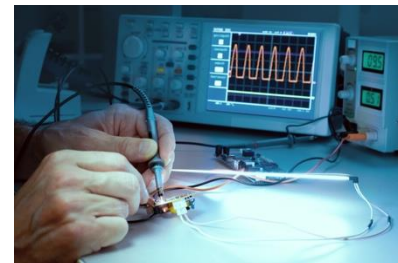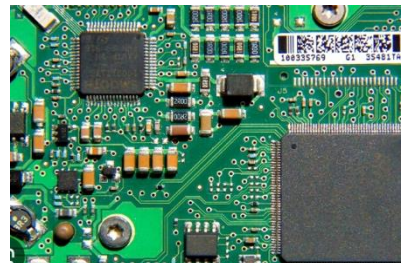[{masood.urrehman, muhammad.aslam.2, ali.imran}@glasgow.ac.uk](mailto:masood.urrehman@glasgow.ac.uk)



Agenda

- ☐ Natural response of RL circuit
- ☐ Step response of RL circuit

Introduction

- ❑ When a **capacitor or an inductor possesses initial energy**, the circuit responds to the initial energy until all the energy is spent, even when there is no input signal.
- ❑ The **response of a circuit due to initial energy only** is called a **natural response** (also transient response, zero input response, and source-free response).
- ❑ The **response of a circuit to a dc input signal (step input)** is called a **step response**. The step response includes the response due to the initial energy stored in the capacitor or inductor.

Natural Response of RL Circuit

- ❑ The switch in Figure 7.29 has been closed for a long time before it is opened at $t = 0$. At $t = 0$, the current through the inductor is equal to the current from the source I_S ; that is, $i(0) = I_0 = I_S$. For $t \geq 0$, the circuit shown in Figure 7.29 becomes the circuit shown in Figure 7.30, with initial current of $i(0) = I_0 = I_S$.
- ❑ Summing the currents leaving node 1, we obtain

$$i(t) + \frac{L}{R} \frac{di(t)}{dt} = 0 \Rightarrow \frac{di(t)}{dt} = -\frac{R}{L} i(t) \Rightarrow \frac{\frac{di(t)}{dt}}{i(t)} = -\frac{R}{L} \Rightarrow \frac{d}{dt} \ln[i(t)] = -\frac{R}{L} \quad (1)$$

- ❑ Integrating on both sides of the last expression of (1), we get

$$\ln[i(t)] = -\int_0^t \frac{R}{L} dt + K \quad (2)$$

- ❑ Exponentiation on both sides of Equation (2), we obtain

$$e^{\ln[i(t)]} = i(t) = e^{\left(-\frac{R}{L}t + K\right)} = e^K e^{-\frac{R}{L}t} = Ae^{-\frac{R}{L}t} \quad (3)$$

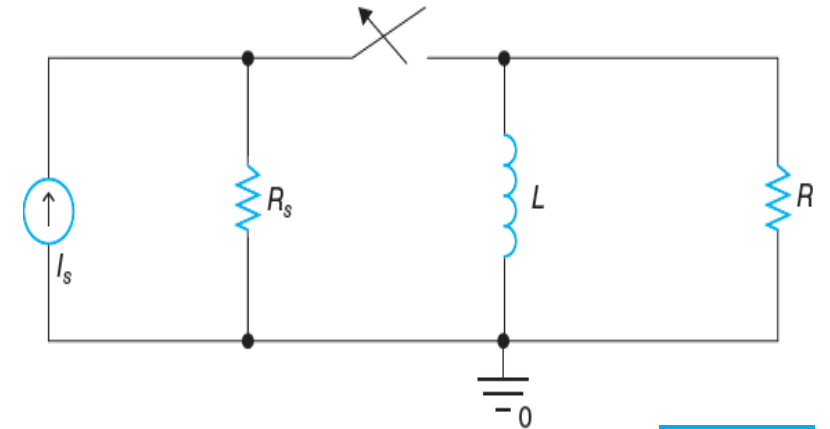


FIGURE 7.29

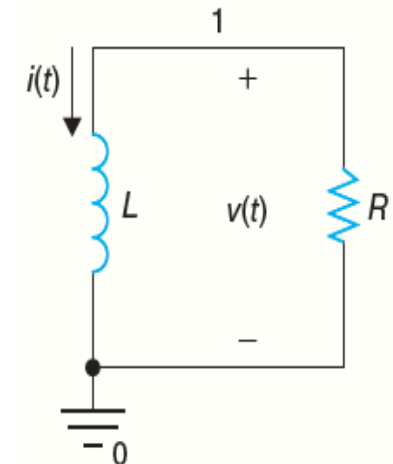


FIGURE 7.30

Natural Response of RL Circuit (Continued)

□ At $t = 0$, Equation (3) becomes : $i(0) = Ae^{-\frac{R}{L}0} = A$

□ Since, $A = i(0) = I_0$, therefore,

the **current through the inductor** (also resistor) is given by: $i(t) = i(0)e^{-\frac{t}{L/R}}u(t) = I_0e^{-\frac{t}{L/R}}u(t) \quad (4)$

where $u(t) = 1$ for $t \geq 0$ and $u(t) = 0$ for $t < 0$. $u(t)$ is called unit step function.

□ The **voltage across the inductor** is given by :

$$v(t) = L \frac{di(t)}{dt} = L \left(-\frac{R}{L} \right) i(0) e^{-\frac{t}{L/R}} = -Ri(0) e^{-\frac{t}{L/R}} = -RI_0 e^{-\frac{t}{L/R}} u(t)$$

□ The **instantaneous power** on the inductor is given by:

$$p(t) = v(t)i(t) = -I_0^2 R e^{-\frac{2t}{L/R}} u(t) \quad (\text{power is released})$$

□ The **energy** on the resistor is given by:

$$w(t) = \int_0^t p(\lambda) d\lambda = \frac{1}{2} LI_0^2 \left(1 - e^{-\frac{2t}{L/R}} \right) u(t)$$

▪ At $t = \infty$, $w(\infty) = 0.5LI_0^2$.

Time Constant of an RL Circuit

- ❑ The **ratio of L over R , L/R** , has a unit of seconds and is called a **time constant** of the RL circuit. The time constant is denoted by τ . Thus, $\tau = L/R$.
- ❑ In terms of τ , $i(t)$, $v(t)$, and $p_L(t)$ for the circuit shown in Figure 7.30 become, respectively

$$i(t) = I_0 e^{-\frac{t}{\tau}} u(t), v(t) = -RI_0 e^{-\frac{t}{\tau}} u(t), p_L(t) = -I_0^2 R e^{-\frac{2t}{\tau}} u(t)$$

- ❑ Figure 7.31 shows $i(t)$ for $\tau = 1, 2, 3, 4$, and 5 [$i(0) = 1$ A].
- ❑ **As the time constant τ increases, it takes longer time for the current through the inductor to decay.**

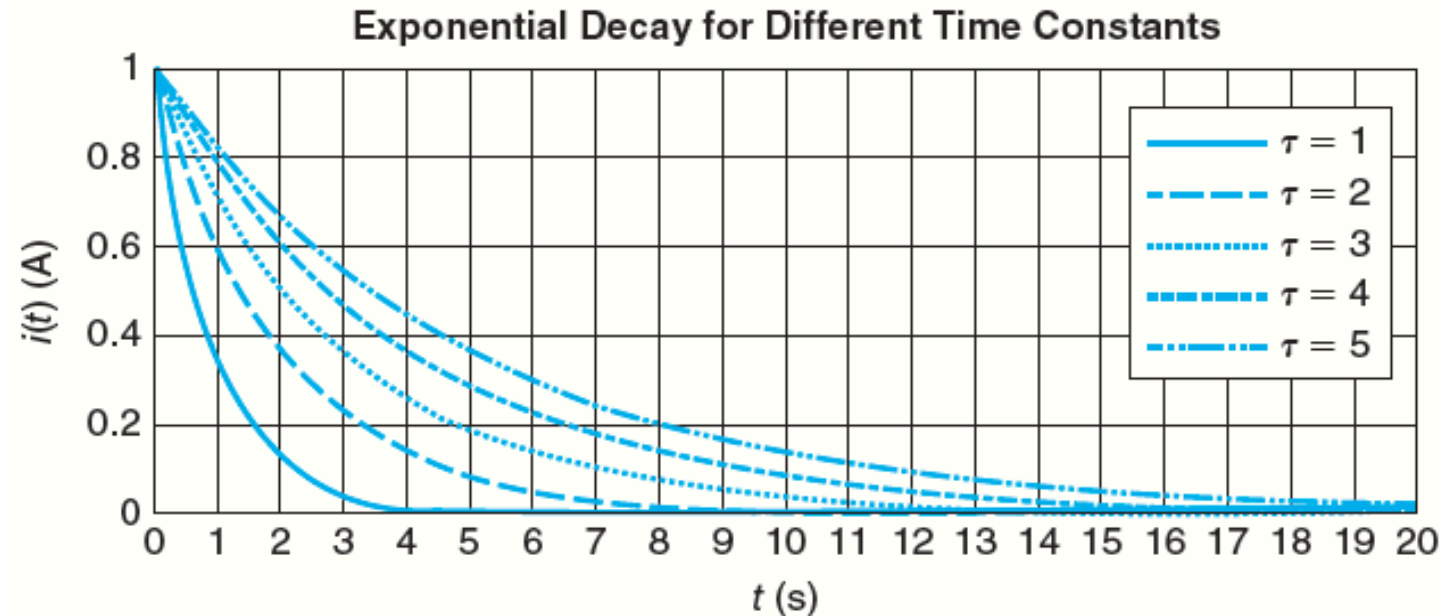


FIGURE 7.31

Time Constant of an RL Circuit (Continued)

- At $t = 0$, the current is at its peak value $i(0)$. At time $t = \tau$, the current is

$$i(\tau) = i(0)e^{-\frac{\tau}{\tau}} = i(0)e^{-1} = 0.3678794412i(0)$$

- At $t = \tau$, the current through the inductor drops to 36.788% of the initial value at $t = 0$.
For $t = 2\tau, 3\tau, 4\tau, 5\tau, \dots, 10\tau$, we have the values shown in Table 7.3.

n	$\exp(-n)$
0	1.0000000000000000
1.0000000000000000	0.367879441171442
2.0000000000000000	0.135335283236613
3.0000000000000000	0.049787068367864
4.0000000000000000	0.018315638888734
5.0000000000000000	0.006737946999085
6.0000000000000000	0.002478752176666
7.0000000000000000	0.000911881965555
8.0000000000000000	0.000335462627903
9.0000000000000000	0.000123409804087
10.0000000000000000	0.000045399929762

TABLE 7.3

Current Through
the Inductor
Normalized to I_0
at $t = n\tau$.

Time Constant of an RL Circuit (Continued)

- ❑ At five times the time constant, the current through the inductor due to initial energy on the inductor is less than 1% of the initial voltage (0.6738%). For all practical purposes, the transient response can be ignored after about five times the time constant.
- ❑ The time derivative of the current through the inductor is given by

$$\frac{di(t)}{dt} = I_0 \frac{d}{dt} e^{-\frac{t}{\tau}} = -\frac{I_0}{\tau} e^{-\frac{t}{\tau}} = -\frac{RI_0}{L} e^{-\frac{t}{\tau}}$$

- ❑ The rate of decay of the current through the inductor is at its maximum at $t = 0$ and slows down as time progresses. The rate of decay at $t = 0$ is $-I_0/\tau$.

- ❑ If the current decreases at this rate, $i(t)$ is given by

$$i_1(t) - I_0 = -\frac{I_0}{\tau}(t - 0)$$

- ❑ Figure 7.33 shows $i(t)$ and $i_1(t)$.

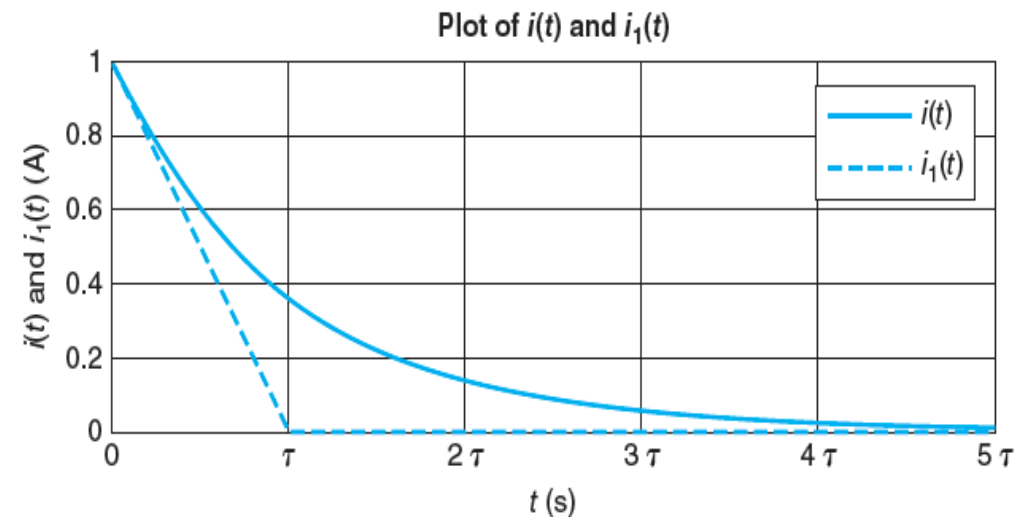


FIGURE 7.33

Finding the Time Constant

- ❑ If there is **one resistor with resistance R** and **one inductor with inductance L** , as in the circuit shown in Figure 7.30, the time constant is the ratio of L over R ; that is, $\tau = L/R$.
- ❑ If there is **one inductor with inductance L** and **more than one resistor** in the circuit,
 1. Find the **equivalent resistance R_{eq}** of all the resistors in the circuit seen from the inductor (Thévenin equivalent resistance).
 2. Then, the circuit reduces to **one inductor with inductance L** and **one resistor with resistance R_{eq}** . The time constant is given by $\tau = L/R_{eq}$.
- ❑ The current through the inductor is given by :
$$i(t) = I_0 e^{-\frac{t}{\tau}} u(t) \text{ A}$$
- ❑ Finding the current $i(t)$ through the inductor for the given circuit involves
 1. **finding the initial current $i(0)$ through the inductor,**
 2. **finding the equivalent resistance R_{eq} , and**
 3. **finding the time constant $\tau = L/R_{eq}$.**

EXAMPLE 7.9

□ The switch in the circuit shown in Figure 7.34 has been closed for a long time before it is opened at $t = 0$. Find the current $i(t)$ through the inductor and voltage $v(t)$ across the inductor for $t \geq 0$. Also, plot $i(t)$ and $v(t)$ for $t \geq 0$.

- For $t \leq 0$, the inductor can be treated as a short circuit. $i(0) = I_0 = V_s/R_1 = 12 \text{ V}/4 \text{ k}\Omega = 3 \text{ mA}$
- For $t \geq 0$, the time constant is $\tau = L/R = 0.5/100 = 0.005 \text{ s} = 5 \text{ ms}$. $1/\tau = 200 \text{ (1/s)}$
- For $t \geq 0$, $i(t) = I_0 \exp(-t/\tau) = 3 \exp(-200t) \text{ u(t) mA}$.
- For $t \geq 0$, $v(t) = L di(t)/dt = 0.5 \times 3 \times 10^{-3} \times (-200) \exp(-200t) \text{ u(t) V} = -0.3 \exp(-200t) \text{ u(t) V}$

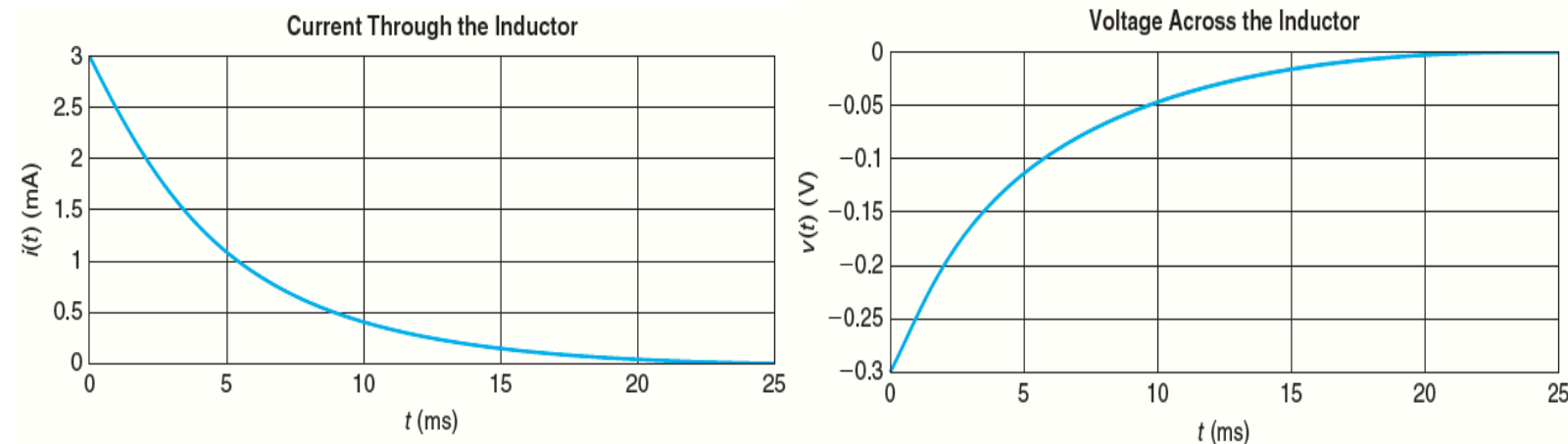


FIGURE 7.35

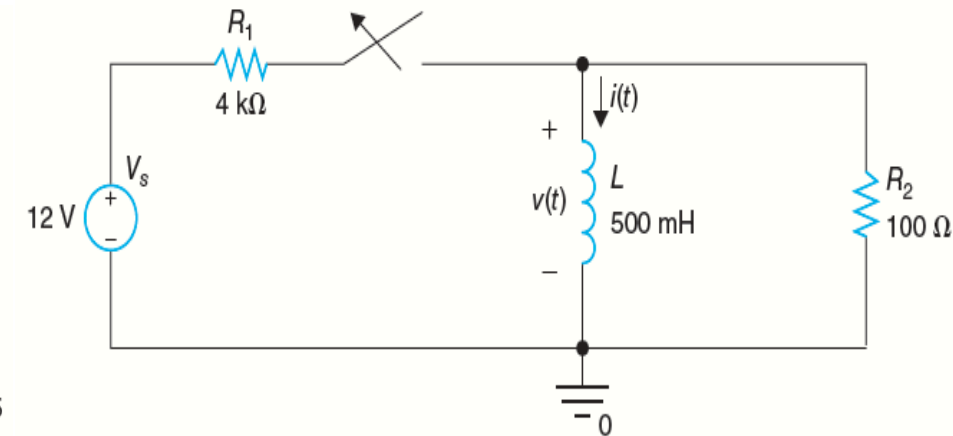


FIGURE 7.34

EXAMPLE 7.10

- The switch in the circuit shown in Figure 7.36 has been closed for a long time before it is opened at $t = 0$. Find the current $i(t)$ through the inductor for $t \geq 0$.
- For $t < 0$, the inductor can be treated as a short circuit. From the current divider rule, we get
$$i(0) = I_0 = I_s \times R_1 / (R_1 + R_2) = 20 \text{ mA} \times 2 \text{ k}\Omega / (2 \text{ k}\Omega + 3 \text{ k}\Omega) = 8 \text{ mA}$$
 - For $t \geq 0$, $R_{eq} = R_3 \parallel (R_4 + R_5) = 6 \times 30 / (6 + 30) \text{ k}\Omega = 5 \text{ k}\Omega$
 - For $t \geq 0$, the time constant is $\tau = L / R_{eq} = 0.01 / 5000 = 2 \text{ }\mu\text{s}$. $1/\tau = 500,000 \text{ (1/s)}$
 - For $t \geq 0$, $i(t) = I_0 \exp(-t/\tau) = 8 \exp(-500,000t) u(t) \text{ mA}$.


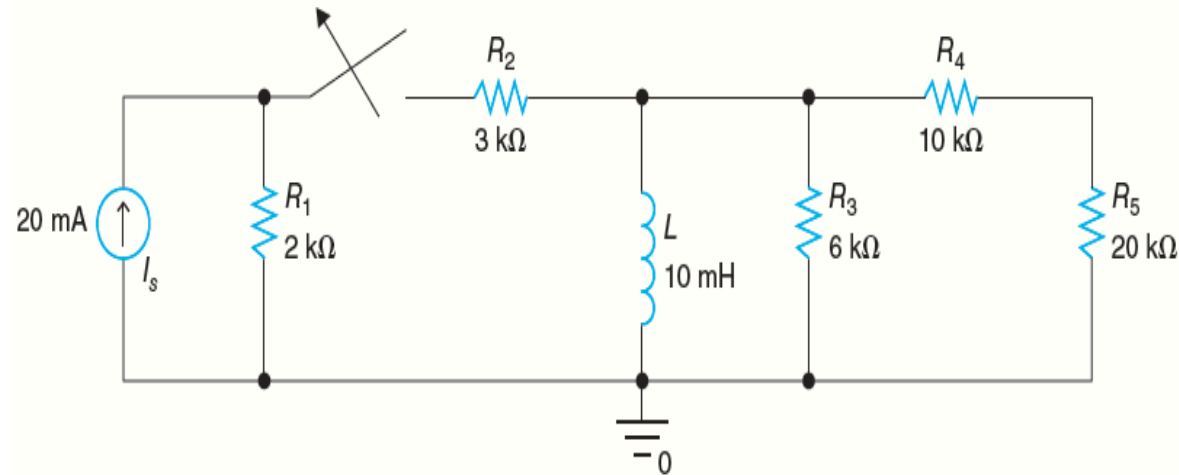


FIGURE 7.36

Class Quiz

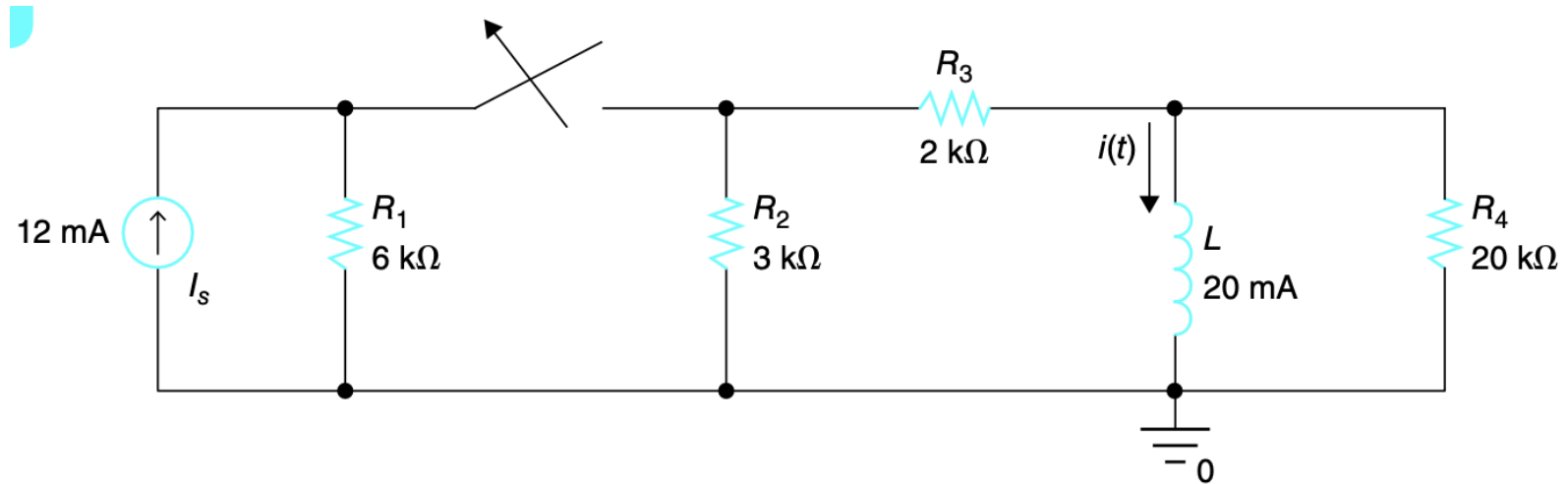- The switch in the circuit has been closed for a long time before it is opened at $t > 0$. Find the $i(0) = I_0$, the current at $t=0$ and τ through the inductor for $t > 0$.



- A. $I_0 = 3\text{ mA}$ and $\tau = 500 \times 10^{-6}\text{ s}$
- B. $I_0 = 6\text{ mA}$ and $\tau = 400 \times 10^{-6}\text{ s}$
- C. $I_0 = 6\text{ mA}$ and $\tau = 500 \times 10^{-6}\text{ s}$

EXAMPLE 7.11

□ The switch in the circuit shown in Figure 7.39 has been closed for a long time before it is opened at $t = 0$. Find the current $i(t)$ through the inductor for $t \geq 0$.

- For $t < 0$, the inductor can be treated as a short circuit.
- Let $R_a = R_3 \parallel R_4$. Then, $R_a = 12 \times 4 / (12 + 4) \text{ k}\Omega = 48/16 \text{ k}\Omega = 3 \text{ k}\Omega$.
- Let $R_b = R_a \parallel R_5$. Then, $R_b = 3 \times 3 / (3 + 3) \text{ k}\Omega = 9/6 \text{ k}\Omega = 1.5 \text{ k}\Omega$.
- Let $R_c = R_1 + R_2 + R_b$. Then, $R_c = 4.5 \text{ k}\Omega$. $I_{R1} = V_s / R_c = 2 \text{ mA}$, $V_a = V_s - 3 \text{ k}\Omega \times 2 \text{ mA} = 3 \text{ V}$
- $i(0) = I_0 = V_a / R_5 = 3 \text{ V} / 3 \text{ k}\Omega = 1 \text{ mA}$
- For $t \geq 0$, $R_{eq} = R_5 + (R_3 \parallel R_4) = 3 \text{ k}\Omega + 3 \text{ k}\Omega = 6 \text{ k}\Omega$
- $\tau = L / R_{eq} = 0.048 / 6000 = 8 \text{ }\mu\text{s}$. $1/\tau = 125,000 \text{ (1/s)}$
- For $t \geq 0$, $i(t) = I_0 \exp(-t/\tau) = \exp(-125,000t) \text{ u(t) mA}$.

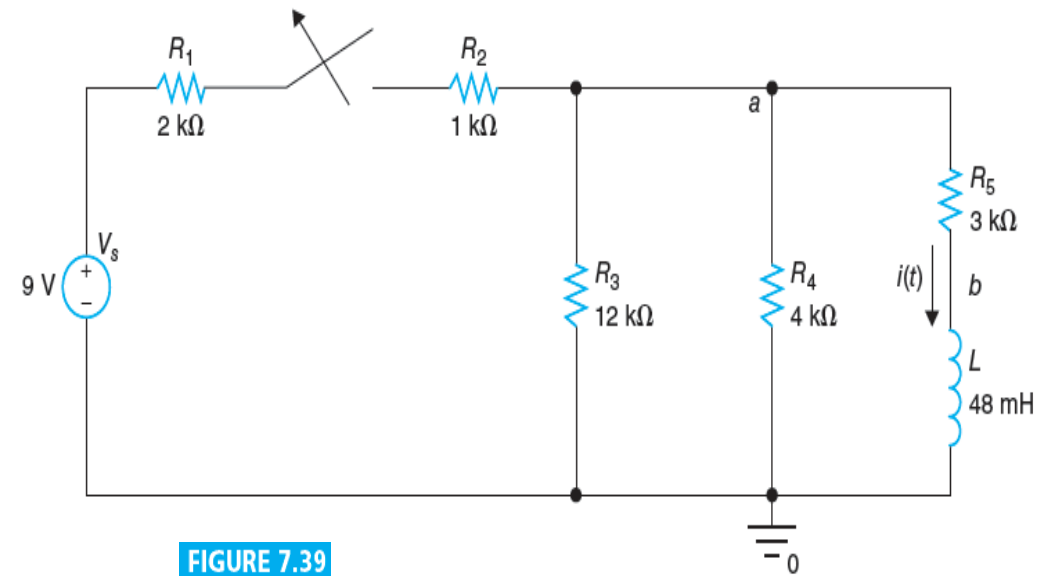


FIGURE 7.39

EXAMPLE 7.12

- The switch in the circuit shown in Figure 7.41 has been closed for a long time before it is opened at $t = 0$. Find the current $i(t)$ through the inductor and the voltage $v(t)$ across the inductor for $t \geq 0$. $R_a = R_2 + (R_3 \parallel R_4) + R_5 = 8 \text{ k}\Omega$
- From the current divider rule, the current through R_a is

$$I_{R_a} = I_s \times \frac{\frac{1}{R_a}}{\frac{1}{R_1} + \frac{1}{R_a} + \frac{1}{R_6}} = 11 \text{ mA} \times \frac{\frac{1}{8}}{\frac{1}{12} + \frac{1}{8} + \frac{1}{4}} = 11 \text{ mA} \times \frac{3}{11} = 3 \text{ mA}$$

- $i(0) = I_0 = I_{R_a}/2 = 1.5 \text{ mA}$
- $R_{eq} = R_3 + [R_4 \parallel (R_2 + R_6 + R_5)] = 12 \text{ k}\Omega$
- $\tau = L/R_{eq} = 0.036/12000 = 3 \mu\text{s}$. $1/\tau = 333,333 \text{ (1/s)}$
- $i(t) = I_0 \exp(-t/\tau) = 1.5 \exp(-333,333t) u(t) \text{ mA}$.
- $v(t) = L di(t)/dt = -18 \exp(-333,333t) u(t) \text{ V}$.

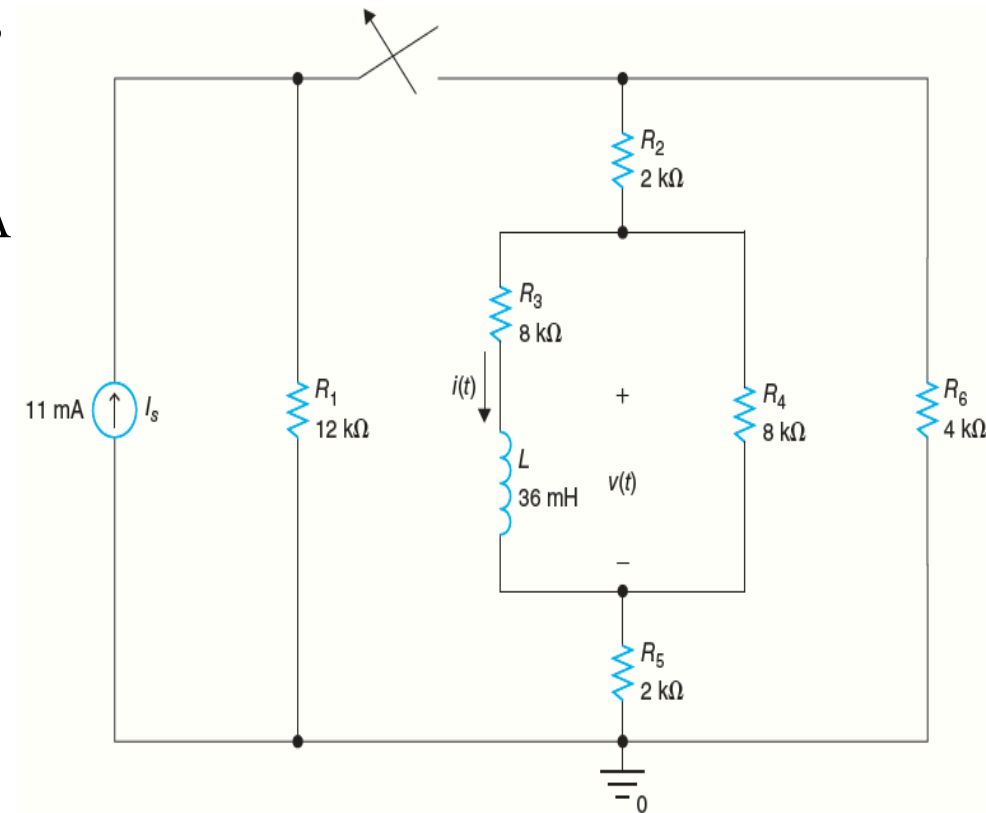


FIGURE 7.41

Step Response of RL Circuit

- The switch in the circuit shown in Figure 7.43 is closed at $t = 0$. At $t = 0$, the current through the inductor is $i(0) = I_0$. For $t \geq 0$, summing the currents leaving node 1, we obtain

$$-I_s + \frac{L}{R} \frac{di(t)}{dt} + i(t) = 0 \Rightarrow \frac{di(t)}{dt} = -\frac{R}{L} [i(t) - I_s] \Rightarrow \frac{\frac{di(t)}{dt}}{i(t) - I_s} = -\frac{R}{L} \Rightarrow \frac{d}{dt} \ln [i(t) - I_s] = -\frac{R}{L} \quad (1)$$

- Integrating on both sides of Equation (1), we obtain

$$\ln |i(t) - I_s| = \int_0^t \frac{-R}{L} dt = \frac{-Rt}{L} + K \quad (2)$$

- Exponentiation on both sides of Equation (2) yields

$$e^{\ln |i(t) - I_s|} = |i(t) - I_s| = e^K e^{-\frac{Rt}{L}} \Rightarrow i(t) - I_s = \pm e^K e^{-\frac{Rt}{L}} \quad (3)$$

- Let

$$A = \pm e^K$$

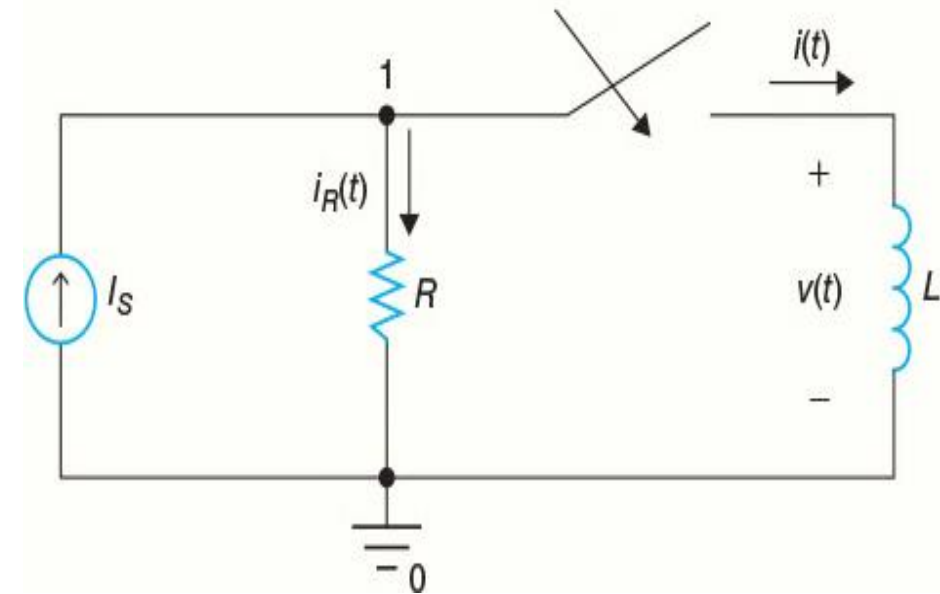


FIGURE 7.43

RL circuit with dc input.

Step Response of RL Circuit (Continued)

- Then, Equation (3) can be rewritten as

$$i(t) = I_S + Ae^{-\frac{t}{L/R}} \quad (4)$$

- The constant A can be found by applying the initial condition:

$$i(0) = I_0 = I_S + A \Rightarrow A = I_0 - I_S$$

- The current through the inductor can be written as ($\tau = L/R$)

$$i(t) = I_S + (I_0 - I_S)e^{-\frac{t}{L/R}} = I_S + (I_0 - I_S)e^{-\frac{t}{\tau}} \quad (5)$$

- This solution is valid for $t \geq 0$.

- At $t = 0$, the current is $i(0) = I_0$, and at $t = \infty$, the current is $i(\infty) = I_S$. The current through the inductor changes from the initial value of $i(0) = I_0$ at $t = 0$ to the final value of $i(\infty) = I_S$ at $t = \infty$.

Step Response of RL Circuit (Continued)

- ❑ The final value of $i(\infty) = I_S$ can be obtained from the circuit shown in Figure 7.43. At $t = \infty$, the inductor can be treated as a short circuit. The current through the inductor is I_S .
- ❑ Equation (5) can be rewritten as ($\tau = L/R$)

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}} = (\text{Final Value}) + [(\text{Initial Value}) - (\text{Final Value})]e^{-\frac{t}{(\text{Time Constant})}} \quad (6)$$

- ❑ Equation (6) is the solution to a differential equation given by the first equation in Equation (1):

$$\frac{di(t)}{dt} + \frac{1}{L/R}i(t) = \frac{1}{L/R}I_S \Rightarrow \frac{di(t)}{dt} + \frac{1}{\tau}i(t) = \frac{1}{\tau}I_S \quad (7)$$

- ❑ In the steady state at $t = \infty$, since $di(t)/dt = 0$, Equation (7) becomes $\frac{1}{\tau}i(\infty) = \frac{1}{\tau}I_S$

- ❑ Thus, $i(\infty) = I_S$.

- ❑ If there is a time delay t_d , replace t by $t - t_d$ in Equation (6).

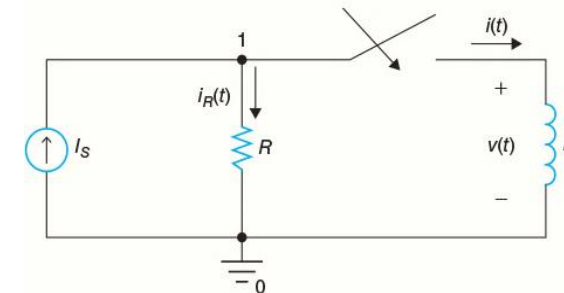


FIGURE 7.43
RL circuit with dc input.

Time Constant

- For RL circuits with one inductor in the circuit, the time constant is given by $\tau = L/R_{eq}$ where R_{eq} is the equivalent resistance seen from the inductor.
 - The equivalent resistance R_{eq} is the Thévenin equivalent resistance when the rest of the circuit (excluding the inductor) is converted to the Thévenin equivalent circuit.
 - In general, R_{eq} can be found by deactivating independent sources (short-circuit current sources and open-circuit voltage sources) and finding the equivalent resistance seen from the inductor. Other methods, such as test voltage and test current, can also be used.

- Figure 7.44 shows $i(t)$ given by Equation (5) for $I_S = 1\text{ A}$, $I_0 = 0\text{ A}$, and five different values of τ .
- At $t = \tau$, $i(\tau) = 0.63212 I_S$. At $t = \tau$, the current reaches 63.212% of the final value.
- At $t = 5\tau$, the current reaches 99.3262% of the final value.

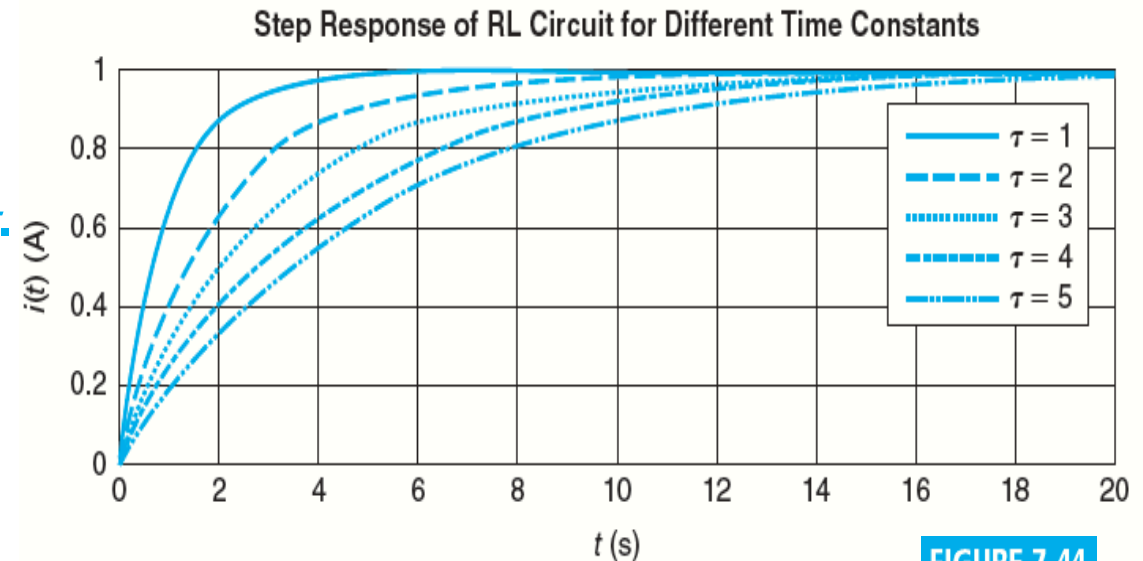


FIGURE 7.44

EXAMPLE 7.13

□ Let $L = 700 \text{ mH}$, $R = 200 \Omega$, $I_S = 5 \text{ mA}$, and $I_0 = 0 \text{ A}$ in the circuit shown in Figure 7.43. Find the current $i(t)$ through the inductor and voltage $v(t)$ across the inductor for $t \geq 0$, and plot $i(t)$ and $v(t)$.

- **Final value:** $i(\infty) = I_S = 5 \text{ mA}$
- **Time constant:** $\tau = L/R = 0.7/200 = 3.5 \text{ ms}$, $1/\tau = 285.7143 \text{ (1/s)}$
- $i(t) = [I_S + (I_0 - I_S)\exp(-285.7143t)] u(t) = 5[1 - \exp(-285.7143t)] u(t) \text{ mA}$
- $v(t) = L di(t)/dt = 0.7 \times (-0.005) \times (-285.7143) \exp(-285.7143t) u(t) = \exp(-285.7143t) u(t) \text{ V}$

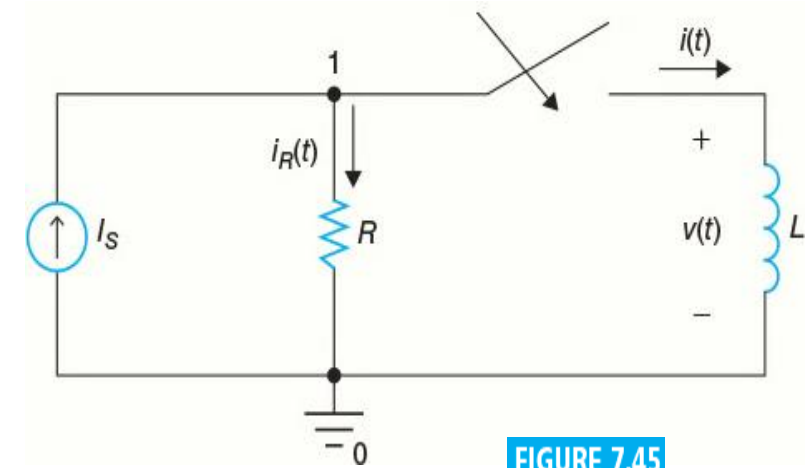
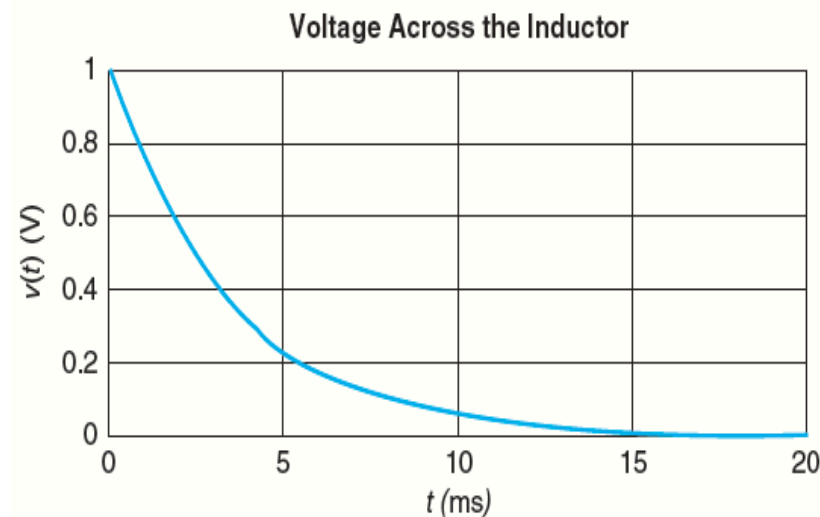
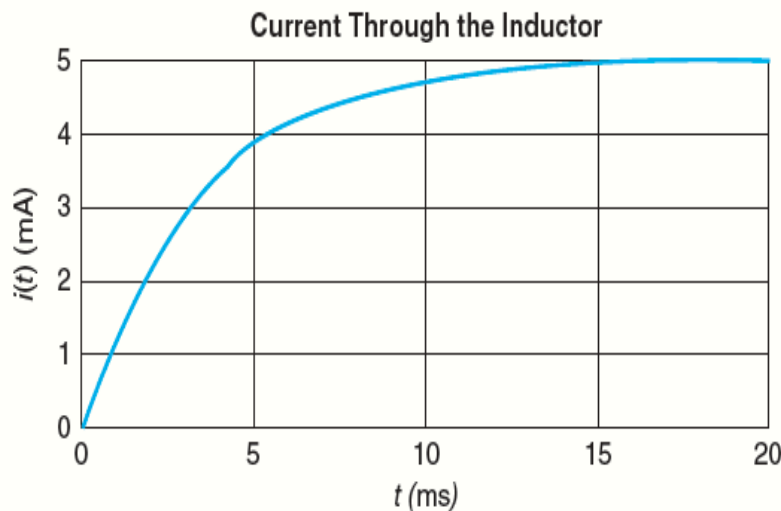


FIGURE 7.45

EXAMPLE 7.14

❑ The switch in the circuit shown in Figure 7.46 is closed at $t = 0$. The initial current through the inductor is $i(0) = I_0$. Find the current $i(t)$ through the inductor and the voltage $v(t)$ across the inductor.

❑ Sum the voltage drops around the mesh: $-V_s + Ri(t) + L \frac{di(t)}{dt} = 0 \Rightarrow \frac{di(t)}{dt} + \frac{R}{L}i(t) = \frac{1}{L}V_s$

❑ Final value: $\frac{R}{L}i(t) = \frac{1}{L}V_s \Rightarrow i(\infty) = \frac{V_s}{R}$

❑ Time constant: $\tau = L/R$

❑ Current: $i(t) = \left[\frac{V_s}{R} + \left(I_0 - \frac{V_s}{R} \right) e^{-\frac{t}{L/R}} \right] u(t) \text{ A}$

❑ Voltage: $v(t) = (V_s - RI_0) e^{-\frac{t}{L/R}} u(t) \text{ V}$

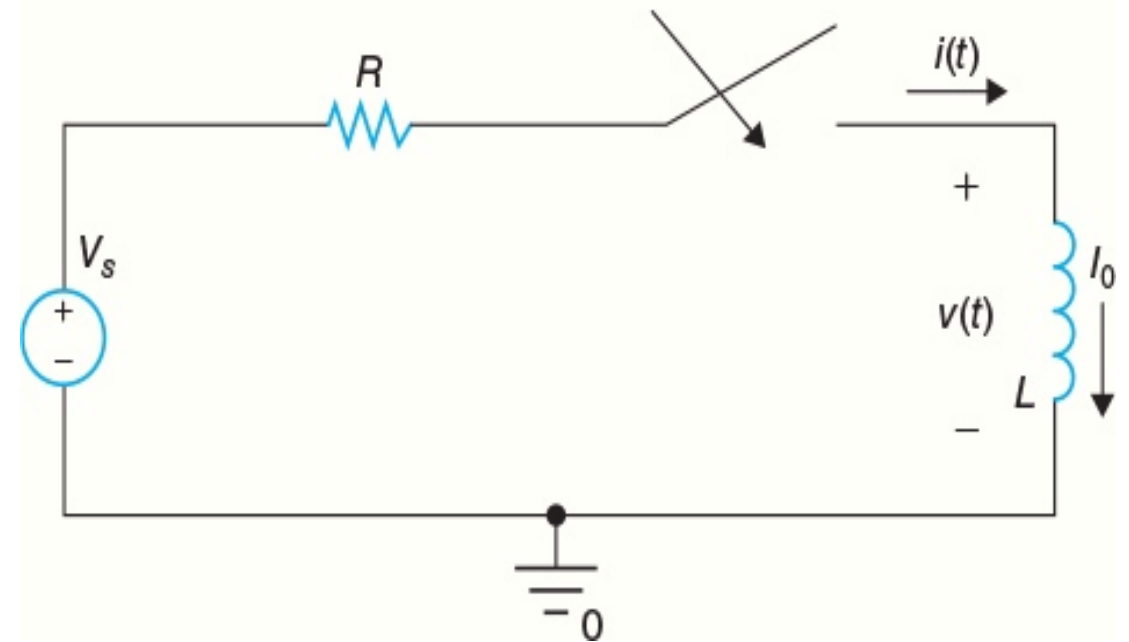


FIGURE 7.46

An RL circuit for EXAMPLE 7.14.

EXAMPLE 7.15

- In the circuit shown in Figure 7.48, switch 1 has been closed for a long time before it is opened at $t = 0$. Switch 2 is closed at $t = 12 \mu\text{s}$. Find the current $i(t)$ through the inductor for $t \geq 0$. Initial value: from the current divider rule, $i(0) = 9 \text{ mA} \times 2/(2 + 1) = 6 \text{ mA}$
- For $0 \leq t \leq 12 \mu\text{s}$, $R_{eq} = R_3 + R_4 = 4 \text{ k}\Omega$, $\tau = L/R = 6 \mu\text{s}$, $1/\tau = 166,667 \text{ (1/s)}$
 - For $0 \leq t \leq 12 \mu\text{s}$, $i(t) = 6 \exp(-166,667t)[u(t) - u(t - 12 \times 10^{-6})] \text{ mA}$, $i(12 \times 10^{-6}) = 0.8120 \text{ mA}$
 - At $t = \infty$, $V_{R4} = 18 \text{ V} \times 0.75/(6 + 0.75) = 2 \text{ V}$, $i(\infty) = V_{R4}/R_3 = 2 \text{ mA}$
 - For $12 \mu\text{s} \leq t$, $R_{eq} = R_3 + (R_4 || R_5) = 3 \text{ k}\Omega$, $\tau = L/R_{eq} = 8 \mu\text{s}$, $1/\tau = 125,000 \text{ (1/s)}$
 - $i(t) = [2 + (0.8120 - 2)\exp(-125,000(t - 12 \times 10^{-6}))] u(t - 12 \times 10^{-6}) \text{ mA}$
 - $= [2 - 1.188 \exp(-125,000(t - 12 \times 10^{-6}))] u(t - 12 \times 10^{-6}) \text{ mA}$


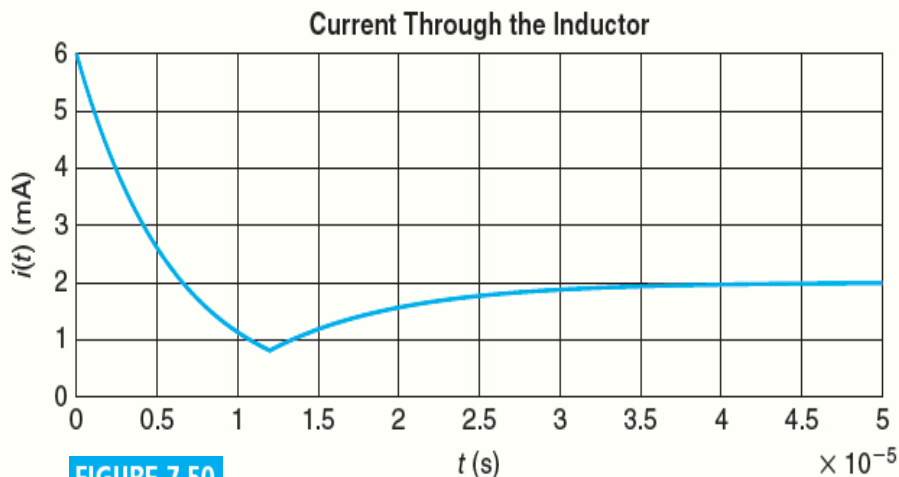



FIGURE 7.48

Circuit for
EXAMPLE 7.15.

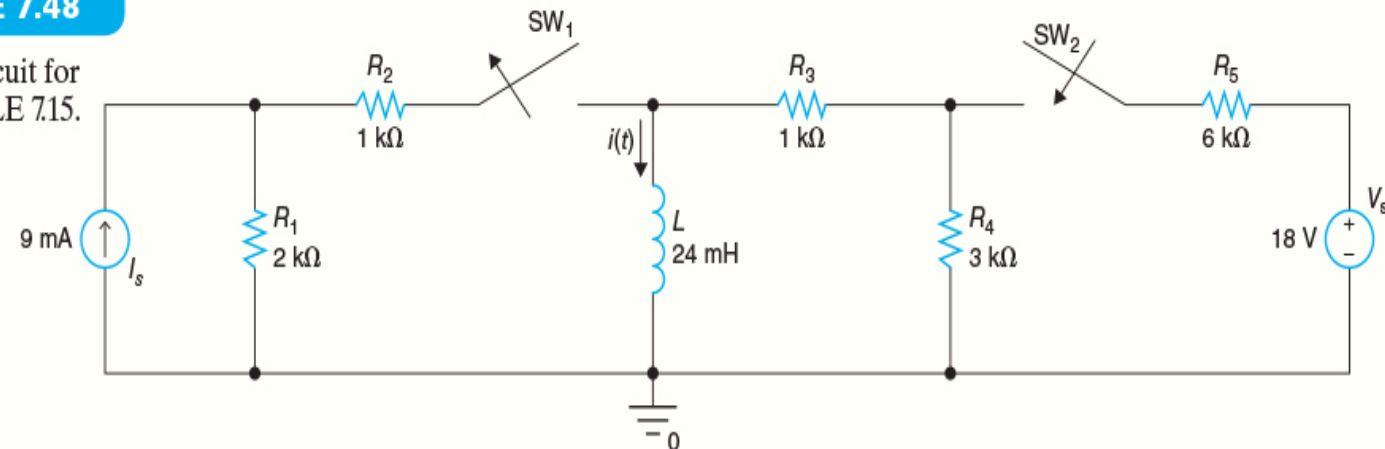

EXAMPLE 7.16

- In the circuit shown in Figure 7.51, switch 1 has been closed for a long time before it is opened at $t = 0$. Switch 2 is closed at $t = 2 \mu\text{s}$. Find the current $i(t)$ through the inductor for $t \geq 0$. Initial value: $R_2 \parallel (R_3 + R_5) = 10 \text{ k}\Omega$, $I_{R1} = 18 \text{ V}/18 \text{ k}\Omega = 1 \text{ mA}$, $i(0) = 1 \text{ mA} / 2 = 0.5 \text{ mA}$
- For $0 \leq t \leq 2 \mu\text{s}$, $R_{eq1} = R_4 \parallel (R_3 + R_2 + R_5) = 8 \text{ k}\Omega$, $\tau = L/R_{eq1} = 3.75 \mu\text{s}$, $1/\tau = 266,667 \text{ (1/s)}$
 - For $0 \leq t \leq 2 \mu\text{s}$, $i(t) = 0.5 \exp(-266,667t)[u(t) - u(t - 2 \times 10^{-6})] \text{ mA}$, $i(2 \times 10^{-6}) = 0.2933 \text{ mA}$
 - At $t = \infty$, $R_a = R_6 \parallel (R_3 + R_2) = 20 \text{ k}\Omega$, $i(\infty) = I_s \times R_a / (R_5 + R_a) = 1.2 \text{ mA}$
 - For $2 \mu\text{s} \leq t$, $R_{eq2} = R_4 \parallel (R_a + R_5) = 7.5 \text{ k}\Omega$, $\tau = L/R_{eq2} = 4 \mu\text{s}$, $1/\tau = 250,000 \text{ (1/s)}$
 - $i(t) = [1.2 + (0.2933 - 1.2)\exp(-250,000(t - 2 \times 10^{-6}))] u(t - 2 \times 10^{-6}) \text{ mA}$
 $= [1.2 - 0.9067 \exp(-250,000(t - 2 \times 10^{-6}))] \times u(t - 2 \times 10^{-6}) \text{ mA}$

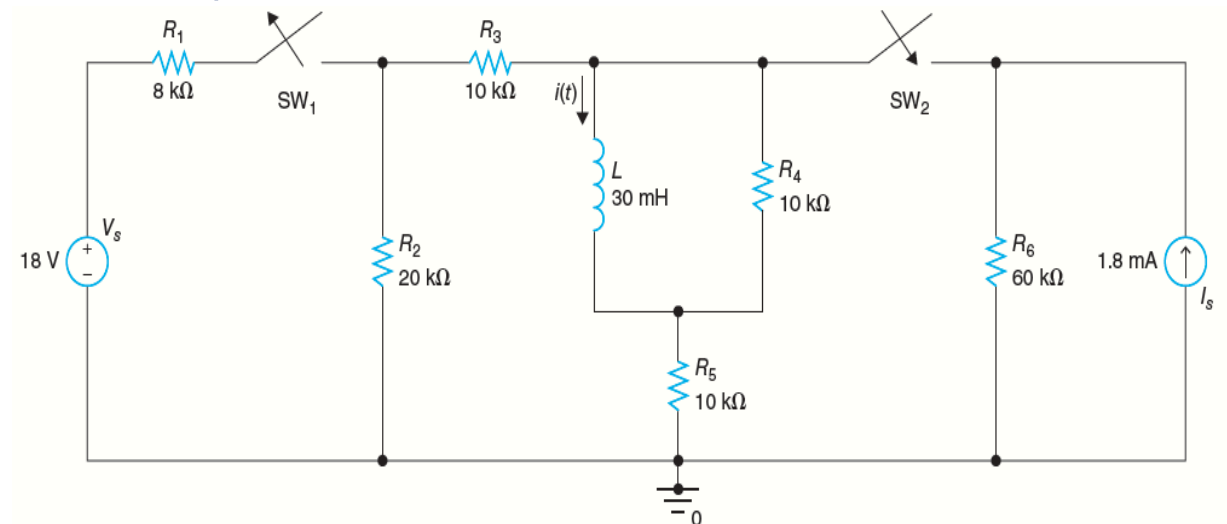

EXAMPLE 7.17

□ In the circuit shown in Figure 7.55, the switch has been closed for a long time before it is opened at $t = 0$. Find the current $i(t)$ through the inductor for $t \geq 0$.

- $i(0)$ from V_s : $R_a = (R_1 + R_2) \parallel R_3 = 254.5455 \, \Omega$, $V_{a1} = V_s \times R_a / (R_a + R_4) = 8.4 \, \text{V}$, $i_1(0) = V_{a1} / R_3 = 0.021 \, \text{A}$
- $i(0)$ from I_s : $R_b = R_3 \parallel R_4 = 133.3333 \, \Omega$, $R_c = R_1 \parallel (R_2 + R_b) = 200 \, \Omega$, $V_{R1} = R_c \times I_s = 11 \, \text{V}$
- $V_{a2} = V_{R1} \times R_b / (R_b + R_2) = 4.4 \, \text{V}$, $i_2(0) = V_{a2} / R_3 = 0.011 \, \text{A}$
- $i(0) = i_1(0) + i_2(0) = 32 \, \text{mA}$
- $i(\infty) = I_s \times R_1 / (R_1 + R_2 + R_3) = 25 \, \text{mA}$
- $R_{eq} = R_2 + R_1 + R_3 = 1100 \, \Omega$
- $\tau = L / R_{eq} = 2 \times 10^{-4} \, \text{s} = 0.2 \, \text{ms}$, $1/\tau = 5000 \, (1/\text{s})$
- $i(t) = [25 + (32 - 25)\exp(-5000t)] u(t) \, \text{mA}$
- $i(t) = [25 + 7\exp(-5000t)] u(t) \, \text{mA}$

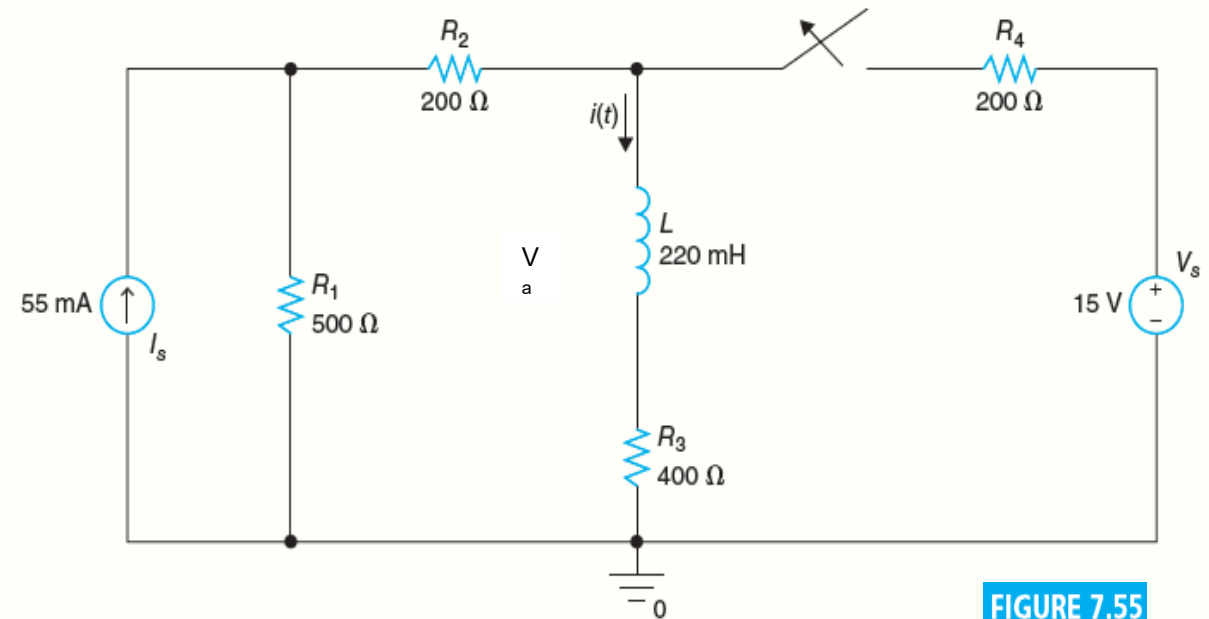


FIGURE 7.55

EXAMPLE 7.18

□ The initial current through the inductor is $i(0) = 1 \text{ A}$ in the circuit shown in Figure 7.59. Find the current $i_o(t)$ through R_2 for $t \geq 0$.

- Sum the voltage drops around the mesh in the left side:

$$-9 + 3i(t) + 5 \frac{di(t)}{dt} = 0 \Rightarrow \frac{di(t)}{dt} + 0.6i(t) = 1.8$$

- $0.6 i(\infty) = 1.8 \Rightarrow i(\infty) = 3 \text{ A}$
- $1/\tau = 0.6 \Rightarrow \tau = 1/0.6 = 5/3 = 1.6667$
- $i(t) = [3 + (1 - 3)\exp(-0.6t)] u(t) \text{ A}$
- $i(t) = [3 - 2\exp(-0.6t)] u(t) \text{ A}$
- $di(t)/dt = 1.2 \exp(-0.6t) u(t) \text{ A}$
- $i_o(t) = (2/6) \times di(t)/dt = 0.4 \exp(-0.6t) u(t) \text{ A}$

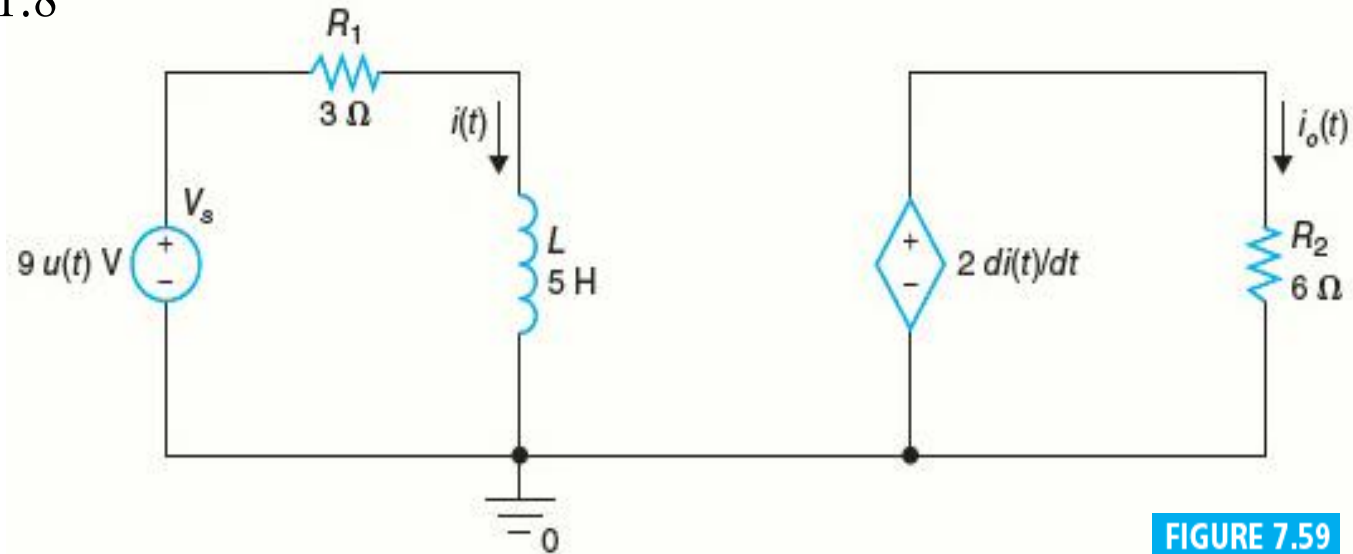


FIGURE 7.59

Summary

- Figure 7.30 shows a circuit with one inductor with inductance L and one resistor with resistance R connected in parallel. Let the initial current through the inductor at $t = 0$ be $i(0)$. Then, the current $i(t)$ through the inductor for $t \geq 0$ is given by

$$i(t) = i(0)e^{-\frac{t}{\tau}}u(t) \text{ A}$$

where the time constant τ is given by $\tau = L/R$.

- Figure 7.43 shows a circuit with a current source with current I_s , a resistor with resistance R , and an inductor with inductance L connected in parallel. Let the initial current through the inductor at $t = 0$ be $i(0) = I_0$. Then, the current $i(t)$ through the inductor for $t \geq 0$ is given by

$$i(t) = I_s + (I_0 - I_s)e^{-\frac{t}{\tau}}$$

where the time constant τ is given by $\tau = L/R$.