




# Circuit Analysis and Design

Academic Year 2025/2026 – Semester 1
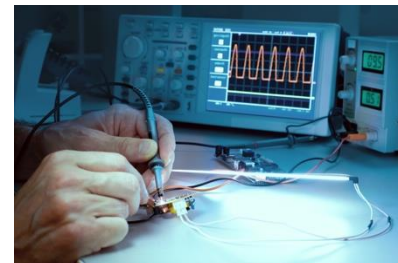
## Lecture 8 - Circuit Theorems

Masood Ur-Rehman, Muhammad Aslam and Ali Imran

[{masood.urrehman, muhammad.aslam.2, ali.imran}@glasgow.ac.uk](mailto:masood.urrehman@glasgow.ac.uk)



# Agenda

- Thévenin's theorem
- Summary


# Thévenin's Theorem

- A circuit consisting of a voltage source  $V_{th}$  and a series resistor  $R_{th}$ , representing the original circuit looking from a pair of terminals, is called a **Thévenin equivalent circuit**. The voltage  $V_{th}$  is called **Thévenin equivalent voltage**, and the resistance  $R_{th}$  is called **Thévenin equivalent resistance**.
- The Thévenin equivalent circuit can be used to **simplify** the circuit. When a load resistor is connected between terminals  $a$  and  $b$ , we can find the **effects of the circuit on the load** from the Thévenin equivalent circuit.
- We **do not need all the details** of the original circuit to find the voltage, current, and power on the load.
- Let the voltage across terminals  $a$  and  $b$  of the Thévenin equivalent circuit be  $V_{oc}$ . This voltage is called **open-circuit voltage** because terminals  $a$  and  $b$  are open (with an infinite resistance between  $a$  and  $b$ ).
- No current flows through the Thévenin equivalent resistor  $R_{th}$ . Thus,

$$V_{oc} = V_{th}$$

FIGURE 4.50

A Thévenin equivalent circuit.

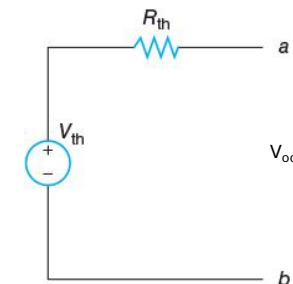

# Thévenin's Theorem (Continued)

- If the terminals  $a$  and  $b$  are short-circuited, as shown in Figure 4.51, the current through the short circuit is given by

$$I_{sc} = \frac{V_{th}}{R_{th}} = \frac{V_{oc}}{R_{th}}$$


- If we solve this equation for  $R_{th}$ , we have

$$R_{th} = \frac{V_{oc}}{I_{sc}}$$

- This equation can be used to find the Thévenin equivalent resistance  $R_{th}$ .

**FIGURE 4.51**

Short-circuit current.

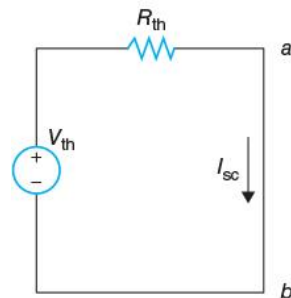

# Finding the Thévenin Equivalent Resistance

## Method 1:

- Deactivate all the independent sources by short-circuiting voltage sources and open-circuiting current sources.
- $R_{th}$  is the equivalent resistance looking into the circuit from terminals  $a$  and  $b$ .
- This method cannot be used if the circuit contains dependent sources.

## Method 2:

- Short-circuit terminals  $a$  and  $b$ . Find the short-circuit current  $I_{sc}$ .
- The Thévenin equivalent resistance is given by  $R_{th} = V_{oc}/I_{sc} = V_{th}/I_{sc}$ .

## Method 3:

- Deactivate all the independent sources.
- Apply a test voltage of 1 V (or any other value) between terminals  $a$  and  $b$  with terminal  $a$  connected to the positive terminal of the test voltage.
- Measure the current  $I_t$  flowing out of the positive terminal of the test voltage source.
- The Thévenin equivalent resistance  $R_{th}$  is given by  $R_{th} = V_t/I_t$ .
- Alternatively, apply a test current between terminals  $a$  and  $b$  after deactivating the independent sources, and measure the voltage across  $a$  and  $b$  of the test current source. The Thévenin equivalent resistance  $R_{th}$  is the ratio of the voltage across  $a$  and  $b$  to the test current.

## Finding $V_{th}$ and $R_{th}$

- Consider the circuit shown in Figure 4.52. We are interested in finding  $V_{th}$  and  $R_{th}$  across terminals  $a$  and  $b$ .
- To find  $V_{th}$ :
  - Sum the currents leaving node 1:

$$\frac{V_1 - 5}{5000} - 0.002 + \frac{V_1}{20000} + \frac{V_1 - V_2}{5000} = 0$$

- Multiply by 20,000:

$$4V_1 - 20 - 40 + V_1 + 4V_1 - 4V_2 = 0 \Rightarrow 9V_1 - 4V_2 = 60 \quad (1)$$

- Sum the currents leaving node 2:


$$\frac{V_2 - V_1}{5000} + \frac{V_2}{6000} = 0$$

- Multiply by 30,000:  $6V_2 - 6V_1 + 5V_2 = 0 \Rightarrow V_1 = 11/6V_2 \quad (2)$

- Substituting (2) in (1):  $V_2 = V_{th} = V_{oc} = 4.8 \text{ V}$

FIGURE 4.52

A circuit with a pair of terminals.

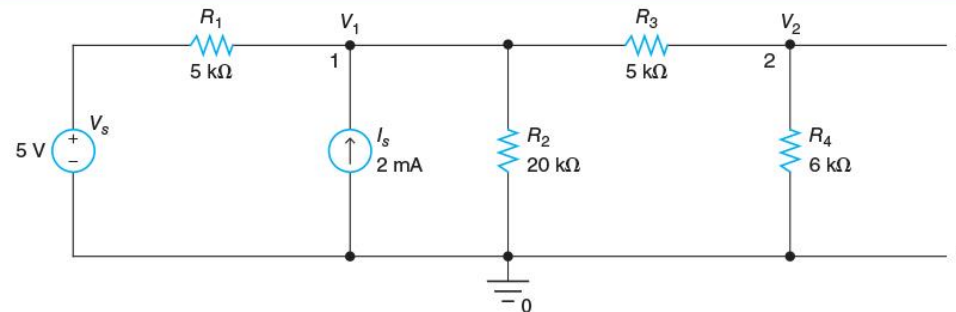


## Finding $V_{th}$ and $R_{th}$ (Continued)

- To find  $R_{th}$  (**Method 1**):
  - We deactivate  $V_s$  by short-circuiting it and  $I_s$  by open-circuiting it as shown in Figure 4.53, and find the equivalent resistance looking into the circuit from terminals  $a$  and  $b$ .
  - $R_a = R_1 \parallel R_2 = 5 \times 20 / (5 + 20) \text{ k}\Omega = 100/25 \text{ k}\Omega = 4 \text{ k}\Omega$
  - $R_b = R_3 + R_a = 9 \text{ k}\Omega$
  - $R_{th} = R_4 \parallel R_b = 6 \times 9 / (6 + 9) \text{ k}\Omega = 54/15 \text{ k}\Omega = 3.6 \text{ k}\Omega$
  - The Thévenin equivalent circuit is shown in Figure 4.57.


**FIGURE 4.53**

The circuit from Figure 4.52 with its sources deactivated.

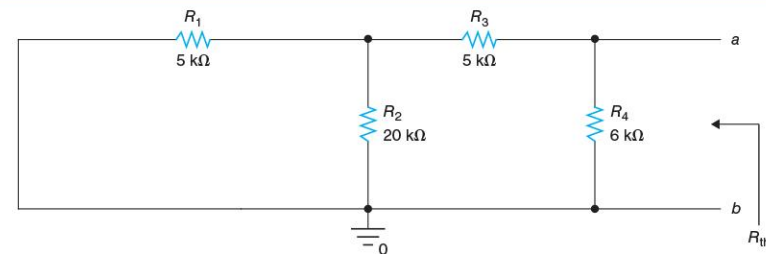

**FIGURE 4.57**

The Thévenin equivalent circuit.

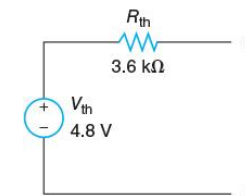

## Finding $V_{th}$ and $R_{th}$ (Continued)

- Consider a circuit shown in Figure 4.58. We are interested in finding  $V_{th}$  and  $R_{th}$  across terminals  $a$  and  $b$ .
- To find  $V_{th}$ :
  - Sum the currents leaving node 1:

$$\frac{V_1 - 5}{2000} + \frac{V_1}{6000} + \frac{V_1 - V_2}{1000} = 0$$

- Multiply by 6000:

$$3V_1 - 15 + V_1 + 6V_1 - 6V_2 = 0 \Rightarrow 10V_1 = 6V_2 + 15 \Rightarrow V_1 = 0.6V_2 + 1.5$$

- Sum the currents leaving node 2:

$$\frac{V_2 - V_1}{1000} + 0.0005V_1 + \frac{V_2}{10000} = 0$$

- Multiply by 10000:


$$10V_2 - 10V_1 + 5V_1 + V_2 = 0 \Rightarrow 11V_2 - 5V_1 = 0$$

$$\Rightarrow 11V_2 - 5(0.6V_2 + 1.5) = 0$$

$$\Rightarrow 8V_2 = 7.5$$

- $V_{th} = V_{oc} = V_2 = 7.5/8 = 0.9375 \text{ V}$

**FIGURE 4.58**  
A circuit with VCCS.

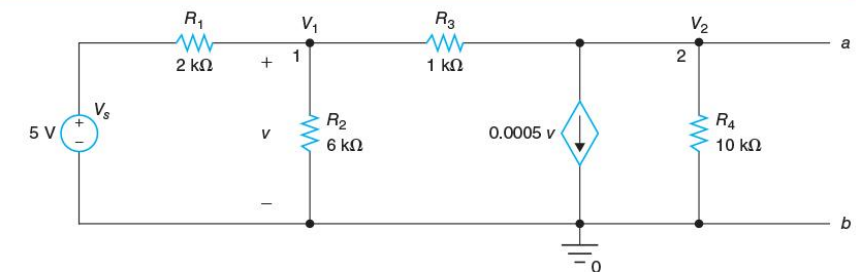



## Finding $V_{th}$ and $R_{th}$ (Continued)

- To find  $R_{th}$  (**Method 2**):
- Since there is a dependent source, Method 1 cannot be used to find  $R_{th}$ . Either Method 2 or Method 3 can be used. We will learn Method 2.

- Terminals  $a$  and  $b$  are short-circuited as shown in Figure 4.59.  $V_2 = 0$ .

- Sum the currents leaving node 1:

$$\frac{V_1 - 5}{2000} + \frac{V_1}{6000} + \frac{V_1}{1000} = 0$$

- Multiply by 6000:

$$3V_1 - 15 + V_1 + 6V_1 = 0 \Rightarrow 10V_1 = 15 \Rightarrow V_1 = 1.5 \text{ V}, \quad v = V_1 = 1.5 \text{ V}$$

- The current through  $R_3$  is given by:  $I_{R3} = V_1/R_3 = 1.5 \text{ V}/1 \text{ k}\Omega = 1.5 \text{ mA}$

- The current through VCCS is given by:


$$I_{VCCS} = 0.0005V_1 = 0.0005 \times 1.5 \text{ A} = 0.75 \text{ mA}$$

- $I_{sc} = I_{R3} - I_{VCCS} = 1.5 \text{ mA} - 0.75 \text{ mA} = 0.75 \text{ mA}$

- $R_{th} = V_{th}/I_{sc} = 0.9675 \text{ V}/0.75 \text{ mA} = 1.25 \text{ k}\Omega$

**FIGURE 4.59**

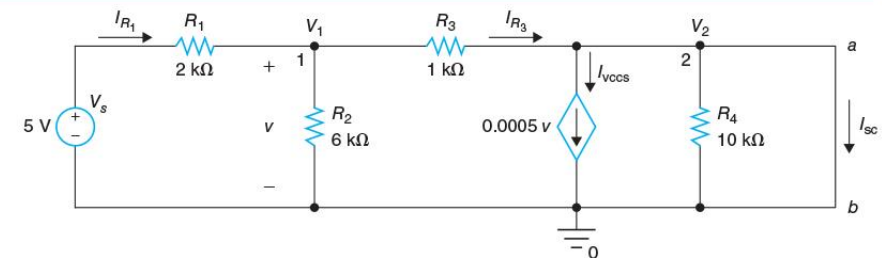A circuit with a short circuit between  $a$  and  $b$ .



## Finding $V_{th}$ and $R_{th}$ (Continued)

- We wish to find  $V_{th}$  and  $R_{th}$  for the circuit shown in Figure 4.79.
- To find  $V_{th}$ :

- Sum the currents leaving node 1: 
$$-0.002 + \frac{V_1}{2000} + \frac{V_1 - V_2}{5000} = 0$$

- Multiply by 10000:

$$20 + 5V_1 + 2V_1 - 2V_2 = 0 \Rightarrow 7V_1 = 2V_2 + 20 \Rightarrow V_1 = (2/7)V_2 + 20/7 \quad (1)$$

- Sum the currents leaving node 2: 
$$\frac{V_2 - V_1}{5000} + 2\frac{V_1}{2000} + \frac{V_2}{3000} = 0$$


- Multiply by 30000:

$$6V_2 - 6V_1 + 30V_1 + 10V_2 = 0 \quad (2)$$

- Substitute (1) into (2):  $24[(2/7)V_2 + 20/7] + 16V_2 = 0 \Rightarrow 160V_2 = -480$   
 $\Rightarrow V_{th} = V_{oc} = V_2 = -3 \text{ V}$


FIGURE 4.79

Circuit with a CCCS.

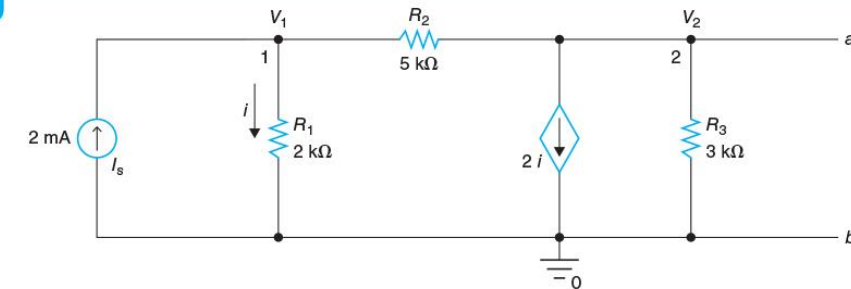
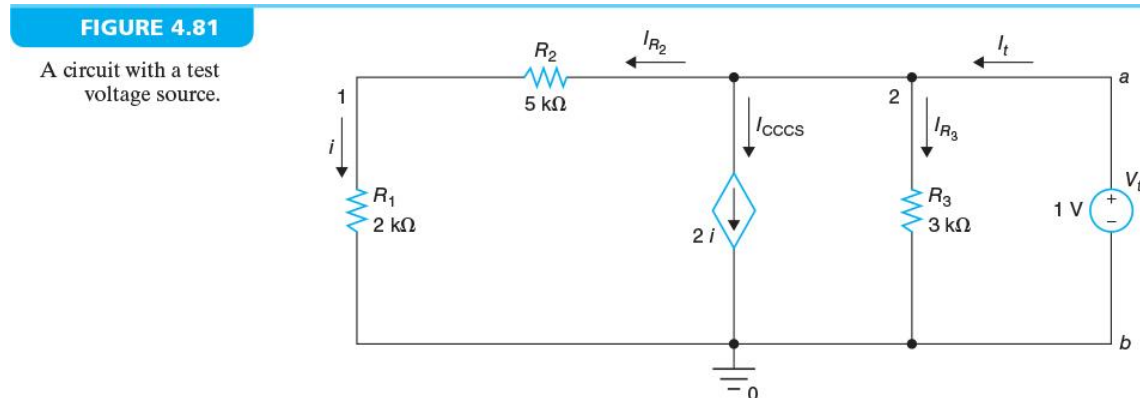
## Finding $V_{th}$ and $R_{th}$ (Continued)

- To find  $R_{th}$  (**Method 3**):
  - $R_{th}$  can be found using Method 2 or Method 3. We will learn Method 3.
  - $I_s$  is open-circuited and a test voltage of 1 V is applied between  $a$  and  $b$  as shown in Figure 4.81.
  - $V_t = 1 \text{ V}$
  - $i = I_{R2} = V_t / (R_1 + R_2) = (1/7) \text{ mA}$
  - $I_{CCCS} = 2i = (2/7) \text{ mA}$ ,  $I_{R3} = V_t / R_3 = (1/3) \text{ mA}$
  - The current flowing out of the positive terminal of the test voltage source is given by:  
 $I_t = I_{R2} + I_{CCCS} + I_{R3} = (3/21) \text{ mA} + (6/21) \text{ mA} + (7/21) \text{ mA} = (16/21) \text{ mA}$
  - Thévenin equivalent resistance is:  $R_{th} = V_t / I_t = 21/16 \text{ k}\Omega = 1.3125 \text{ k}\Omega$



## EXAMPLE 4.8

Find  $V_{th}$  and  $R_{th}$  for the circuit shown in Figure 4.67.

- Sum the currents leaving node 1:

$$\frac{V_1 - 22.5}{15000} + \frac{V_1}{30000} + \frac{V_1 - V_2}{5000} = 0$$

- Multiply by 30,000:

$$2V_1 - 45 + V_1 + 6V_1 - 6V_2 = 0 \Rightarrow 9V_1 = 6V_2 + 45 \Rightarrow V_1 = (2/3)V_2 + 5 \quad (1)$$

- Sum the currents leaving node 2:

$$\frac{V_2 - V_1}{5000} - 0.004 + \frac{V_2}{10000} = 0$$


- Multiply by 10,000:

$$2V_2 - 2V_1 - 40 + V_2 = 0 \quad (2)$$

- Substituting (1)→(2):  $3V_2 - 2[(2/3)V_2 + 5] = 40 \Rightarrow (5/3)V_2 = 40$   
 $\Rightarrow V_{th} = V_{oc} = V_2 = 30 \text{ V}$


FIGURE 4.67

Circuit for  
EXAMPLE 4.8.

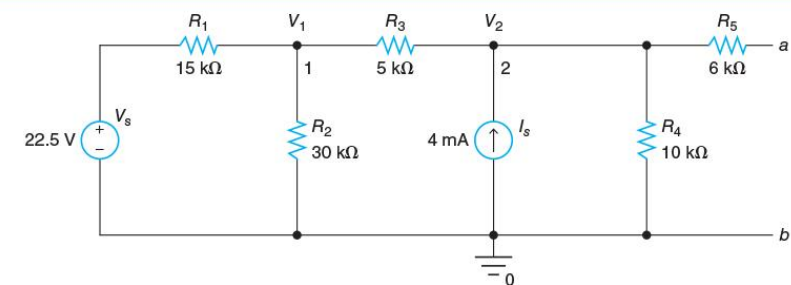


## EXAMPLE 4.8 (Continued)

- To find  $R_{th}$ ,  $V_s$  is short-circuited and  $I_s$  is open-circuited as shown in Figure 4.70.
- $R_a = R_1 \parallel R_2 = 15 \times 30 / (15 + 30) \text{ k}\Omega = 450 / 45 \text{ k}\Omega = 10 \text{ k}\Omega$
- $R_b = R_3 + R_a = 5 \text{ k}\Omega + 10 \text{ k}\Omega = 15 \text{ k}\Omega$
- $R_c = R_4 \parallel R_b = 10 \times 15 / (10 + 15) \text{ k}\Omega = 150 / 25 \text{ k}\Omega = 6 \text{ k}\Omega$
- $R_{th} = R_5 + R_c = 6 \text{ k}\Omega + 6 \text{ k}\Omega = 12 \text{ k}\Omega$
- The Thévenin equivalent circuit is shown in Figure 4.71.

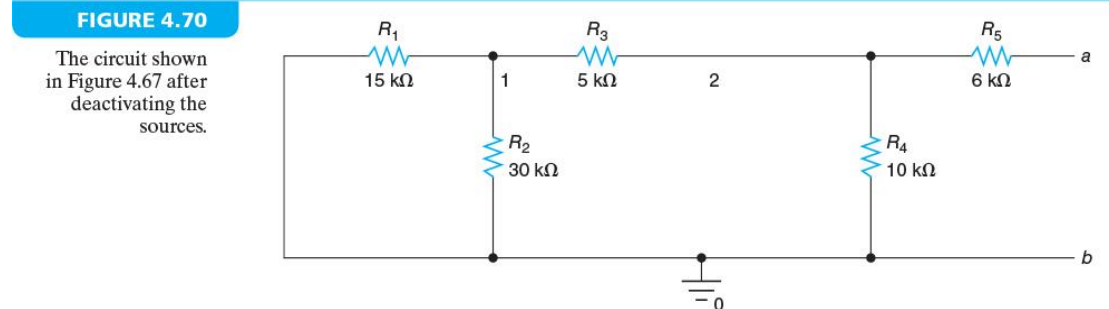

**FIGURE 4.71**

The Thévenin equivalent circuit.

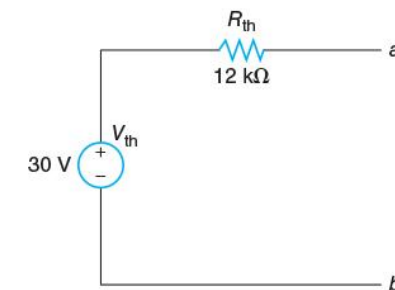


## EXAMPLE 4.9

Find  $V_{th}$  and  $R_{th}$  for the circuit shown in Figure 4.73.

**FIGURE 4.73**

Circuit for  
EXAMPLE 4.9.

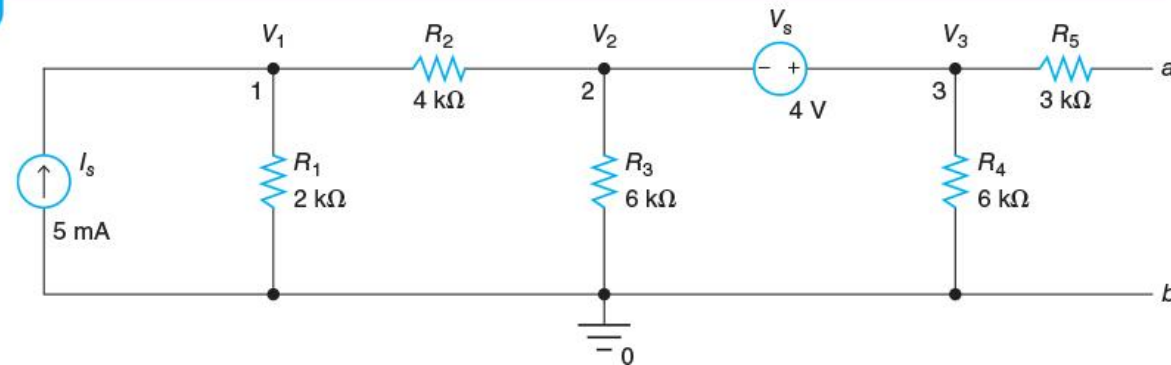

## EXAMPLE 4.11

Find  $V_{th}$  and  $R_{th}$  for the circuit shown in Figure 4.85.

- Since  $i_2 = 0$ , the voltage across CCVS is zero ( $2i_2 = 0$ ). Thus,

$$i_1 = V_s / R_1 = 10 \text{ V} / 5 \Omega = 2 \text{ A}$$

- $V_{th} = V_{oc} = 3i_1 = 6 \text{ V}$

- To find  $R_{th}$ , after deactivating  $V_s$ , a test voltage of 1 V is applied across  $a$  and  $b$  as shown in Figure 4.86.

- $i_1 = -2i_2 / R_1 = -2i_2 / 5$

- $i_2 = (V_t - 3i_1) / 4 = (1 + 6i_2 / 5) / 4$   
 $\Rightarrow 14i_2 = 5 \Rightarrow i_2 = 5/14 \text{ A}$

- $R_{th} = V_t / i_2 = 14/5 \Omega = 2.8 \Omega$

FIGURE 4.85

Circuit for  
EXAMPLE 4.11.


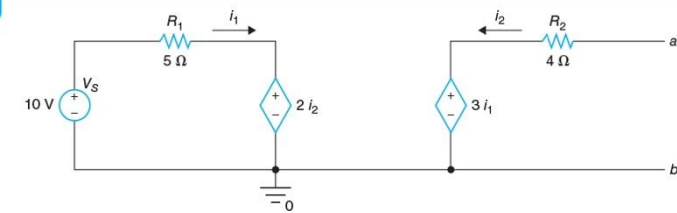


FIGURE 4.86

A circuit with a  
test voltage.

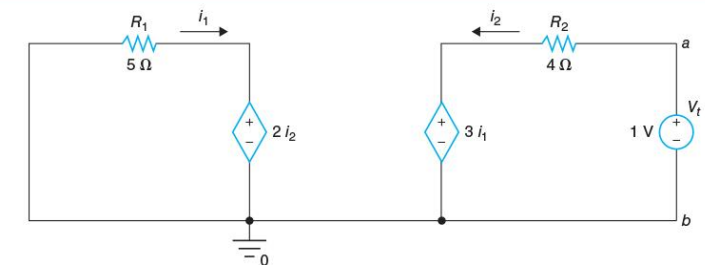


## EXAMPLE 4.12

Find  $V_{th}$  and  $R_{th}$  for the circuit shown in Figure 4.89.

FIGURE 4.89

Circuit for  
EXAMPLE 4.12.

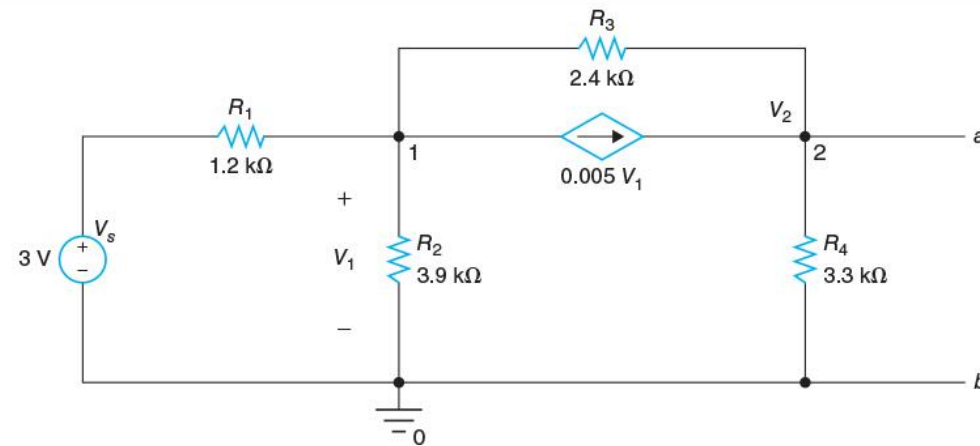



# Summary

- **Thévenin's Theorem:** A circuit consisting of a voltage source  $V_{th}$  and a series resistor  $R_{th}$ , representing the original circuit looking from a pair of terminals, is called a **Thévenin equivalent circuit**. The voltage  $V_{th}$  is called **Thévenin equivalent voltage**, and the resistance  $R_{th}$  is called **Thévenin equivalent resistance**.
- There are three methods to find Thévenin equivalent resistance.
  - **Method 1:** Deactivate all the independent sources by short-circuiting voltage sources and open-circuiting current sources. Find the equivalent resistance looking into the circuit from terminals  $a$  and  $b$ .
  - **Method 2:** Short-circuit terminals  $a$  and  $b$ . Find the short-circuit current  $I_{sc}$ . The Thévenin equivalent resistance is given by  $R_{th} = V_{oc}/I_{sc} = V_{th}/I_{sc}$ .
  - **Method 3:** Deactivate all the independent sources. Apply a test voltage of 1 V between terminals  $a$  and  $b$  with terminal  $a$  connected to the positive terminal of the test voltage. Measure the current flowing out of the positive terminal of the test voltage source. The Thévenin equivalent resistance is the ratio of the voltage to current. Test current can be used also.
- What will we study in next lecture.