

GLASGOW COLLEGE UESTC

Exam paper

Fundamental of Analogue Circuits (UESTC2005)

Date: (remember to complete when info available from Ruoli)

Time: (remember to complete when info available from Ruoli)

Attempt all PARTS. Total 100 marks

**Use one answer sheet for each of the questions in this exam.
Show all work on the answer sheet.**

**Make sure that your University of Glasgow and UESTC Student Identification
Numbers are on all answer sheets.**

**An electronic calculator may be used provided that it does not allow text storage
or display, or graphical display.**

DATA/FORMULAE SHEET IS PROVIDED AT THE END OF PAPER

Q1 Consider the following circuit, where v_i is a small-amplitude input signal, R is a $1\text{k}\Omega$ resistor, C is a capacitor with very large capacitance, V is a 5V DC source, and D is a diode with forward voltage drop of 0.7V when conducting.

(a) Select an appropriate diode model to calculate the DC current I_D through the diode D and the DC output voltage V_D . [6]

(b) Sketch the small-signal equivalent circuit of the circuit. Derive the small signal resistance r_d and small signal gain v_d/v_i . [7]

(c) Using the superposition theorem, determine and sketch the instantaneous output voltage waveform v_D on the diode if the input is $v_i(t) = 0.01\sin(2\pi \times 10^5 t)$. [8]

(d) If C is not ideal (finite capacitance), determine whether the circuit exhibits low-pass, high-pass, or band-pass characteristics for voltage on diode. Justify your reasoning. [4]

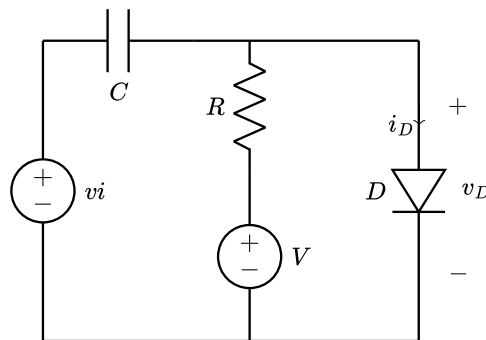


Figure Q1.

Q2 A voltage amplifier shown as Figure Q2 can output the amplified signal to the $4\text{k}\Omega$ load resistor R_L using one N-channel MOSFET with parameters $k_n=1\text{mA/V}^2$, $V_t = 1\text{V}$, $\lambda = 0$, a 5 V DC power supply V_{DD} . $R=1\text{M}\Omega$.

- (a) Specify the value of R_s so that the bias points $I_D=0.5\text{mA}$. [6]
- (b) Choose one of the circuit's MOSFET configuration (common source, common gate, or common drain) and sketch the input signal in Figure Q2. Explain your choice with detailed reasoning. [6]
- (c) Perform small-signal analysis to determine the small signal gain. [7]
- (d) Calculate the input and output resistances of circuit. Evaluate the advantages and disadvantages of the amplifier. [6]

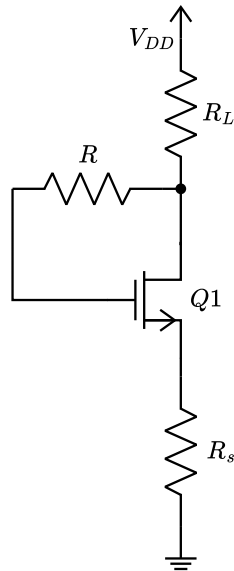


Figure Q2.

Q3 Refer to the 2-stage amplifier circuit in Figure Q3 where the NMOSFETs are characterized by $k_n = 8\text{mA/V}^2$, $V_{tn} = 2.0\text{V}$, and the channel-length modulation can be neglected. $V_{DD}=5\text{V}$.

- Perform DC analysis to calculate each NMOSFETs' V_D , V_G , V_S , and I_D . [8]
- Sketch the small-signal equivalent model of the circuit. [6]
- Using the equivalent model, determine the overall small-signal voltage gain v_o/v_s . [6]
- Determine the input and output resistance of the amplifier and evaluate the total performance of the amplifier. [5]

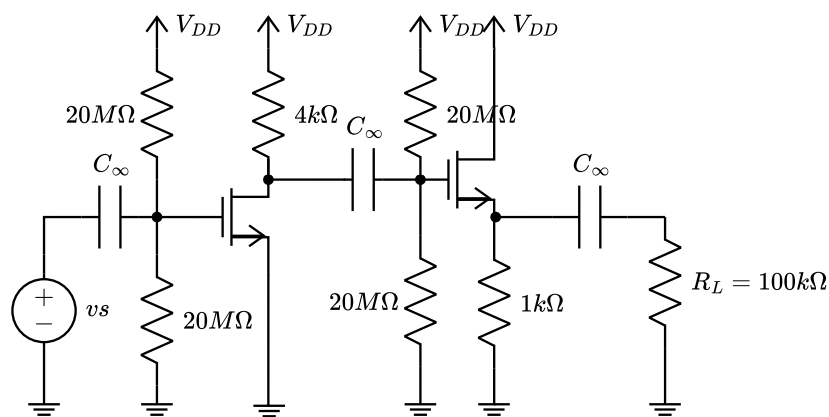


Figure Q3.

Continued overleaf

Q4 A feedback amplifier uses ideal operational amplifier (infinite input resistance, infinite gain, zero output resistance) and a NMOSFET in saturation region as shown in Figure Q4. $R_1=5\text{k}\Omega$, $R_2=10\text{k}\Omega$, $R_f=80\text{k}\Omega$ and load resistance $R_L=2\text{k}\Omega$.

- What is the topology of the feedback? Explain your reasoning. [5]
- Calculate the feedback factor β . [5]
- Determine the closed-loop gain $A_f=V_o/V_s$. [5]
- Find the input resistance R_{in} of the feedback amplifier. [5]
- Find the output resistance R_{out} of the feedback amplifier. [5]

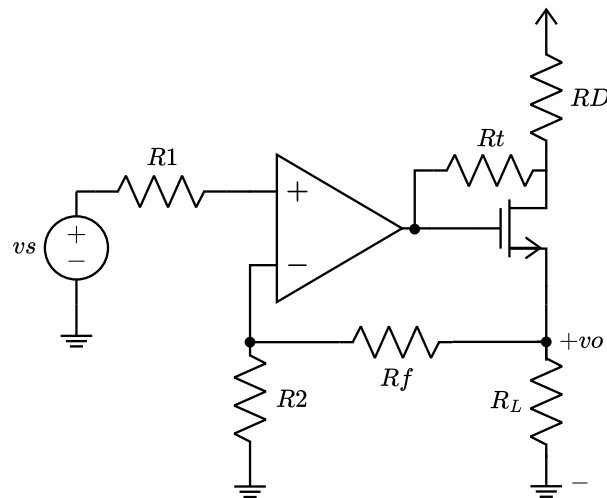


Figure Q4.